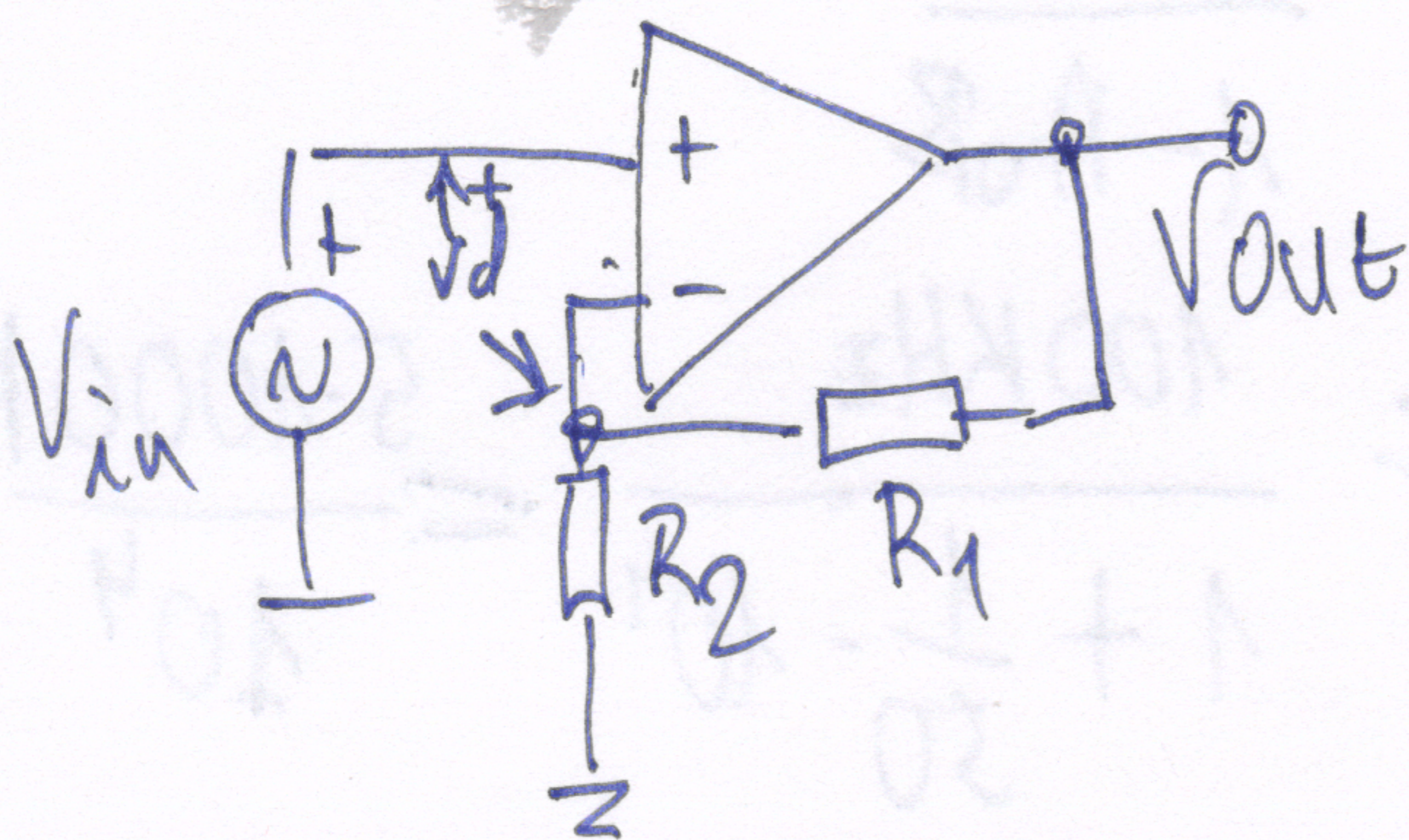


1) Isprojektovati neinvertujući pojačavač sa sledećim specifikacijama: pojačanje u zatvorenoj petlji 50, greška pojačanja 0,5%, širina propusnog opseg u zatvorenoj petlji $BW=100$ kHz. Odrediti pojačanje i širinu propusnog opsega operacionog pojačavača koji bi ispunio zadate zahteve?



$$V_d = V_{in} + \beta \cdot V_{out}$$

$$\beta = -\frac{R_2}{R_1 + R_2}$$

$$V_{out} = A_0 \cdot V_d$$

$$A_0 \cdot V_{in} + A_0 \beta \cdot V_{out} = V_{out}$$

$$V_{out} = \frac{A_0 V_{in}}{1 - A_0 \beta}$$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{A_0}{1 - A_0 \beta}$$

$$\frac{A_0}{1 - A_0 \beta} + \frac{1}{\beta} = \frac{A_0 \beta + 1 - A_0 \beta}{(1 - A_0 \beta) \cdot \beta} = -\frac{1}{\beta}$$

$$\lim_{A_0 \rightarrow \infty} A_{CL} = -\frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$$

$$\delta = \frac{A_{CL} - A_{CL id}}{A_{CL id}} =$$

$$\delta = \frac{1}{A_0 \beta - 1} < \delta_{max}$$

$$A_0 \beta \gg \frac{1}{\delta_{max}} + 1$$

$$A_0 > \frac{1}{\beta} \left(\frac{1}{\delta_{max}} + 1 \right)$$


$$\frac{1}{\beta} = 50 \quad \delta = 5 \cdot 10^{-3}$$

$$A_0 > \frac{50}{5 \cdot 10^{-3}}$$

$$A_0 > 10^4$$

$$f_{CL} = BW > 100 \text{ kHz}$$

$$f_{CL} = f_{OL} (1 - A_0 \beta)$$

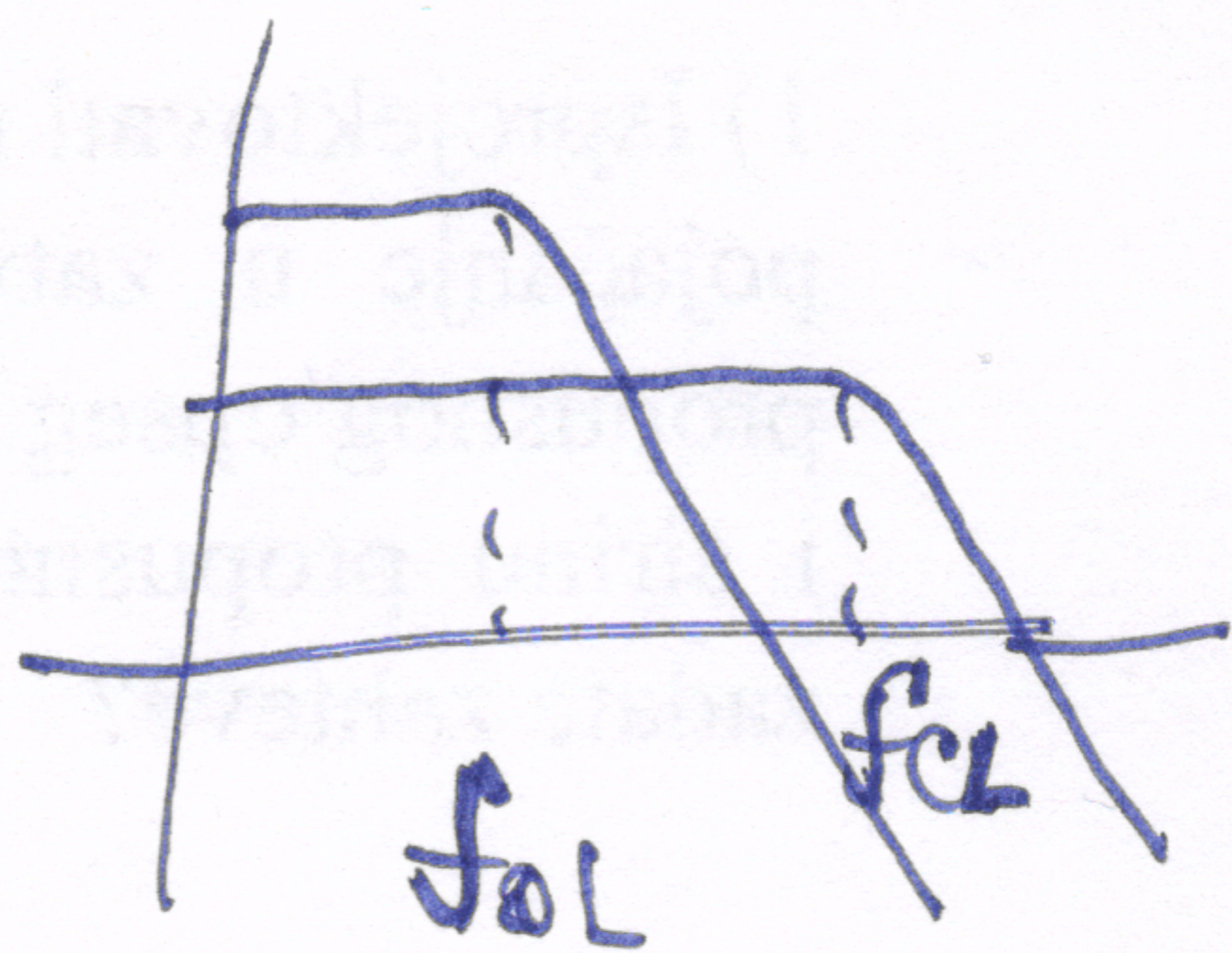


$$f_{OL} \geq \frac{f_{CL}}{1 - A_0 \beta}$$

$$f_{OL} \geq \frac{100 \text{ kHz}}{1 + \frac{1}{50} \cdot 10^4} = \frac{5 \cdot 1000 \text{ kHz}}{10^4}$$

$$\underline{\underline{f_{OL} \geq 500 \text{ Hz}}}$$

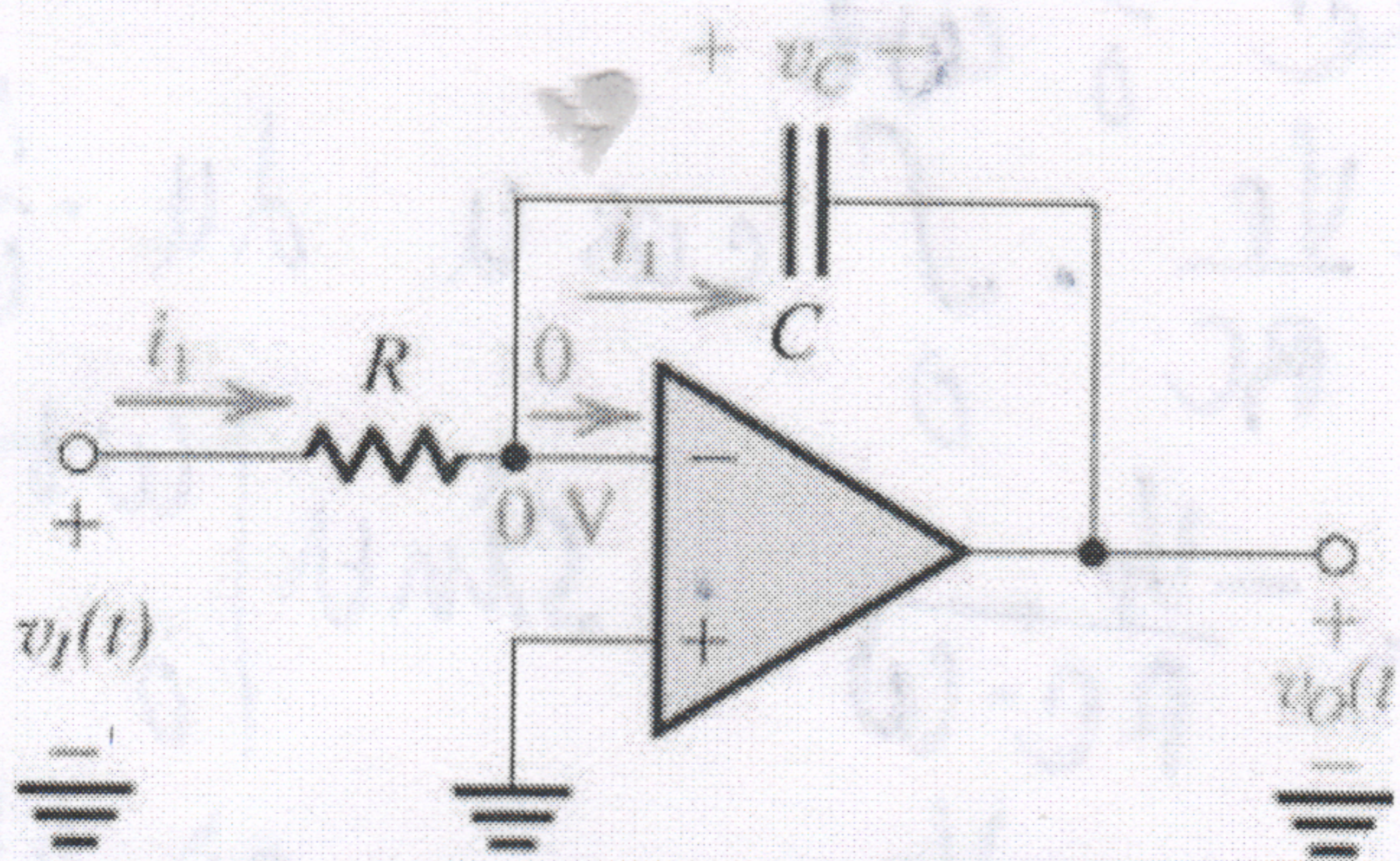2) Isprojektovati integrator čija frekvencija jediničnog pojačanja iznosi 10 kHz i ulazna impedansa 20 kΩ. Operacioni pojačavač ima slew-rate od 0,1 V/μs. Kolo se pobuđuje sinusoidalnim signalom frekvencije 5 kHz. Koliki je najveći opseg promene (peak-to-peak) sinusoidalnog signala na ulazu koji ne prouzrokuje nelinearna izobličenja.



$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{R} \left(-\frac{1}{sC} \right) = \frac{-1}{sCR}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\omega CR}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\omega_T C \cdot R} = 1$$

$$C \cdot R = \frac{1}{2\pi \cdot f_T}$$

$$R_{in} = R = 20 \text{ k}\Omega$$

$$C = \frac{1}{2\pi \cdot f_T \cdot R_{in}}$$

$$C = \frac{1}{6,28 \cdot 10^4 \text{ Hz} \cdot 2 \cdot 10^4 \Omega}$$

$$C = \frac{10^{-8}}{12,56} \text{ F} = 796 \text{ pF}$$

$$V_{in}(t) = V_p \cdot \cos \omega t$$

$$V_{out}(t) = -\frac{1}{C} \int_0^t i_C(\tau) d\tau = -\frac{1}{C} \int_0^t \frac{V_{in}(\tau)}{R} d\tau$$

$$V_{out}(t) = -\frac{1}{RC} \int_0^t V_p \cdot \cos \omega \tau d\tau$$

$$V_{out}(t) = -\frac{V_p}{RC} \int_0^t \cos u du \cdot \frac{1}{\omega}$$

$$V_{out}(t) = -\frac{V_p}{RC \cdot \omega} \cdot \sin u \Big|_0^{\omega t}$$

$$V_{out}(t) = \frac{-V_p}{R \cdot C \cdot \omega} \cdot \sin \omega t$$

$$\frac{dV_{out}(t)}{dt} = \frac{-V_p}{R \cdot C \cdot \omega} \cdot \omega \cdot \cos \omega t$$

$$\frac{dV_{out}(t)}{dt} = \frac{-V_p}{RC} \cdot \cos \omega t$$

$$\left. \frac{dV_{out}}{dt} \right|_{\max} = \frac{V_p}{R \cdot C} < SR$$

$$V_p < SR \cdot R \cdot C$$

$$V_p < 0,1 \frac{V}{\mu s} \cdot 20k\Omega \cdot 796pF$$

$$\underline{\underline{V_p < 1,59 V}}$$