

Projektovanje elektronskih kola

Sadržaj:

1. Uvod - osnovni pojmovi
2. Stilovi projektovanja i izrade prototipova
3. Projektovanje analognih kola
4. Osnove fizičkog projektovanja (projektovanje štampanih ploča)
5. Projektovanje digitalnih kola (vežbe)

LEDA - Laboratory for Electronic Design Automation
<http://leda.elfak.ni.ac.rs/>



14.03.2019.

1

Analiza kola

Analiza kola

Tipovi analize?

Zavisno od vrste pobude, ima smisla analizirati ponašanje kola u

1. jednosmernom domenu (određivanje položaja jednosmerne radne tačke kola).
2. frekvencijskom domenu (frekvencijska karakteristika kola – amplitudska, fazna)
3. vremenskom domenu (talasni oblik napona/struja na izlazu kola pobuđenog impulsima poznatog talasnog oblika)


14.03.2019.

2


Analiza kola

Tipovi analize kola


1. Jednosmerni domen (DC analiza)

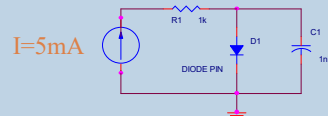

2. Frekvencijski domen (AC analiza)

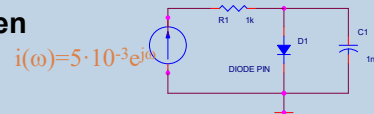

3. Vremenski domen (TR analiza)

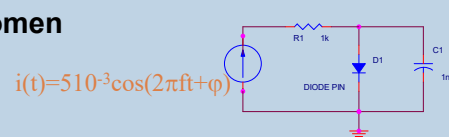

14.03.2019.

3

Analiza kola

Analiza kola

Tipovi analize?

Zavisno od vrste elemenata od kojih se kolo sastoji, različiti tip problema i metoda za analizu

1. Linearna otporna kola (R, linearni generatori, nezavisni i kontrolisani)
2. Linearna reaktivna kola (R, L, C, m, ...)
3. Nelinearna otporna (poluprovodničke komponente, R, ...)
4. Nelinearna reaktivna (poluprovodničke komponente, R, L, C,...)

14.03.2019.

4

Analiza kola

Tipovi elektronskih kola	Tipovi analize kola
1. Linearna otporna R	1. Jednosmerni domen (DC analiza)
2. Linearna reaktivna L, C, m, ...	2. Frekvencijski domen (AC analiza)
3. Nelinearna otporna dioda, tranzistor, R, ...	3. Vremenski domen (TR analiza)
4. Nelinearna reaktivna dioda, tranzistor, R, L, C, ...	

14.03.2019. 5

Projektovanje elektronskih kola

Analiza elektronskih kola

1. Uvod
2. Analiza linearnih kola u DC domenu (jednosmerni režim)
3. Analiza linearnih kola u AC domenu (frekvencijski domen)
4. Analiza linearnih kola u TR domenu (vremenski domen)
5. Analiza nelinearnih kola u DC domenu
6. Analiza nelinearnih kola u TR domenu


14.03.2019. 6

Analiza kola


Analiza elektronskih kola

1. Uvod
2. Analiza linearnih kola u DC domenu (jednosmerni režim)
3. Analiza linearnih kola u AC domenu (frekvencijski domen)
4. Analiza linearnih kola u TR domenu (vremenski domen)
5. Analiza nelinearnih kola u DC domenu
6. Analiza nelinearnih kola u TR domenu

14.03.2019. 7

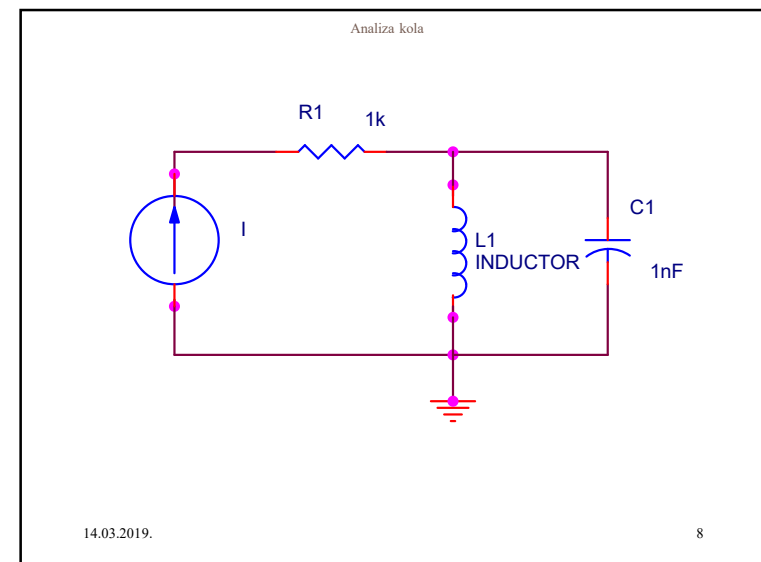

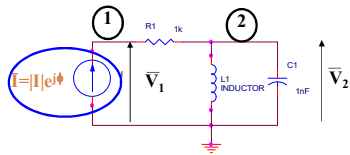Ponašanje linearnih reaktivnih kola u frekvencijskom domenu opisuje se sistemom linearnih algebarskih jednačina sa kompleksnim koeficijentima



$$\frac{\bar{V}_1 - \bar{V}_2}{R_1} = \bar{I}$$

$$\frac{\bar{V}_2 - \bar{V}_1}{R_1} + \frac{\bar{V}_2}{j\omega \cdot L_1} + j\omega \cdot C_1 \bar{V}_2 = 0$$

Tip kola i analize
2. Linearna reaktivna u AC domenu

Matematički model
2. Linearne algebarske jednačine sa kompleksnim koeficijentima

14.03.2019.


Matematički model

2. Linearne jednačine kompleksne
3. Linearne diferencijalne jednačine
4. Nelinearne algebarske jednačine
5. Nelinearne diferencijalne jednačine

Način rešavanja sistema j-na

2. LU faktorizacija (Gauss)
3. Numeričko integraljenje - diskretizacija - svodenje na linearne algebarske (Euler)
4. Linearizacija - iterativno svodenje na linearne algebarske (Newton-Kantorovič)
5. Diskretizacija - svodenje na nelinearne algebarske i linearizacija - iterativno svodenje na linearne algebarske

14.03.2019.

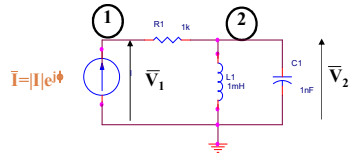

$$\frac{\bar{V}_1 - \bar{V}_2}{R_1} = \bar{I}$$

$$\frac{\bar{V}_2 - \bar{V}_1}{R_1} + \frac{\bar{V}_2}{j\omega \cdot L_1} + j\omega \cdot C_1 \bar{V}_2 = 0$$

$$\frac{1}{R_1} \bar{V}_1 - \frac{1}{R_1} \bar{V}_2 = \bar{I}$$


$$-\frac{1}{R_1} \bar{V}_1 + \left(\frac{1}{R_1} + \frac{1}{j\omega \cdot L_1} + j\omega \cdot C_1 \right) \bar{V}_2 = 0$$

$$10^{-3} \bar{V}_1 - 10^{-3} \bar{V}_2 = \bar{I}$$

$$-10^{-3} \bar{V}_1 + \left(10^{-3} + \frac{1}{j\omega \cdot 10^{-3}} + j\omega \cdot 10^{-9} \right) \bar{V}_2 = 0$$

14.03.2019.

11

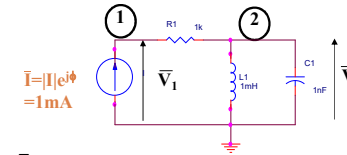

$$\frac{\bar{V}_1 - \bar{V}_2}{R_1} = \bar{I}$$

$$\frac{\bar{V}_2 - \bar{V}_1}{R_1} + \frac{\bar{V}_2}{j\omega \cdot L_1} + j\omega \cdot C_1 \bar{V}_2 = 0$$

$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{j\omega \cdot L_1} + j\omega \cdot C_1 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} \bar{I} \\ 0 \end{bmatrix} \quad \mathbf{Y} \cdot \bar{\mathbf{v}} = \bar{\mathbf{i}}$$

$$\begin{bmatrix} 10^{-3} & -10^{-3} \\ -10^{-3} & 10^{-3} - \frac{j}{\omega \cdot 10^{-3}} + j\omega \cdot 10^{-9} \end{bmatrix} \cdot \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \end{bmatrix}$$

14.03.2019.

12

Analiza kola

$$\bar{\mathbf{I}} = I_0 e^{j\omega t} = 1\text{mA}$$

$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{j\omega \cdot L_1} + j\omega \cdot C_1 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} \bar{\mathbf{I}} \\ \mathbf{0} \end{bmatrix}$$

$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \frac{1}{R_1} + j(\omega \cdot C_1 - \frac{1}{\omega \cdot L_1}) \end{bmatrix} \begin{bmatrix} \mathbf{V}_{1r} + j\mathbf{V}_{1i} \\ \mathbf{V}_{2r} + j\mathbf{V}_{2i} \end{bmatrix} = \begin{bmatrix} \mathbf{I}_r + j\mathbf{I}_i \\ \mathbf{0} \end{bmatrix}$$

$$\begin{bmatrix} 10^{-3} & -10^{-3} \\ -10^{-3} & 10^{-3} + j(\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) \end{bmatrix} \begin{bmatrix} \mathbf{V}_{1r} + j\mathbf{V}_{1i} \\ \mathbf{V}_{2r} + j\mathbf{V}_{2i} \end{bmatrix} = \begin{bmatrix} 10^{-3} + j0 \\ \mathbf{0} \end{bmatrix}$$

14.03.2019. 13

Analiza kola

$$\bar{\mathbf{I}} = I_0 e^{j\omega t}$$

$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{j\omega \cdot L_1} + j\omega \cdot C_1 \end{bmatrix} \begin{bmatrix} \mathbf{V}_{1r} + j\mathbf{V}_{1i} \\ \mathbf{V}_{2r} + j\mathbf{V}_{2i} \end{bmatrix} = \begin{bmatrix} \mathbf{I}_r + j\mathbf{I}_i \\ \mathbf{0} \end{bmatrix}$$

$$\begin{bmatrix} \mathbf{y}_{11r} + j \cdot \mathbf{y}_{11i} & \mathbf{y}_{12r} + j \cdot \mathbf{y}_{12i} \\ \mathbf{y}_{21r} + j \cdot \mathbf{y}_{21i} & \mathbf{y}_{22r} + j \cdot \mathbf{y}_{22i} \end{bmatrix} \cdot \begin{bmatrix} \mathbf{V}_{1r} + j \cdot \mathbf{V}_{1i} \\ \mathbf{V}_{2r} + j \cdot \mathbf{V}_{2i} \end{bmatrix} = \begin{bmatrix} \mathbf{I}_r + j \cdot \mathbf{I}_i \\ \mathbf{0} \end{bmatrix}$$

$$(\tilde{\mathbf{Y}}_r + j \cdot \tilde{\mathbf{Y}}_i) \cdot (\mathbf{v}_r + j \cdot \mathbf{v}_i) = \mathbf{i}_r + j \cdot \mathbf{i}_i$$

$$\begin{bmatrix} \tilde{\mathbf{Y}}_r & -\tilde{\mathbf{Y}}_i \\ \tilde{\mathbf{Y}}_i & \tilde{\mathbf{Y}}_r \end{bmatrix} \cdot \begin{bmatrix} \mathbf{v}_r \\ \mathbf{v}_i \end{bmatrix} = \begin{bmatrix} \mathbf{i}_r \\ \mathbf{i}_i \end{bmatrix}; \quad \text{ili} \quad \begin{bmatrix} -\tilde{\mathbf{Y}}_i & \tilde{\mathbf{Y}}_r \\ \tilde{\mathbf{Y}}_r & -\tilde{\mathbf{Y}}_i \end{bmatrix} \cdot \begin{bmatrix} \mathbf{v}_i \\ \mathbf{v}_r \end{bmatrix} = \begin{bmatrix} \mathbf{i}_i \\ \mathbf{i}_r \end{bmatrix}$$

14.03.2019. 14

Analiza kola

$$\bar{\mathbf{I}} = I_0 e^{j\omega t}$$

$$\begin{bmatrix} 10^{-3} & -10^{-3} \\ -10^{-3} & 10^{-3} + j(\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) \end{bmatrix} \begin{bmatrix} \mathbf{V}_{1r} + j\mathbf{V}_{1i} \\ \mathbf{V}_{2r} + j\mathbf{V}_{2i} \end{bmatrix} = \begin{bmatrix} 10^{-3} + j0 \\ \mathbf{0} \end{bmatrix}$$

$$\tilde{\mathbf{Y}}_r = \begin{bmatrix} 10^{-3} & -10^{-3} \\ -10^{-3} & 10^{-3} \end{bmatrix} \quad \text{i} \quad \tilde{\mathbf{Y}}_i = \begin{bmatrix} 0 & 0 \\ 0 & j(\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) \end{bmatrix}$$

14.03.2019. 15

Analiza kola

$$\bar{\mathbf{I}} = I_0 e^{j\omega t}$$

$$\begin{bmatrix} \tilde{\mathbf{Y}}_r & -\tilde{\mathbf{Y}}_i \\ \tilde{\mathbf{Y}}_i & \tilde{\mathbf{Y}}_r \end{bmatrix} \cdot \begin{bmatrix} \mathbf{v}_r \\ \mathbf{v}_i \end{bmatrix} = \begin{bmatrix} \mathbf{i}_r \\ \mathbf{i}_i \end{bmatrix}$$

$$\left[\begin{array}{cc|cc} 10^{-3} & -10^{-3} & 0 & 0 \\ -10^{-3} & 10^{-3} & 0 & -(\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) \\ \hline 0 & 0 & 10^{-3} & -10^{-3} \\ 0 & (\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) & -10^{-3} & 10^{-3} \end{array} \right] \begin{bmatrix} \mathbf{v}_{1r} \\ \mathbf{v}_{2r} \\ \mathbf{v}_{1i} \\ \mathbf{v}_{2i} \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Red matrice 2x veći, ali je gustina matrice manja

14.03.2019. 16

Analiza kola

Za $\omega=10^3\text{rad/s}$

$$\begin{bmatrix} 10^{-3} & -10^{-3} & 0 & 0 \\ -10^{-3} & 10^{-3} & 0 & -(10^{-6}-1) \\ 0 & 0 & 10^{-3} & -10^{-3} \\ 0 & (10^{-6}-1) & -10^{-3} & 10^{-3} \end{bmatrix} \cdot \begin{bmatrix} v_{1r} \\ v_{2r} \\ v_{1i} \\ v_{2i} \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Za $\omega=10^6\text{rad/s}$

$$\begin{bmatrix} 10^{-3} & -10^{-3} & 0 & 0 \\ -10^{-3} & 10^{-3} & 0 & -(0) \\ 0 & 0 & 10^{-3} & -10^{-3} \\ 0 & (0) & -10^{-3} & 10^{-3} \end{bmatrix} \cdot \begin{bmatrix} v_{1r} \\ v_{2r} \\ v_{1i} \\ v_{2i} \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Za $\omega=10^9\text{rad/s}$

$$\begin{bmatrix} 10^{-3} & -10^{-3} & 0 & 0 \\ -10^{-3} & 10^{-3} & 0 & -(1-10^6) \\ 0 & 0 & 10^{-3} & -10^{-3} \\ 0 & (1-10^6) & -10^{-3} & 10^{-3} \end{bmatrix} \cdot \begin{bmatrix} v_{1r} \\ v_{2r} \\ v_{1i} \\ v_{2i} \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

14.03.2019. 17

Analiza kola

$\begin{bmatrix} -\tilde{Y}_i & \tilde{Y}_r \\ \tilde{Y}_i & \tilde{Y}_r \end{bmatrix} \cdot \begin{bmatrix} \tilde{v}_i \\ \tilde{v}_r \end{bmatrix} = \begin{bmatrix} \tilde{i}_r \\ \tilde{i}_i \end{bmatrix}$

$$\left[\begin{array}{cc|cc} 0 & 0 & 10^{-3} & -10^{-3} \\ 0 & -(\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) & -10^{-3} & 10^{-3} \\ \hline 10^{-3} & -10^{-3} & 0 & 0 \\ -10^{-3} & 10^{-3} & 0 & (\omega \cdot 10^{-9} - \frac{1}{\omega \cdot 10^{-3}}) \end{array} \right] \cdot \begin{bmatrix} v_{1i} \\ v_{2i} \\ v_{1r} \\ v_{2r} \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

14.03.2019. 18

Analiza kola

Za $\omega=10^6\text{rad/s}$

$$\begin{bmatrix} 0 & 0 & 10^{-3} & -10^{-3} \\ 0 & -(0) & -10^{-3} & 10^{-3} \\ 10^{-3} & -10^{-3} & 0 & 0 \\ -10^{-3} & 10^{-3} & 0 & (0) \end{bmatrix} \cdot \begin{bmatrix} v_{1i} \\ v_{2i} \\ v_{1r} \\ v_{2r} \end{bmatrix} = \begin{bmatrix} 10^{-3} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

14.03.2019. 19

Analiza kola


Šta može Spice?

Primer analize AC linearni

.ac dec 5 10 500k

21.03.2019. 20


Šta može Spice?

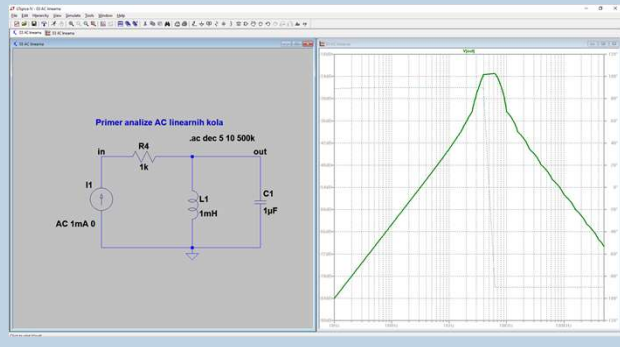

21.03.2019.

21


Šta može Spice?

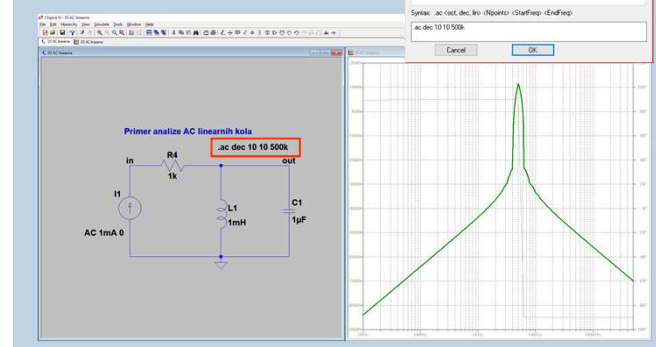

21.03.2019.

22

Šta može Spice?

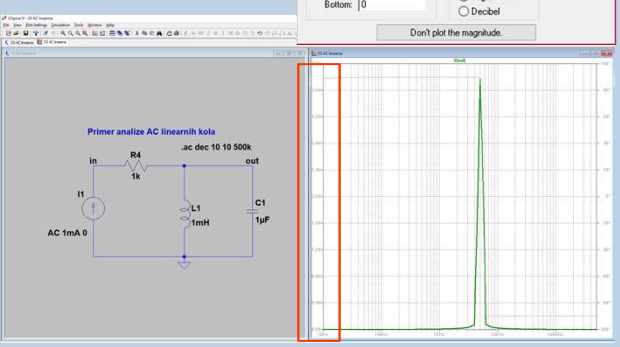


21.03.2019.

23

Postoji potpuna korespondencija sa elementima linearnih otpornih kola

$$Z_C = 1/j\omega C$$


$$Z_L = j\omega L$$

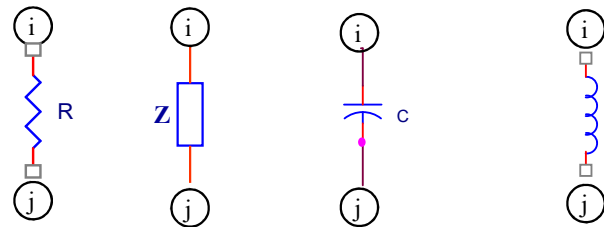

14.03.2019.

24

Sprengnute induktivnosti

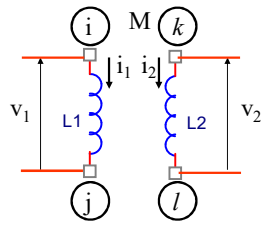

$$V_1 = j\omega L_1 i_1 + j\omega M i_2$$


$$V_2 = j\omega M i_1 + j\omega L_2 i_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

14.03.2019.

25

Sprengnute induktivnosti

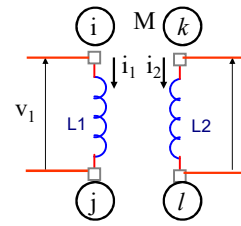

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{j\omega} \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}^{-1} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} =$$


$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{j\omega(L_1 L_2 - M^2)} \begin{bmatrix} L_2 & -M \\ -M & L_1 \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

14.03.2019.

26

Automatizacija formulacije jednačina

Sprengnute induktivnosti

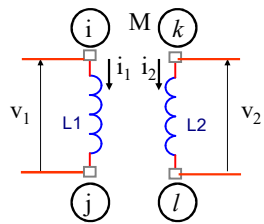

$$i_1 = \frac{1}{j\omega L_{11}} V_1 - \frac{1}{Z} V_2$$

$$i_2 = -\frac{1}{Z} V_1 + \frac{1}{j\omega L_{22}} V_2$$

$$L_{11} = \frac{L_1 L_2 - M^2}{L_2}$$


$$L_{22} = \frac{L_1 L_2 - M^2}{L_1}$$

$$Z = j\omega \frac{L_1 L_2 - M^2}{M}$$

14.03.2019.


27

Sprengnute induktivnosti

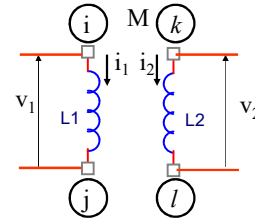

$$i_1 = \frac{1}{j\omega L_{11}} V_1 - \frac{1}{Z} V_2$$
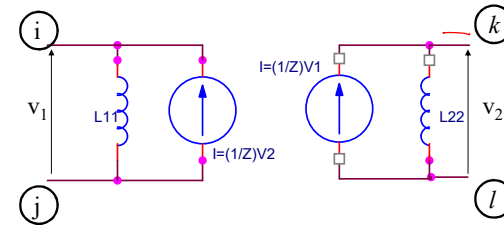
$$i_2 = -\frac{1}{Z} V_1 + \frac{1}{j\omega L_{22}} V_2$$



14.03.2019.

28

Analiza kola

Transformator

$$I_{ul} = -nI_{iz}$$

$$n(V_i - V_j) = V_k - V_l$$

14.03.2019. 29

Analiza kola

Transformator

$$I_{ul} = -nI_{iz}$$

$$n(V_i - V_j) = V_k - V_l$$

14.03.2019. 30

Analiza kola

Šta može Spice?

21.03.2019. 31

Analiza kola

Šta može Spice?

21.03.2019. 32


Kako se predstavljaju nelinearne komponente:

- Diode
- BJT
- MOST

pri AC analizi?

Predstavljaju se modelima za male signale
(kako mali signal vidi nelinearnu karakteristiku)


-Dioda u elektronskom kolu

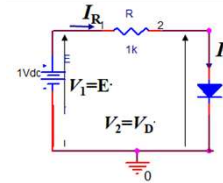

Model diode – **nelinearan** – za **velike signale**

$$\frac{E - V_D}{R} = I_R$$



$$I_D = I_S (e^{\frac{V_D}{V_T}} - 1)$$

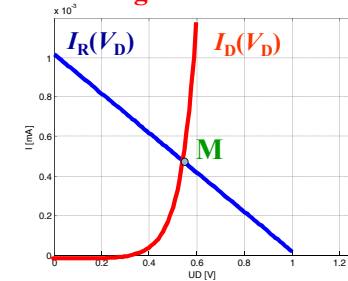

Dioda


-Dioda u elektronskom kolu

Grafička interpretacija problema

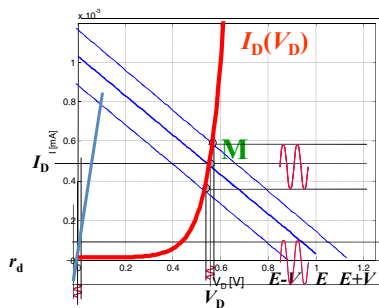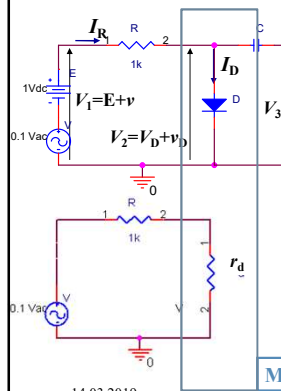

Model za male signale


Dioda **VAŽNO** model za male signale

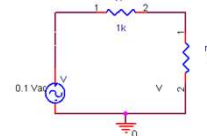

koristi se u analizi ponašanja kola pobuđenih malim naizmeničnim signalima.

Tada se svi elementi kola zamenjuju **dinamičkim parametrima**

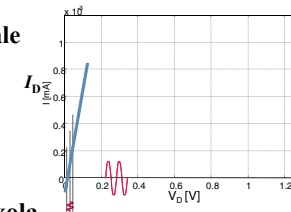Dinamički parametar diode jeste **unutrašnja otpornost diode u radnoj tački.**



$$r_d = \frac{dV_D}{dI_D} \approx \frac{\Delta V_D}{\Delta I_D}$$

$$r_d = \frac{1}{\frac{dI_D}{dV_D}} \approx \frac{1}{I_S e^{V_D/V_T} \frac{1}{V_T}}$$

$$r_d \approx \frac{V_T}{I_D}$$


Dioda Spice model

Diode SPICE parameters

Symbol	Name	Parameter	Units	Default
I _s	IS	Saturation current (diode equation)	A	1E-14
R _s	RS	Parasitic resistance (series resistance)	Ω	0
n	N	Emission coefficient, 1 to 2	-	1
τ ₀	TT	Transit time	s	0
C ₀ (0)	CJO	Zero-bias junction capacitance	F	0
φ _b	VJ	Junction potential	V	1
m	M	Junction grading coefficient	-	0.5
-	-	0.33 for linearly graded junction	-	-
-	-	0.5 for abrupt junction	-	-
E _g	EG	Activation energy:	eV	1.11
-	-	Si: 1.11	-	-
-	-	Ge: 0.67	-	-
-	-	Schottky: 0.69	-	-
p _i	XTI	IS temperature exponent	-	3.0
-	-	pn junction: 3.0	-	-
-	-	Schottky: 2.0	-	-
k _f	KF	Flicker noise coefficient	-	0
a _f	AF	Flicker noise exponent	-	1
FC	FC	Forward bias depletion capacitance coefficient	-	0.5
BV	BV	Reverse breakdown voltage	V	∞
IBV	IBV	Reverse breakdown current	A	1E-3

14.03.2019.

Model MOS tranzistora za male signale

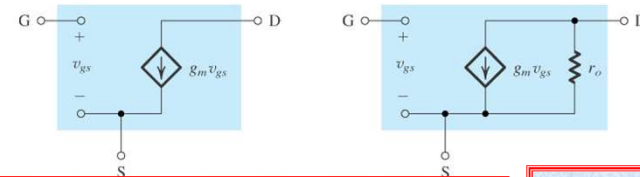

$$g_m = \mu_n C'_{ox} \frac{W}{L} (V_{GS} - V_t) = \frac{2I_D}{(V_{GS} - V_t)} = \frac{2I_D}{V_{OV}} \quad r_o = \frac{V_A}{I_D}$$


$$\left(g_m r_o \equiv \mu = \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{DS}}{\partial I_D} = \frac{\partial V_{DS}}{\partial V_{GS}} = \frac{2V_A}{(V_{GS} - V_t)} \right) \quad (r_o \equiv R_i)$$

14.03.2019.

MOS tranzistor Spice model

14.03.2019.

Tranzistor

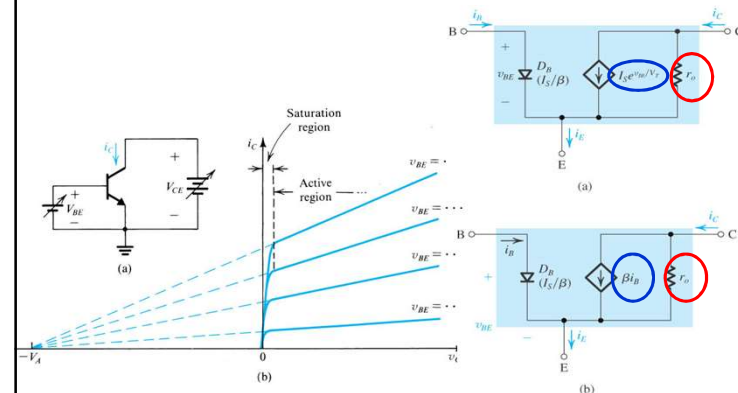

14.03.2019.

40

BJT Spice model

Pri AC analizi sve komponente se zamenjuju linearnim modelima!

- AC podrazumeva analizu LINEARNIH kola
- Sadrže reaktivne komponente (L i C)


Njih opisuje sistem linearnih algebarskih jednačina sa kompleksnim koeficijentima.

Rešavaju se LU faktorizacijom (Gaus)

Izazovi i specifičnosti AC analize?

Izazovi i specifičnosti AC analize?

Primer

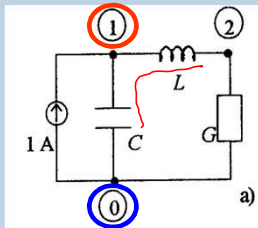


$$\begin{bmatrix} j\omega C - j\frac{1}{\omega L} & j\frac{1}{\omega L} \\ j\frac{1}{\omega L} & G - j\frac{1}{\omega L} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

Izazovi i specifičnosti AC analize?

Izazovi i specifičnosti AC analize?

Primer

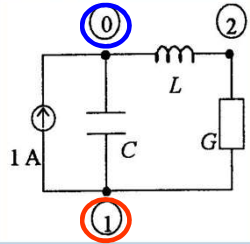


$$\begin{bmatrix} j\omega \cdot C + G & -G \\ -G & G - \frac{j}{\omega \cdot L} \end{bmatrix} \begin{bmatrix} \overline{V}_1 \\ \overline{V}_2 \end{bmatrix} = \begin{bmatrix} -\overline{I} \\ 0 \end{bmatrix}$$

14.03.2019.

45

Izazovi i specifičnosti AC analize?

Primer

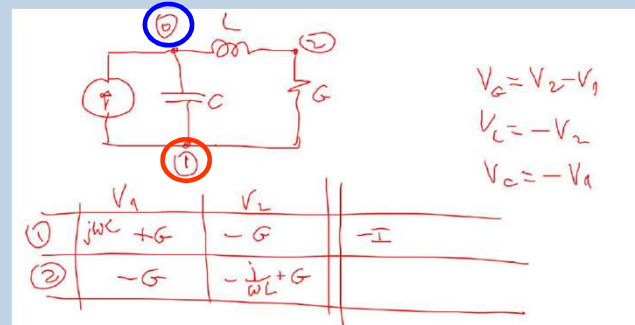

14.03.2019.

46

Karakteristike analize u AC domenu:

Analiza od f_d do f_g

Voditi računa o veličini koraka i veličini propusnog opsega kola koje se analizira.

Svi modeli poluprovodničkih komponenata su linearni i malosignalni. U Spice-u uvek se najpre obavi DC analiza, da bi se odredio položaj radne tačke, a zatim se izračunavaju parametri modela.

14.03.2019.

47

Izbor koraka frekvencije

Logaritamska skala





Broj tačaka po dekadi/oktavi

Linearna skala

$$\Delta_f = (f_g - f_d) / N$$

14.03.2019.


48

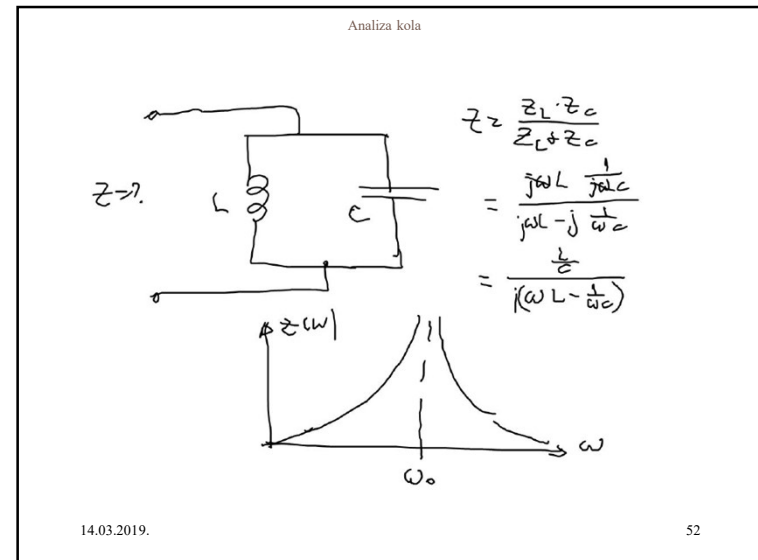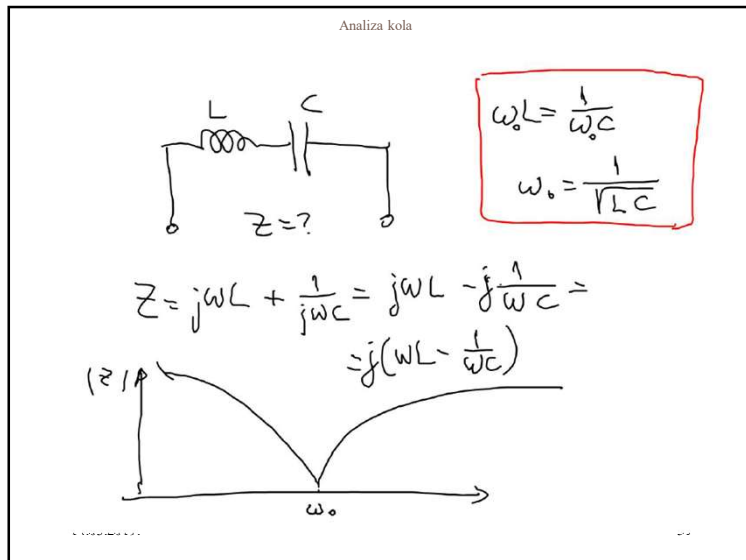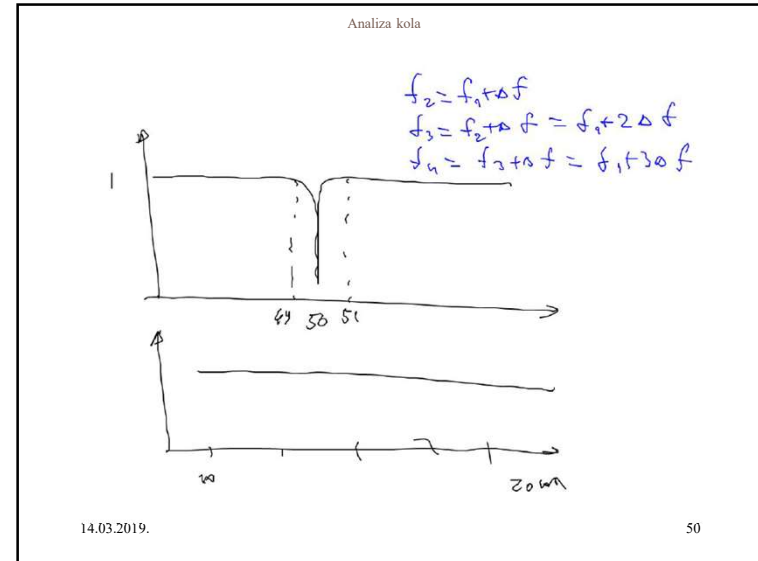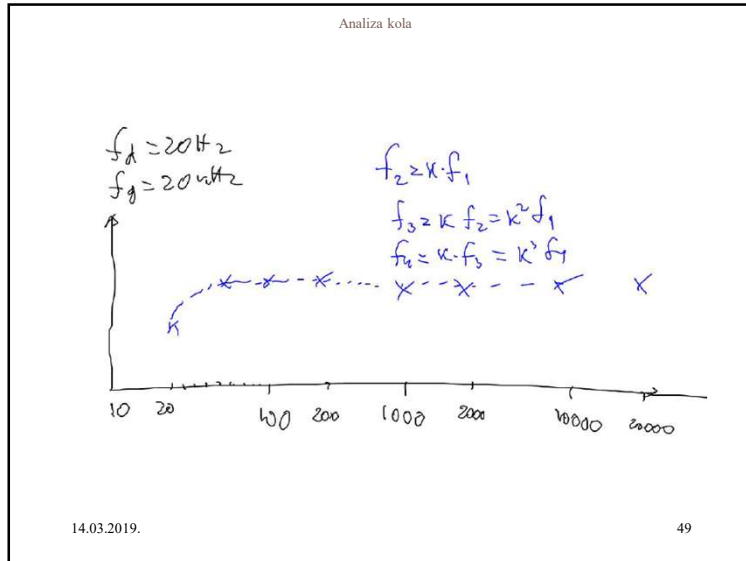


Analiza kola

Analiza VF kola - parazitni efekti


R

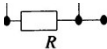

C

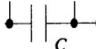

L

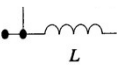


14.03.2019. 53


Analiza kola

Analiza VF kola - parazitni efekti


R

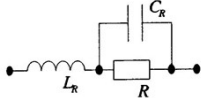

C

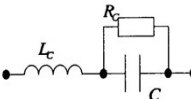


L

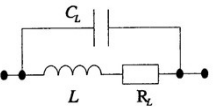

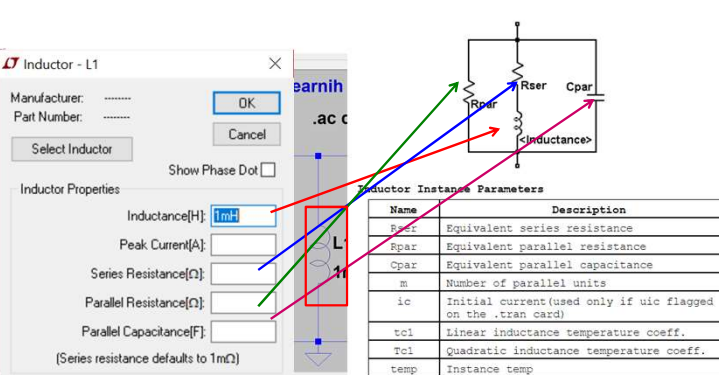14.03.2019. 54

Analiza kola

Analiza VF kola - parazitni efekti LTSpice



The screenshot shows the 'Inductor - L1' properties dialog box with the following fields:

- Inductance[H]: 1mH
- Peak Current[A]:
- Series Resistance[Ω]:
- Parallel Resistance[Ω]:
- Parallel Capacitance[F]:


The schematic shows an inductor model with parameters: Rpar, Rser, Cpar, and Inductance. A table of parameters is shown below:

Name	Description
Rser	Equivalent series resistance
Rpar	Equivalent parallel resistance
Cpar	Equivalent parallel capacitance
m	Number of parallel units
ic	Initial current (used only if uic is flagged on the .tran card)
tcl	Linear inductance temperature coeff.
tcq	Quadratic inductance temperature coeff.
temp	Instance temp

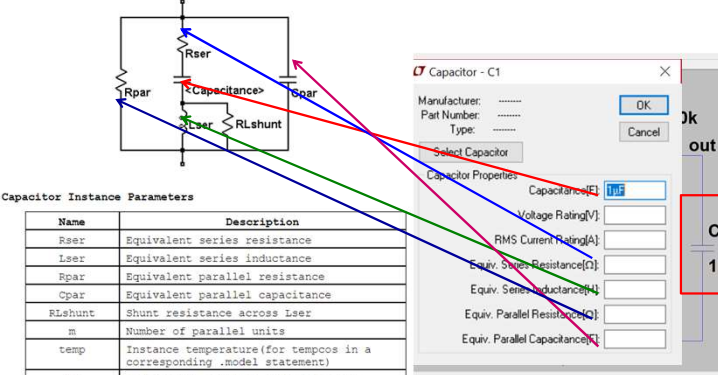14.03.2019. 55

Analiza kola

Analiza VF kola - parazitni efekti LTSpice



The screenshot shows the 'Capacitor - C1' properties dialog box with the following fields:

- Capacitance[F]: 1μF
- Voltage Rating[V]:
- RMS Current Rating[A]:
- Equiv. Series Resistance[Ω]:
- Equiv. Parallel Resistance[Ω]:
- Equiv. Parallel Capacitance[μF]:

The schematic shows a capacitor model with parameters: Rpar, Rser, RLshunt, and Cpar. A table of parameters is shown below:

Name	Description
Rser	Equivalent series resistance
Lser	Equivalent series inductance
Rpar	Equivalent parallel resistance
Cpar	Equivalent parallel capacitance
RLshunt	Shunt resistance across Lser
m	Number of parallel units
temp	Instance temperature (for tempcos in a corresponding .model statement)
ic	Initial voltage (used only if uic is flagged on the .tran card)

14.03.2019. 56

Analiza kola

Spice:
Koje parametre treba zadati da bi se kolo analiziralo u AC domenu?

- Tip analize: AC
- Parametri generatora: magnituda i faza
- Donja granična frekvencija
- Gornja granična frekvencija
- Broj tačaka:
 - Linearno
 - Logaritamski
 - (po dekadi)
 - (po oktavi)

14.03.2019. 57

Analiza kola

Šta može Spice?

Primer AC analiza nelinearnog kola
Nelinearne komponente su zamenjene linearnim modelima
parametri linearnih modela izracunavaju se u radnoj tacki
zato AC analizi prethodi DC analiza nelinearnih kola

Primer dodavanja nove biblioteke

14.03.2019. 58

Analiza kola

Šta može Spice?

Primer AC analiza nelinearnog kola
Nelinearne komponente su zamenjene linearnim modelima
parametri linearnih modela izracunavaju se u radnoj tacki
zato AC analizi prethodi DC analiza nelinearnih kola

14.03.2019. 59


Analiza kola

Šta može Spice?

Primer AC analiza nelinearnog kola
Nelinearne komponente su zamenjene linearnim modelima
parametri linearnih modela izracunavaju se u radnoj tacki
zato AC analizi prethodi DC analiza nelinearnih kola

14.03.2019. 60


Šta može Spice?

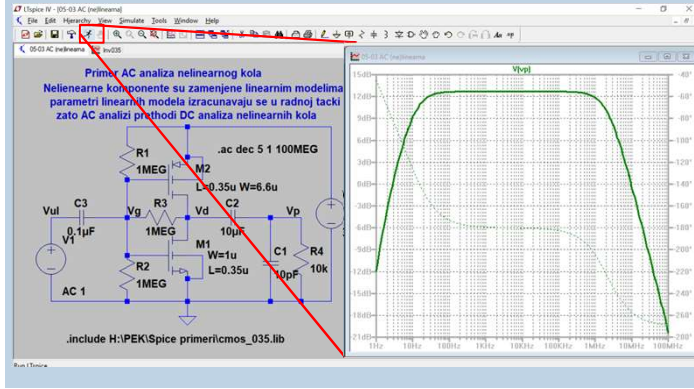

14.03.2019.

61


Šta može Spice?

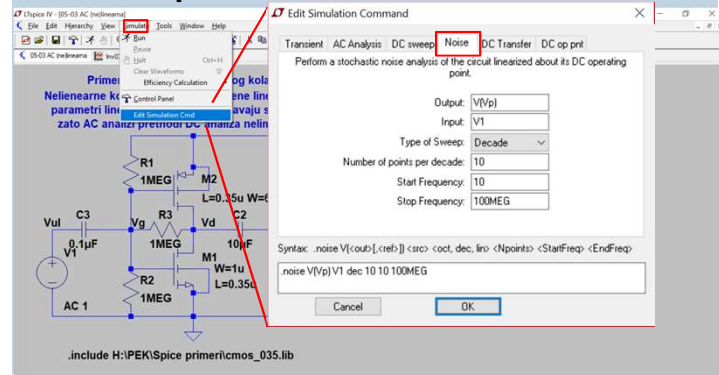

14.03.2019.

62

Šta može Spice?

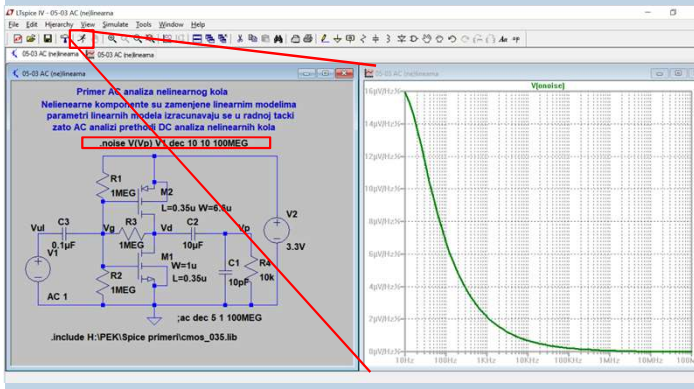

14.03.2019.

63

Analiza linearnih kola u AC domenu

Šta treba da znamo?

Elementarno (za potpis)

Šta se dobija kao rezultat analize u frekvencijskom domenu?

Osnovna (za 6)

1. Koje parametre treba zadati da bi se u programu Spice analiziralo kolo u frekvencijskom domenu?
2. Kakvi se modeli poluprovodničkih komponenta koriste pri AC analizi?

64

Analiza linearnih kola u AC domenu

Ispitna pitanja

- a) Koliko puta se formira i rešava sistem jednačina pri jednoj analizi kola u AC režimu ukoliko se traži analiza u 4 tačke po dekadi u opsegu od 5Hz do 50kHz/Koliko puta se formira i rešava sistem jednačina pri jednoj analizi kola u AC režimu ukoliko se traži analiza u 2 tačke po oktavi u opsegu od 5Hz do 50kHz?
- b) Koji su karakteristični problemi vezani za zadavanje koraka u AC analizi?
- c) Koji su karakteristični problemi vezani za rezonantnu frekvenciju u AC analizi? Kako ih izbeći?