

Deo 1: Modelovanje kombinacione logike u VHDL-u

1.1 Entiteti i arhitekture

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity and2 is
    port(x,y:in bit; z:out bit);
end entity and2;

architecture ex1 of and2 is
begin
    z<=x and y;
end architecture ex1;
```

1.2 Identifikatori, komentari i razmaci

1.3 Netliste

--- $Z=(\text{not } A \text{ and } B) \text{ or } (A \text{ and } C)$

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity comb_function is
    port(a,b,c:in bit; z:out bit);
end entity comb_function;

architecture expression of comb_function is
begin
    z<=(not a and b) or (a and c);
end architecture expression;
-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity or2 is
    port(x,y:in bit; z:out bit);
end entity or2;

architecture ex1 of or2 is
begin
    z<=x or y;
end architecture ex1;
-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity not1 is
    port( x : in bit; z : out bit);
end entity not1;

architecture ex1 of not1 is
begin
```

```

        z<=not x;
end architecture ex1;
-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity comb_function is
    port(a,b,c:in bit; z:out bit);
end entity comb_function;

architecture netlist of comb_function is

    component and2 is
        port(x,y:in bit; z:out bit);
    end component and2;
    component or2 is
        port(x,y:in bit; z:out bit);
    end component or2;
    component not1 is
        port(x:in bit; z:out bit);
    end component not1;

    signal p,q,r :bit;

begin
    lab1: not1 port map(a,p);
    lab2: and2 port map (p,b,q);
    lab3: and2 port map(a,c,r);
    lab4: or2 port map (q,r,z);
end architecture netlist;
-----

lab2: and2 port map (z=>q, x=>p, y=>b);

architecture direct of comb_function is
    signal p,q,r :bit;
begin
    lab1: entity work.not1(ex1) port map(a,p);
    lab2: entity work.and2(ex1) port map (p,b,q);
    lab3: entity work.and2(ex1) port map(a,c,r);
    lab4: entity work.or2(ex1) port map (q,r,z);
end architecture direct;

```

1.4 Dodeljivanje vrednosti signalima

```

z<=x and y;

z<=x;

z<=not (( x and y) or (a and b));

z<=x after 4 ns;

z<= transport x after 4 ns;

z<=x and y after 5 ns;

z<= transport not ((x and y) or (a and b)) after 5 ns;

```

```
z<= x after 4 ns, not x after 8 ns;
```

1.5 Generici

```
z<=x and y after 5 ns;
z<=x and y after delay;
-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity and2 is
    generic(delay:time);
    port(x,y:in bit; z:out bit);
end entity and2;

architecture ex2 of and2 is
begin
    z<=x and y after delay;
end architecture ex2;
-----

lab1: and2 generic map (5 ns) port map (p,b,q);

lab2: and2 generic map (delay=> 5 ns) port map(z=>q, x=>p, y=>b);

generic(delay:time:=5ns);

lab3: and2 port map (p,b,q);

lab4: and2 generic map (3 ns) port map (p,b,q);

lab5: and2 generic map (open) port map (p,b,q);
```

1.6 Konstantni i otvoreni portovi

```
-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity universal is
    port(x,y,invert:in bit; a,o:out bit);
end entity universal;

architecture univ of universal is
begin
    a<=(y and (x xor invert)) or (invert and not y);
    o<=(not x and (y xor invert)) or (x and not invert);
end architecture univ;
-----

u0: universal port map (x,y,'0',a,open);

entity universal is
    port( x,y:in bit;
          invert:in bit:='0');
end entity universal;
```

```

        a,o:out bit);
end entity universal;

u0: universal port map (x,y,open,a,open);

```

1.7 Testbenčevi

```

-----
library ieee;
use ieee.std_logic_1164.all;

entity and2_tb is
end entity and2_tb;

architecture TB_ARCHITECTURE_1 of and2_tb is
    component and2
        port( x,y : in BIT; z : out BIT );
    end component;
    signal a,b,c : BIT;
begin

    lab1 : and2 port map (x => a,y => b,z => c);
    a<='0','1' after 100 ns;
    b<='0','1' after 150 ns;

end architecture TB_ARCHITECTURE_1;
-----

```

1.8 Konfiguracije

```

-----
architecture ex3 of and2 is
    signal xy : bit_vector(0 to 1);
begin
    xy<=x&y;
    with xy select
        z<='1' when "11",
        '0' when others;
end architecture ex3;
-----

lab1: entity work.not1(ex1) port map (a,p);

for lab1:and2 use entity work.and2(ex1);

-----
library ieee;
use ieee.std_logic_1164.all;

entity and2_tb is
end entity and2_tb;

architecture TB_ARCHITECTURE_2 of and2_tb is
    component and2
        port( x,y : in BIT; z : out BIT );
    end component;
    for all: and2 use entity work.and2(ex1);

```

```

        signal a,b,c : BIT;
begin
    lab1 : and2 port map (x => a,y => b,z => c);
    a<='0','1' after 100 ns;
    b<='0','1' after 150 ns;

end architecture TB_ARCHITECTURE_2;

```

```

-----
configuration Konfiguracija1 of and2_tb is
    for TB_ARCHITECTURE_1
        for lab1 : and2
            use entity work.and2(ex1);
        end for;
    end for;
end Konfiguracija1;

```

```

-----

library ieee;
use ieee.std_logic_1164.all;

```

```

entity and2_tb is
end entity and2_tb;

```

```

architecture TB_ARCHITECTURE_3 of and2_tb is
    component and2
        generic(dly:time);
        port( in1,in2 : in BIT; out1 : out BIT );
    end component and2;
    signal a,b,c : BIT;
begin

```

```

    lab1 : and2 generic map(6 ns) port map (a,b,c);
    a<='0','1' after 100 ns;
    b<='0','1' after 150 ns;

```

```

end architecture TB_ARCHITECTURE_3;

```

```

configuration Konfiguracija2 of and2_tb is
    for TB_ARCHITECTURE_3
        for lab1 : and2
            use entity work.and2(ex2)
            generic map(delay=>dly)
            port map (x=>in1,y=>in2,z=>out1);
        end for;
    end for;
end Konfiguracija2;

```

Deo 2: Kombinacioni blokovi

2.1 *Three-state* baferi

2.1.1 Višeznačna logika

```
type tri is ('0','1','Z');

signal a,b,c : tri;

a<='0' and '1';
b<=a or c after 5 ns;

function "and" (Left,Right:tri) return tri is
type tri_array is array(tri,tri) of tri;
constant and_table : tri_array:=(('0','0','0'),
                                   ('0','1','1'),
                                   ('0','1','1'));

begin
  return and_table(Left, Right);
end function "and";
```

2.1.2 *Standard logic package*

```
library ieee;
use ieee.std_logic_1164.all;
```

2.1.2 *When ... else* naredba

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity three_state is
  port(a,enable:in std_ulogic; z:out std_ulogic);
end entity three_state;

architecture when_else of three_state is
begin
  z<=a when enable = '1' else 'Z';
end architecture when_else;

architecture after_when_else of three_state is
begin
  z<=a after 5 ns when enable = '1' else 'Z';
end architecture after_when_else;
```

2.2 Dekoderi

2.2.1 2 u 4 dekodier

```
type std_ulogic_vector is array ( natural range <>) of std_ulogic;
type std_logic_vector is array ( natural range <>) of std_logic;
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder is
    port( a : in  std_ulogic_vector(1 downto 0);
          z : out std_ulogic_vector(3 downto 0));
end entity decoder;

architecture when_else of decoder is
begin
    z<="0001" when a = "00" else
      "0010" when a = "01" else
      "0100" when a = "10" else
      "1000" when a = "11" else
      "XXXX";
end architecture when_else;
-----

    z<="0001" when a = "00" else
      "0010" when a = "01" else
      "0100" when a = "10" else
      "1000" when a = "11";

    z<="0001" when a = "00" else
      "0010" when a = "01" else
      "0100" when a = "10" else
      "1000" when a = "11" else
      unaffected;

    z<="0001" when a = "00" else
      "0010" when a = "01" else
      "0100" when a = "10" else
      "1000" when a = "11" else
      z;

z<="0001" when (a = "00" and (en='1' or en2='0)) else ...

```

2.2.2 *With ... select* naredba

```

architecture with_select of decoder is
begin
    with a select
        z<="0001" when "00" ,
          "0010" when "01" ,
          "0100" when "10" ,
          "1000" when "11" ,
          "XXXX" when others ;
end architecture with_select;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity seven_seg is
    port( a : in  std_ulogic_vector(3 downto 0);
          z : out std_ulogic_vector(6 downto 0));
end entity seven_seg;

architecture with_select of decoder is
begin
    with a select
        z<="1110111" when "0000" ,
          "0010010" when "0001" ,
          "1011101" when "0010" ,
          "1011011" when "0011" ,
          "0111010" when "0100" ,
          "1101011" when "0101" ,
          "1101111" when "0110" ,
          "1010010" when "0111" ,
          "1111111" when "1000" ,
          "1111011" when "1001" ,
          "1101101" when "1010"|"1011"|"1100"|"1101"|"1110"|"1111",
          "0000000" when others;
end architecture with_select;
-----
"1101101" when "1010" to "1111",

```

2.2.3 n u 2^n dekodler

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity decoder is
    generic( n:positive)
    port( a : in  std_ulogic_vector(n-1 downto 0);
          z : out std_ulogic_vector(2**n-1 downto 0));
end entity decoder;

constant z_out :bit_vector(2**n-1 downto 0):=(0=>'1',others=>'0');

sll, sla, rol, ror srl, sra

x<=unsigned(y)
y<=std_ulogic_vector(x);

-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;

entity decoder is
    generic( n:positive)
    port( a : in  std_ulogic_vector(n-1 downto 0);
          z : out std_ulogic_vector(2**n-1 downto 0));
end entity decoder;

```



```

architecture rotate of decoder is
constant z_out :bit_vector(2**n-1 downto 0):=(0=>'1',others=>'0');
begin
    z<=to_StdULogicVector(z_out sll to_integer(unsigned(a)));
end architecture rotate;
-----

```

2.3 4 u 1 multiplekser

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux is
    port( a,b,c,d : in std_ulogic;
          s: in std_ulogic_vector(1 downto 0);
          y: out std_ulogic);
end entity mux;

```

```

architecture with_select of mux is
begin
    with s select
        y<=a when "00",
            b when "01",
            c when "10",
            d when "11",
            'X' when others;
end architecture with_select;
-----

```

```

architecture when_else of mux is
begin
    y<=a when s = "00" else
        b when s = "01" else
        c when s = "10" else
        d when s = "11" else
        'X';
end architecture when_else;
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity mux is
    port( a,b,c,d : in std_ulogic;
          s: in std_ulogic_vector(1 downto 0);
          y: out std_ulogic);
end entity mux;

```

```

architecture three_state of mux is
begin
    y<= a when s = "00" else 'Z';
    y<= b when s = "01" else 'Z';
    y<= c when s = "10" else 'Z';
    y<= d when s = "11" else 'Z';

```

```
end architecture three_state;
```

2.4 Enkoder prioriteta

2.4.1 *Don't Cares*

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity priority is
    port( a : in  std_ulogic_vector(3 downto 0);
          y : out std_ulogic_vector(1 downto 0);
          valid: out std_ulogic);
end entity priority;

architecture dont_care of priority is
begin
    with a select
        y<="00" when "0001",
          "01" when "001-",
          "10" when "01--",
          "11" when "1---",
          "00" when others;
        valid<='1' when
            (a(0)='1' or a(1)='1' or a(2)='1' or a(3)='1') else '0';
end architecture dont_care;
```

```
architecture ordered of priority is
begin
    y<="00" when a(3)='1' else
      "01" when a(2)='1' else
      "10" when a(1)='1' else
      "11" when a(0)='1' else
      "00" ;
    valid<= '1' when
        (a(0)='1' or a(1)='1' or a(2)='1' or a(3)='1') else '0';
end architecture ordered;
```

```
-----
use numeric_std.all;
architecture match of priority is
begin
    y<="00" when std_match(a,"0001") else
      "01" when std_match(a,"001-") else
      "10" when std_match(a,"01--") else
      "11" when std_match(a,"1---") else
      "00" ;
    valid<= '1' when
        (a(0)='1' or a(1)='1' or a(2)='1' or a(3)='1') else '0';
end architecture match;
```

2.4.2 Sekvencijalni VHDL

```

architecture sequential of priority is
begin
  process(a) is
  begin
    if a(3)='1' then
      y<="11";
      valid<='1';
    elsif a(2)='1' then
      y<="10";
      valid<='1';
    elsif a(1)='1' then
      y<="01";
      valid<='1';
    elsif a(0)='1' then
      y<="00";
      valid<='1';
    else
      y<="00";
      valid<='0';
    end if;
  end process;
end architecture sequential;

```

```

-----

architecture sequential2 of priority is
begin
  process(a) is
  begin
    valid<='1';
    if a(3)='1' then
      y<="11";
    elsif a(2)='1' then
      y<="10";
    elsif a(1)='1' then
      y<="01";
    elsif a(0)='1' then
      y<="00";
    else
      y<="00";
      valid<='0';
    end if;
  end process;
end architecture sequential2;

```

2.5 Sabirači

```

library ieee;
use ieee.std_logic_1164.all;

entity FA1 is
  port (
    a: in STD_LOGIC; -- Inputs
    b: in STD_LOGIC;

```

```

        ci: in STD_LOGIC; -- Carry input
        co: out STD_LOGIC; -- Carry output
        z: out STD_LOGIC -- Sum
    );
end FA1;

architecture Concurrent of FA1 is
begin

    z <= a xor b xor ci;
    co <= (a and b) or (a and ci) or (b and ci);

end Concurrent;

-----

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity adder1 is
    generic(N:natural:=24); -- Adder width

    port( in1: in std_logic_vector(N-1 downto 0); -- Inputs
          in2: in std_logic_vector(N-1 downto 0);
          cin: in std_logic; -- Carry input
          sum: out std_logic_vector(N-1 downto 0) -- Sum
        );
end adder1;

architecture Structural of adder1 is
    component FA1 is
        port( a,b,ci:in std_logic;  co,z:out std_logic);
    end component;
    signal c : std_logic_vector(N-1 downto 0);
begin

    elements : for i in N-1 downto 0 generate
        LSB: if i = 0 generate
            fad16: FA1 port map(a=>in1(0),b=>in2(0),
ci=>cin,co=>c(0),z=>sum(0));
        end generate;
        MSBs: if i > 0 generate
            fad17: FA1 port map(a=>in1(i),b=>in2(i),
ci=>c(i-1),co=>c(i),z=>sum(i));
        end generate;
    end generate;

end Structural;

```

2.5 Parity Checker

Loop
While *condition* loop

```
For identifier in range loop

For I in 0 to n-1 loop

For I in a'range loop

-----

library ieee;
use ieee.std_logic_1164.all;

entity parity is
  port(a :in std_ulogic_vector;
        y:out std_ulogic);
end entity parity;

architecture iterative of parity is
begin
  process(a) is
    variable even:std_ulogic;
  begin
    even:='0';
    for I in a'range loop
      if a(i)='1' then even:=not even;
      end if;
    end loop;
    y<=even;
  end process;
end architecture iterative;

-----
```