

## Deo 3: Sekvencijalni blokovi

### SR lec

```
library ieee;
use ieee.std_logic_1164.all;

entity SR_latch1 is
  port(S,R :in std_ulogic;
        Q,Qbar:buffer std_ulogic);
end entity SR_latch1;

architecture dataflow of SR_latch1 is
begin
  Q<='1' when R='0' else
    '0' when S='0' else Q;
  Qbar<='1' when S='0' else
    '0' when R='0' else Qbar;
end architecture dataflow;

-----

library ieee;
use ieee.std_logic_1164.all;

entity SR_latch2 is
  port(S,R :in std_ulogic;
        Q,Qbar:out std_ulogic);
end entity SR_latch2;

architecture behavioural of SR_latch2 is
begin
  po:process (R,S) is
  begin
    case std_ulogic_vector(R,S) is
      when "00" =>
        Q<='1';
        Qbar<='1';

      when "01" =>
        Q<='1';
        Qbar<='0';

      when "10" =>
        Q<='0';
        Qbar<='1';

      when others =>
        null;
    end case;
  end process po;
end architecture behavioural;

-----

architecture dataflow of SR_latch2 is
begin
  Q<='1' when R='0' else
    '0' when S='0' else
      unaffected;
```

```

    Qbar<='1' when S='0' else
        '0' when R='0' else
            unaffected;
end architecture dataflow;

```

## D lec

```

library ieee;
use ieee.std_logic_1164.all;

entity D_latch is
    port( D,Enable :in std_ulogic;
          Q:out std_ulogic);
end entity D_latch;

architecture beh of D_latch is
begin
    po:process(D, Enable) is
    begin
        if (Enable='1') then
            Q<=D;
        end if;
    end process po;
end architecture beh;

```

-----

## D flipflop

```

library ieee;
use ieee.std_logic_1164.all;

entity D_FF is
    port( D,Clock :in std_ulogic;
          Q :out std_ulogic);
end entity D_FF;

architecture beh of D_FF is
begin
    po : process is
    begin
        wait until (Clock='1');
        Q<=D;
    end process po;
end architecture beh;

```

-----

```

architecture beh2 of D_FF is
begin
    po : process(Clock) is
    begin
        if (Clock='1') then
            Q<=D;
        end if;
    end process po;
end architecture beh2;

```

```

    end process po;
end architecture beh2;

architecture beh3 of D_FF is
begin
    po : process is
    begin
        if (Clock='1') then
            Q<=D;
        end if;
        wait on Clock;
    end process po;
end architecture beh3;

architecture neg_egde of D_FF is
begin
    po : process is
    begin
        wait until (Clock='0');
        Q<=D;
    end process po;
end architecture neg_edge;

```

## **Asinhroni set i reset**

```

library ieee;
use ieee.std_logic_1164.all;

entity D_FF_R is
    port( D,Clock,Reset :in std_ulogic;
          Q :out std_ulogic);
end entity D_FF_R;

architecture beh of D_FF_R is
begin
    po : process(Clock,Reset) is
    begin
        if (Reset='0') then
            Q<='0';
        elsif (Clock='1' and Clock'event) then
            Q<=D;
        end if;
    end process po;
end architecture beh;

library ieee;
use ieee.std_logic_1164.all;

entity D_FF_RS is
    port( D,Clock,Reset,Set :in std_ulogic;
          Q :out std_ulogic);
end entity D_FF_RS;

architecture beh of D_FF_RS is
begin
    po : process(Clock,Reset,Set) is
    begin
        if (Set='0') then

```

```

        Q<='1';
    elsif (Reset='0') then
        Q<='0';
    elsif (Clock='1' and Clock'event) then
        Q<=D;
    end if;
end process po;
end architecture beh;

```

## **Rising\_edge I Falling\_edge**

```

architecture true_edge of D_FF_R is
begin
    po : process(Clock,Reset) is
    begin
        if (Reset='0') then
            Q<='0';
        elsif (Clock='1' and Clock'last_value='0' and Clock'event) then
            Q<=D;
        end if;
    end process po;
end architecture true_edge;

```

```

architecture r_edge of D_FF_R is
begin
    po : process(Clock,Reset) is
    begin
        if (Reset='0') then
            Q<='0';
        elsif rising_edge(Clock) then
            Q<=D;
        end if;
    end process po;
end architecture r_edge;

```

## **Sinhroni set i reset I clock enable**

```

architecture syn_reset of D_FF_R is
begin
    po : process(Clock) is
    begin
        if rising_edge(Clock) then
            if (Reset='0') then
                Q<='0';
            else
                Q<=D;
            end if;
        end if;
    end process po;
end architecture syn_reset;

```

```

library ieee;
use ieee.std_logic_1164.all;

```

```

entity D_FF_E is
  port( D,Clock,Enable :in std_ulogic;
        Q :out std_ulogic);
end entity D_FF_E;

```

```

architecture beh of D_FF_E is
begin
  po : process(Clock) is
  begin
    if Rising_edge(Clock) then
      if (Enable='1') then
        Q<=D;
      end if;
    end if;
  end process po;
end architecture beh;

```

```

architecture gated_clock of D_FF_E is
signal ce : std_ulogic;
begin
  ce<=Enable and Clock;
  po : process(ce) is
  begin
    if Rising_edge(ce) then
      Q<=D;
    end if;
  end process po;
end architecture beh;

```

## **Vremenske I logicke provere**

```

Assert condition
Report message
Severity level

```

```

Assert (Set='1' or Reset='1')
Report "Set and reset are both asserted"
Severity warning;

```

```

Assert (not(Set='0' and Reset='0'))

```

```

Assert (not(Clk='1' and D'event and not Clk'stable(3 ns)))
Report "Hold time violation"
Severity warning;

```

-----

```

library ieee;
use ieee.std_logic_1164.all;

entity D_FF is
  generic(CQ_Delay,SQ_delay,RQ_delay:time:=5 ns;
          Setup:time:=3ns );
  port( D,Clock,Reset,Set,Enable :in std_ulogic;
        Q :out std_ulogic);
Begin
  Assert(not(rising_edge(Clock) and not D'stable(Setup)))
  Report "Setup time violation"
  Severity warning;
end entity D_FF;

architecture beh of D_FF is
begin
  po : process(Clock,Reset,Set) is
  begin
    assert (not(Set='0' and Reset='0'))
    report "Set and Reset are both asserted"
    severity error;
    if (Set='0') then
      Q<='1' after SQ_delay;
    elsif (Reset='0') then
      Q<='0'after RQ_delay;
    elsif rising_edge(Clock) then
      if Enable='1' then
        Q<=D after CQ_delay;
      end if;
    end if;
  end process po;
end architecture beh;

```

## **JK I T flipflopovi**

```

library ieee;
use ieee.std_logic_1164.all;
entity D_FF_R is
  port( D,Clock,Reset :in std_ulogic;
        Q :out std_ulogic);
end entity D_FF_R;

architecture sig of D_FF_R is
  signal state:std_ulogic;
begin
  po : process(Clock,Reset) is
  begin
    if (Reset='0') then
      state<='0';
    elsif (Clock='1' and Clock'event) then
      state<=D;
    end if;
  end process po;
  Q<=state;
  Qbar<= not state;
end architecture sig;

```

```

architecture var of D_FF_R is
begin
  po : process(Clock,Reset) is
    variable state : std_ulogic;
  begin
    if (Reset='0') then
      state:='0';
    elsif (Clock='1' and Clock'event) then
      state:=D;
    end if;
  end process po;
  Q<=state;
  Qbar<= not state;
end architecture var;

```

```

-----
library ieee;
use ieee.std_logic_1164.all;

```

```

entity JK_FF is
  port( J,K,Clock,Reset :in std_ulogic;
        Q :out std_ulogic);
end entity D_FF_R;

```

```

architecture sig of JK_FF is
  signal state:std_ulogic;
begin
  po : process(Clock,Reset) is
  begin
    if (Reset='0') then
      state<='0';
    elsif rising_edge(Clock) then
      case std_ulogic_vector(J,K) is
        when "11" => state<=not state;
        when "10" => state<='1';
        when "01" => state<='0';
        when others => null;
      end case;
    end if;

    end process po;
  Q<=state;
  Qbar<= not state;
end architecture sig;

```

```

architecture var of T_FF is
begin
  po : process(Clock,Reset) is
    variable state : std_ulogic;
  begin
    if (Reset='0') then
      state:='0';
    elsif (Clock='1' and Clock'event) then
      if T='1' then
        state:=not state;
      end if;
    end if;
  end process po;
  Q<=state;
  Qbar<= not state;

```

```
end architecture var;
```

## **Registri i SHIFT registri**

```
--Registar sa n bitova
library ieee;
use ieee.std_logic_1164.all;

entity reg is
  generic(n:natural:=4);
  port(   D: in std_logic_vector(n-1 downto 0);
         Clock,Reset : in std_logic;
         Q : out std_logic_vector(n-1 downto 0));
end entity reg;

architecture beh of reg is
begin
  po : process(Clock,Reset) is
  begin
    if (Reset='0') then
      Q<=(others=>'0');
    elsif rising_edge(Clock) then
      Q<=D;
    end if;
  end process po;
end architecture beh;

-- shift registrar
library ieee;
use ieee.std_logic_1164.all;

entity sipo is
  generic(n:natural:=8);
  port(   A,Clock : in std_logic;
         Q : out std_logic_vector(n-1 downto 0));
end entity sipo;

architecture beh of sipo is
begin
  po : process(Clock) is
  variable reg: std_logic_vector(n-1 downto 0);
  begin
    if rising_edge(Clock) then
      reg:=reg(n-2 downto 0)&A;
    end if;
    Q<=reg;
  end process po;
end architecture beh;
```

```

-- Sinhroni binarni brojac

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity counter is
    generic(n:natural:=4);
    port(   Reset,Clock : in std_logic;
          Q : out std_logic_vector(n-1 downto 0));
end entity counter;

architecture beh of counter is
begin
    po : process(Clock,Reset) is
        variable cnt: std_logic_vector(n-1 downto 0));
    begin
        if Reset='1' then
            cnt:=(others=>'0');
        elsif rising_edge(Clock) then
            cnt:=cnt+1;
        end if;
        Q<=cnt;
    end process po;
end architecture beh;

-- Opis asinhronog brojaca kao niza T flip flopova

architecture ripple of counter is
    component T_FF is
        port(   T,Clock,Reset:in std_logic;
              Q, Qbar :out std_logic);
    end component;

    signal carry:std_logic_vector(n downto 0);

begin
    carry(0)<=Clock;
    g0: for i in 0 to n-1 generate
        ti: T_FF port map ('1',carry(i),reset,count(i),carry(i+1));
    end generate g0;
end architecture ripple;

-- Opis T flip flopa sa kasnjenjem

architecture delayed of T_FF is
begin
    po : process(Clock,Reset) is
        variable state : std_ulogic;
    begin
        if (Reset='0') then
            state:='0';
        elsif (Clock='1' and Clock'event) then
            if T='1' then
                state:=not state;
            end if;
        end if;
    end process po;
end architecture delayed;

```

```

        end if;
    end if;
    end process po;
    Q <= state after 5ns;
    Qbar<= not state after 5ns;
end architecture var;

```

## ROM memorija

```

library ieee;
use ieee.std_logic_1164.all;

entity rom16x7 is
    port(    address : in range 0 to 15;
           data : out std_logic_vector(6 downto 0));
end entity rom16x7;

architecture beh of rom16x7 is
    type rom_array is array(0 to 15) of std_logic_vector(6 downto 0);
    constant rom: rom_array:= (
        "1110111" ,
        "0010010",
        "1011101",
        "1011011",
        "0111010",
        "1101011",
        "1101111",
        "1010010",
        "1111111",
        "1111011",
        "1101101",
        "1101101",
        "1101101",
        "1101101",
        "1101101",
        "1101101",
        "1101101",
        "1101101");
begin
    data<=rom(address);
end architecture beh;

```

## staticka RAM memorija

```

library ieee;
use ieee.std_logic_1164.all;

entity RAM16x8 is
    port(address : in range 0 to 15;
         data : inout std_logic_vector(7 downto 0);
         cs,we,oe : in std_logic );
end entity RAM16x8;

architecture beh of RAM16x8 is
begin
    po : process(address,cs,we,oe) is
        type ram_array is array(0 to 15) of std_logic_vector(7 downto 0);
        variable mem: ram_array;

```

```

begin

data<=(others=>'Z');
if cs='0' then
  if oe='0' then
    Data<=mem(address);
  elsif we='0' then
    mem(address):=data;
  end if;
end if;
end process po;

end architecture beh;

```

## Opisivanje SEKVENCERA

```

library ieee;
use ieee.std_logic_1164.all;
entity traffic is
  port( clock,timed,car: in std_logic;
        start_timer,minor_green,major_green : out std_logic));
end entity traffic;

architecture asml of traffic is
  type state_type is (G,R);
  signal present_state,next_state: state_type;
begin
  proc1: process(clock) is
  begin
    if rising_edge(clock) then
      present_state<=next_state;
    end if;
  end process proc1;

  proc2: process(car,timed,present_state) is
  begin
    start_timer<='0';
    case present_state is
      when G =>
        major_green<='1';
        minor_green<='0';
        if (car='1') then
          start_timer<='1';
          next_state<=R;
        else
          next_state<=G;
        end if;
      when R=>
        major_green<='0';
        minor_green<='1';
        if (timed='1') then
          next_state<=G;
        else
          next_state<=R;
        end if;
    end case;
  end process proc2;

```

```

end architecture asm1;

architecture asm2 of traffic is
  type state_type is (G,R);
  signal present_state,next_state: state_type;
begin
  proc1: process(clock) is
  begin
    if rising_edge(clock) then
      present_state<=next_state;
    end if;
  end process proc1;

  proc2: process(car,timed,present_state) is
  begin
    case present_state is
      when G =>
        if (car='1') then
          next_state<=R;
        else
          next_state<=G;
        end if;
      when R=>
        if (timed='1') then
          next_state<=G;
        else
          next_state<=R;
        end if;
    end case;
  end process proc2;

  proc3: process(car, present_state) is
  begin
    start_timer<='0';
    if (present_state=G) then
      major_green<='1';
      minor_green<='0';
      if (car='1') then
        start_timer<='1';
      end if;
    else
      major_green<='0';
      minor_green<='1';
    end if;
  end process proc3;

end architecture asm2;

```