 


Timing in Asynchronous Circuits



What do we mean by clock?

- The system clock for an integrated circuit is a voltage signal that pulses at a regular frequency.



- The clock tells each stage of a circuit that the inputs of that stage are valid and can be processed.

Current PC Technology

- One of the defining performance characteristics of current personal computers is the clock speed of the microprocessor.
- Current home PC microprocessors approach **3 GHz**.
- The Pentium 4 chip has an area of around 217 mm², or around 15 mm from edge to edge.
- A clock signal must travel the 15 mm distance in less than .333 nanoseconds = **100 million miles/ hour**.

What does this mean?


- As clock speeds increase, it becomes more difficult to get the clock signal to propagate to all parts of the chip fast enough for the circuit to operate properly.
- There is some upper limit to clock speed that depends on the material properties of the device.

Another Option:

- Eliminate the global clock.
- Use handshaking between the stages to handle data transfer.
- A circuit that does not utilize a synchronized clock is called an **ASYNCHRONOUS** circuit.



Synchronous Logic Comparison

 - Only active circuits run
- Entire chip runs




Synchronous Logic Comparison

  - Worst case timing
 - Clock forces short functions to take same amount of time as long functions
- Best case timing: each module runs as fast as it can




Synchronous circuit

 


Implicit (global) synchronization between blocks
 Clock period $>$ Max Delay (CL + R)

Asynchronous circuit

 

Explicit (local) synchronization:
 Req / Ack handshakes

Globally Async Locally Sync (GALS)

 

Clock disadvantages:

- Clock trees take up large amounts of space on die
- They consume large amounts of power
- Introduce noise
- Introduce delays
- Clock skew displaces useful work

$$T_{\text{synch}} = T_{\text{logic}} + T_{\text{skew}} + T_{\text{flip-flop}}$$

$$T_{\text{asynch}} = T_{\text{logic}} + T_{\text{hand-shake}}$$

Clock disadvantages ctnd.:

- Can take up to 40% power of consumption, 10% of chip area, and up to 50% of the performance
- Feature sizes decreasing, local clock speeds increasing
- Interconnects not keeping pace with transistor speed:
 - Past: Transistors limit speed
 - Future: Wires limit speed
- Clock skew tends to be proportional to interconnect delay

Benefits of Asynchronous Circuits

- High Speed -- Each stage can process as fast as possible, independent of a global clock.
- Low Power -- When system is idle, there is no clock driving the circuit.
- Modularity -- One design can easily be integrated into another design, without regard to how fast each section works.
- Design Time -- Less of the design time is spent making sure the timing assumptions of the circuit work at the given clock speed.


Disadvantages of Asynchronous Circuits

- Handshaking control can increase the overall circuit area.
- More difficult to design:
 - Most circuit designers learn only synchronous design.
 - Most CAD tools only support synchronous design.
 - Asynchronous circuit CAD tools still in early development.

Uses of Asynchronous Circuits


- Custom-designed circuits for high speed calculations.
- Modular designs that can be quickly changed for different applications.
- Low power uses, such as mobile phones and pagers.

Synchronous communication

 


- Clock edges determine the time instants where data must be sampled
- Data wires may glitch between clock edges (set-up/hold times must be satisfied)
- Data are transmitted at a fixed rate (clock frequency)

Dual rail

 


- Two wires with L(low) and H (high) per bit
 - “LL” = “spacer”, “LH” = “0”, “HL” = “1”
- n -bit data communication requires $2n$ wires
- Each bit is *self-timed*
- Other *delay-insensitive* codes exist (e.g. k-of-n) and event-based signalling (choice criteria: pin and power efficiency)

Bundled data

 


- Validity signal
 - Similar to an aperiodic local clock
- n -bit data communication requires $n+1$ wires
- Data wires may glitch when no valid
- Signaling protocols
 - level sensitive (latch)
 - transition sensitive (register): 2-phase / 4-phase

Example: memory read cycle

 

- Transition signaling, 4-phase


Asynchronous modules

 


- **Signaling protocol:**

reqin+ start+ [computation] done+ reqout+ ackout+ ackin+
 reqin- start- [reset] done- reqout- ackout- ackin-
 (more concurrency is also possible)


Elements for Asynchronous Design

 

Micropipelines (Sutherland 89)

 

Data-path / Control

 


Handshake Communication


- Most common control protocol is the Request/Acknowledge protocol
- The sender issues a Request to the receiver before sending the data. The receiver replies by sending an Acknowledge to the sender. Then the sender sends the data.
- If the sender initiates the data transfer, the transfer channel is a *push-channel*. On the other hand if the receiver initiates the transfer, the channel is a *pull-channel*.

Bundled data
(push) channel

(a)

 


Synchronous v. Asynchronous

 


How Handshaking Works




How Handshaking Works

 

How Handshaking Works

 


How Handshaking Works

 

Handshake Protocols

 
- Two Phase
 - The sender sends data and produces a Req event
 - The receiver absorbs data and produces an Ack event
 - Edge sensitive



Handshake Protocols

Four Phase

 - The sender issues data and sets Req to high
- The receiver absorbs the data and sets Ack to high
- The sender responds by setting Req to low
- The receiver acknowledges by setting Ack to low
- Level sensitive



Conclusion

- Asynchronous design provides delay-independent circuits.
- Synthesis from STGs can be fully automated.
- Great reduction in power
- No affect in functionality



