
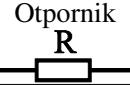
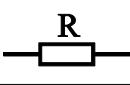
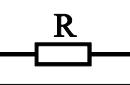
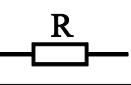
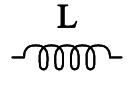
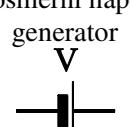
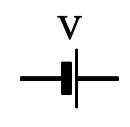
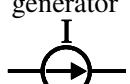
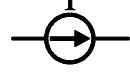
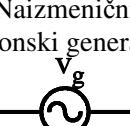
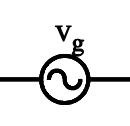
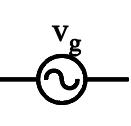
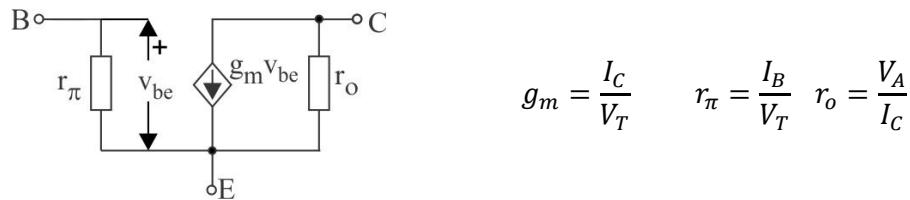


ANALIZA POJAČAVAČA SA BIPOLARNIM TRANZISTORIMA

Element	Jednosmerni model (DC)	Naizmenični model (AC)	
		Opšti slučaj	Srednje frekvencije
Otpornik 			
Kondenzator 	—○—		$\omega C \rightarrow \infty$ —○—
Kalem 	—○—○—		$\omega L \rightarrow \infty$ —○—○—
Jednosmerni naponski generator 		—○—	—○—○—
Jednosmerni strujni generator 		—○—	—○—○—
Naizmenični naponski generator 	—○—○—		

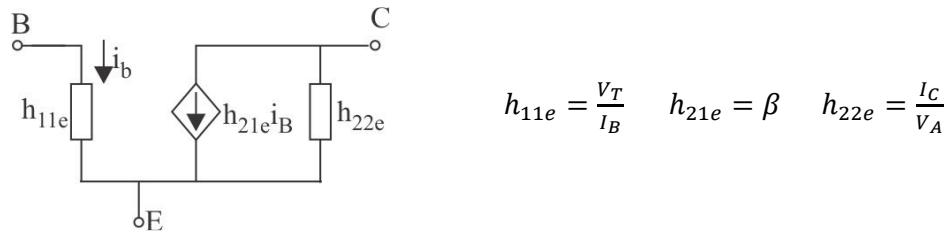


Veza između „h“ parametara i parametara pi modela:

$$r_\pi = h_{11E} \quad g_m = \frac{h_{21E}}{h_{11E}} \quad r_o = \frac{1}{h_{22E}}$$

1. ZADATAK

Na slici je prikazan pojačavač u spoju sa zajedničkim kolektorom. Poznati su parametri tranzistora: $V_{BE}=0,6$ V; $h_{12E} = 0$; $\beta=h_{21E} = 80$; $h_{22E} = 0$ S. Elementi kola: $R_p = R_E = 6$ k Ω ; $R_g = 600$ Ω ; $C_1 = C_2 \rightarrow \infty$; $R_B = 335$ k Ω ; $V_{CC}=12$ V. Smatrati da je $R_B >> R_g$. Odrediti:

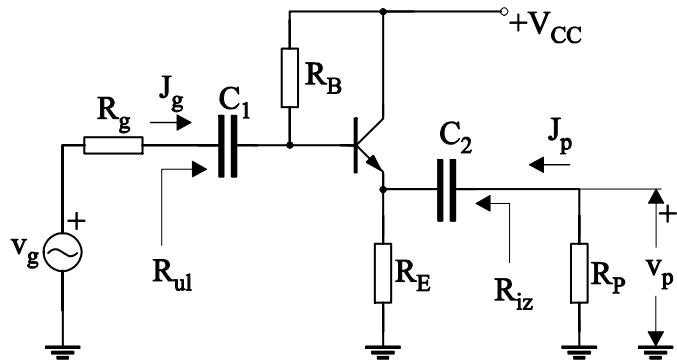- a) Dinamičke parametre tranzistora;
- b) Ulaznu otpornost pojačvača R_{ul} ;
- c) Izlaznu otpornost pojačavača R_{iz} ;
- d) Naponsko pojačanje $A = v_p/v_g$.



Rešenje:

a)

$$-R_E \cdot I_B \cdot (1 + \beta) - V_{BE} - R_B \cdot I_B + V_{CC} = 0$$


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) \cdot R_E} = 14 \mu A$$

$$h_{ie} = h_{11e} = \frac{V_T}{I_B} = \frac{26mV}{14\mu A} = 1,85 k\Omega$$

$$h_{fe} = h_{21e} = \beta = 80$$

b)

Šema za naizmeničnu struju

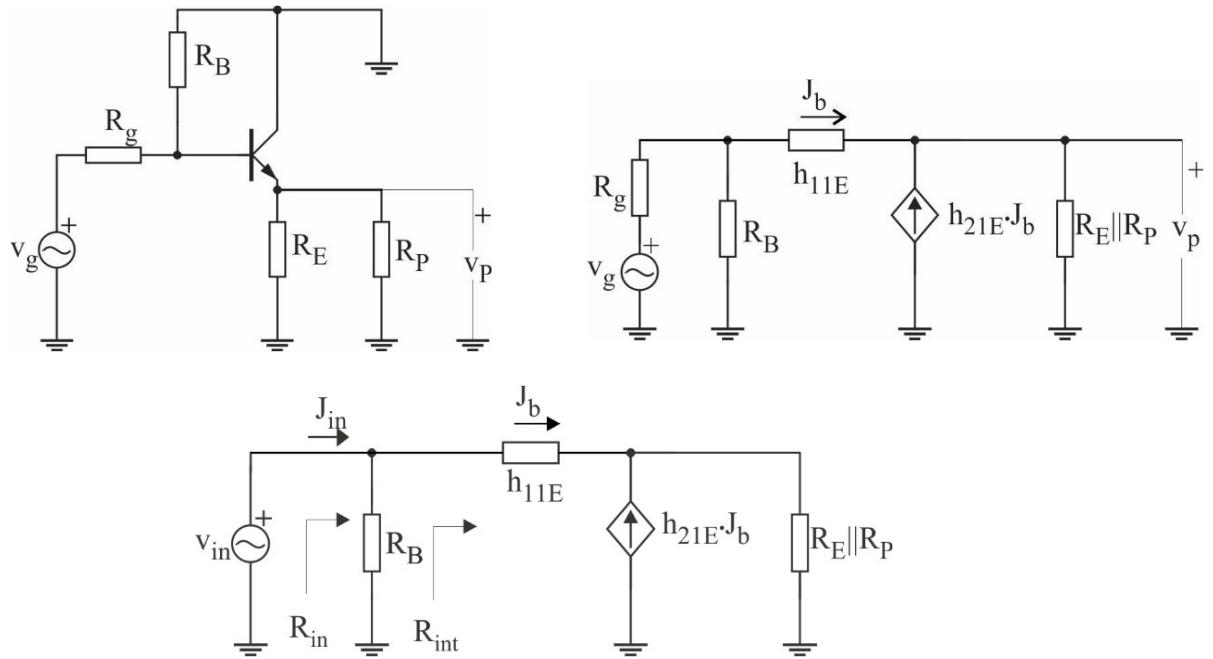

$$R_E \parallel R_P = R_{EC}$$

$$(B) \quad \frac{v_{in}}{R_B} + i_b - i_{in} = 0$$

$$(E) \quad -i_b - h_{21E} \cdot i_b + \frac{v_e}{R_{EC}} = 0$$

$$i_b = \frac{v_{in} - v_e}{h_{11e}}$$

$$(E) \quad v_e = R_{EC} \cdot i_b \cdot (1 + h_{21e})$$

$$i_b = \frac{v_{in} - R_{EC} \cdot J_b \cdot (1 + h_{21e})}{h_{11e}}$$

$$i_b = \frac{v_{in}}{h_{11e} + R_{EC} \cdot (1 + h_{21e})}$$

$$R_{int} = \frac{v_{in}}{i_b} = h_{11e} + R_{EC} \cdot (1 + h_{21e}) = 244,8 \text{ k}\Omega$$

$$(B) \quad i_{in} = \frac{v_{in}}{R_B} + \frac{v_{in}}{h_{11e} + R_{EC} \cdot (1 + h_{21e})}$$

$$\frac{1}{R_{in}} = \frac{i_{in}}{v_{in}} = \frac{1}{R_B} + \frac{1}{h_{11e} + R_{EC} \cdot (1 + h_{21e})}$$


$$R_{in} = 133,8 \text{ k}\Omega$$

Ulagna otpornost može da izrazi i na sledeći način:

$$\frac{1}{R_{in}} = \frac{1}{R_B} + \frac{1}{R_{int}}$$

$$R_{in} = R_B \parallel R_{int}$$

c)

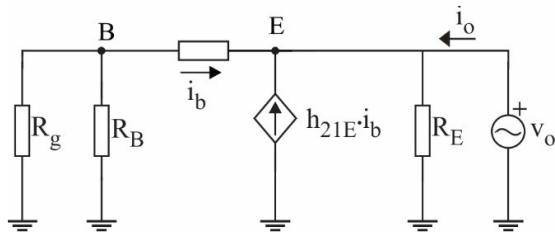

$$R_B \parallel R_g = R_{BC}$$

$$(B) \quad \frac{v_b}{R_{BC}} + i_b = 0$$

$$(E) \quad -i_o - h_{21E} \cdot i_b - i_b + \frac{v_o}{R_E} = 0$$

$$i_b = \frac{v_b - v_o}{h_{11e}}$$

$$(B) \quad v_b = -i_b \cdot R_{BC}$$

$$i_b = \frac{-i_b \cdot R_{BC} - v_o}{h_{11e}}$$

$$i_b = -\frac{v_o}{h_{11e} + R_{BC}}$$

(E)

$$i_o = -(h_{21E} + 1) \cdot i_b + \frac{v_o}{R_E} = (h_{21E} + 1) \cdot \frac{v_o}{h_{11e} + R_{BC}} + \frac{v_o}{R_E}$$


$$\frac{1}{R_o} = \frac{i_o}{v_o} = \frac{1 + h_{21e}}{h_{11e} + R_{BC}} + \frac{1}{R_E}$$

$$R_o = 30 \Omega$$

$$R_o = R_E \parallel R_{ot} \approx R_{ot} = \frac{h_{11e} + R_{BC}}{1 + h_{21e}}$$

d)

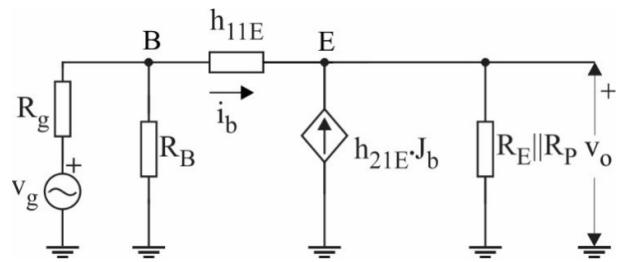I način primenom metoda potencijala čvorova



$$R_E \parallel R_P = R_{EC}$$

$$(B) \quad \frac{v_b}{R_B} + i_b + \frac{v_b - v_g}{R_g} = 0$$

$$(E) \quad -i_b - h_{21E} \cdot i_b + \frac{v_o}{R_{EC}} = 0$$

$$i_b = \frac{v_b - v_o}{h_{11e}}$$

$$(B) \quad v_b = v_g \cdot \frac{R_B}{R_g + R_B} - i_b \cdot \frac{R_B \cdot R_g}{R_g + R_B}$$

$$(E) \quad v_o = R_{EC} \cdot i_b \cdot (1 + h_{21e})$$

$$v_b = h_{11e} \cdot i_b + v_o$$

$$i_b = v_g \cdot \frac{\frac{R_B}{R_B + R_g}}{h_{11E} + \frac{R_B \cdot R_g}{R_g + R_B} + (1 + h_{21E}) \cdot R_{EC}}$$



Zamenom izraza za struju baze u (E) dobija se:

$$A_n = \frac{v_o}{v_g} = \frac{R_{EC} \cdot (1 + h_{21e}) \cdot \frac{R_B}{R_B + R_g}}{h_{11E} + \frac{R_B \cdot R_g}{R_g + R_B} + (1 + h_{21E}) \cdot R_{EC}}$$

$$A_n = 0,99$$

II načine

Primenom teoreme o kompoenzaciji.

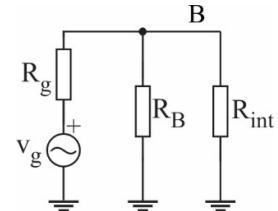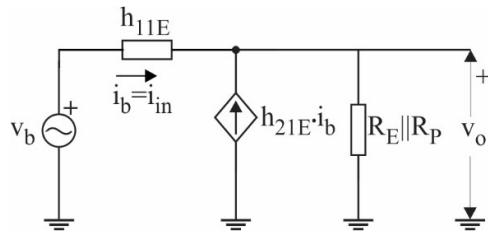

$$R_E \parallel R_P = R_{EC}$$

$$(E) \quad -i_b - h_{21E} \cdot i_b + \frac{v_o}{R_{EC}} = 0$$

$$i_b = \frac{v_b - v_o}{h_{11e}} = \frac{v_b}{R_{int}}$$

$$v_o = (1 + h_{21e}) \cdot R_{EC} \cdot \frac{v_b}{R_{in}}$$

$$\frac{v_o}{v_b} = \frac{(1 + h_{21e}) \cdot R_{EC}}{R_{int}}$$

$$\frac{v_b}{v_g} = \frac{R_B \parallel R_{int}}{R_g + R_B \parallel R_{int}} = \frac{R_{in}}{R_g + R_{in}}$$

$$A_n = \frac{v_o}{v_g} = \frac{v_o}{v_b} \cdot \frac{v_b}{v_g} = \frac{(1 + h_{21e}) \cdot R_{EC}}{R_{int}} \cdot \frac{R_{in}}{R_g + R_{in}}$$


2. ZADATAK

Kolo na slici predstavlja jednostepeni pojačavač sa bipolarnim tranzistorom. Parametri tranzistora su: $V_{BE}=0,6$ V; $h_{12E}=0$; $h_{21E}=\beta=50$; $h_{22E}=0$ S. Elementi kola su: $R_p=R_C=5\text{ k}\Omega$; $R_g=1\text{ k}\Omega$; $R_1=500\text{ k}\Omega$; $R_E=200\Omega$; $V_{CC}=12$ V; $C_1 \rightarrow \infty$; $C_2 \rightarrow \infty$.

Odrediti:

a) ulaznu otpornost pojačvača R_{in} ;

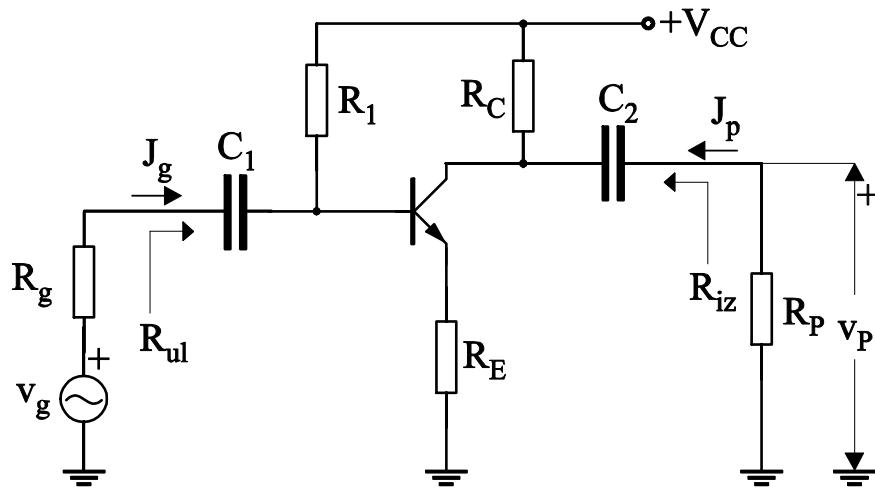b) naponsko pojačanje $A = \frac{v_p}{v_g}$.



Rešenje:



$$V_{CC} - R_1 \cdot I_B - V_{BE} - R_E \cdot (1 + \beta) \cdot I_B = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_1 + R_E \cdot (1 + \beta)} = 20 \mu A$$


$$h_{11E} = r_\pi = \frac{V_T}{I_B} = \frac{26 \text{ mV}}{20 \mu A} = 1,3 \text{ k}\Omega$$

$$h_{21E} = \beta$$
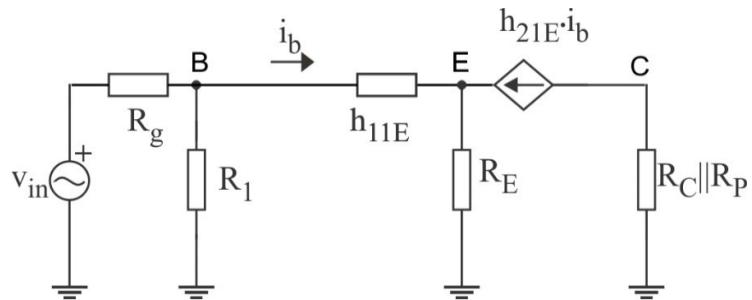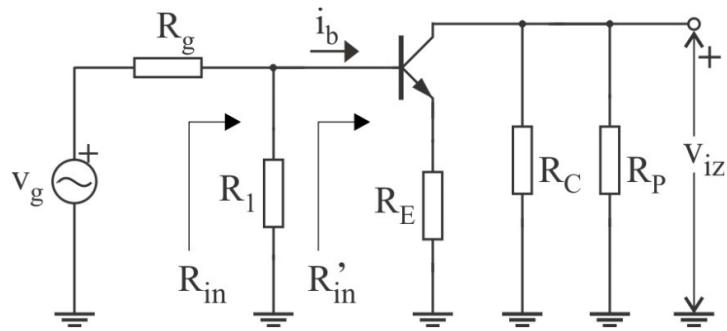
$$g_m = \frac{h_{21E}}{r_\pi} = \frac{I_C}{V_T} = 38,5 \text{ mS}$$



a)

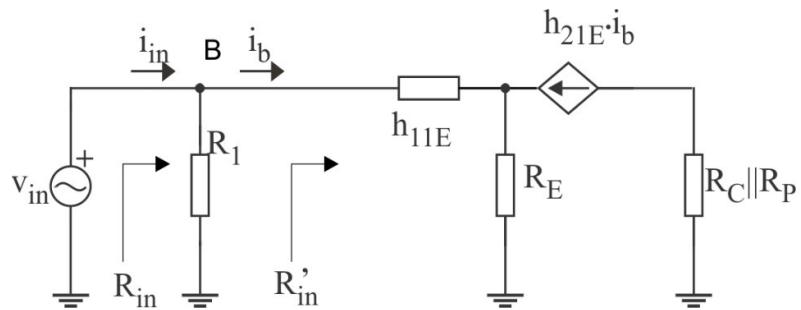

$$(E) \quad \frac{v_e}{R_E} - i_b - h_{21E} \cdot i_b = 0$$

$$i_b = \frac{v_{in} - v_e}{h_{11E}}$$


$$(E) \quad v_e = R_E \cdot i_b \cdot (1 + h_{21E})$$

$$i_b = \frac{v_{in}}{h_{11E} + R_E \cdot (1 + h_{21E})}$$

$$R'_{in} = \frac{v_{in}}{i_b} = h_{11E} + R_E \cdot (1 + h_{21E}) = 11,5 \text{ k}\Omega$$

$$R_{in} = R'_{in} \parallel R_1 = 11,24 \text{ k}\Omega$$

b)

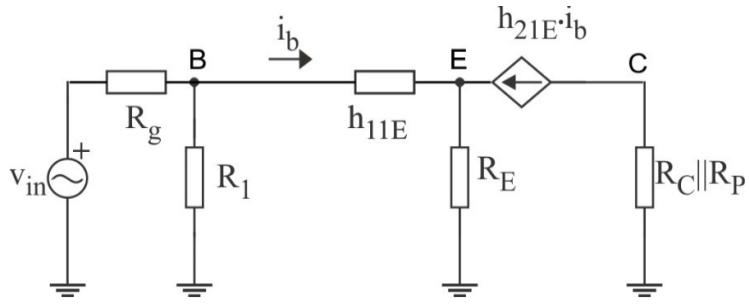

$$(E) \quad \frac{v_e}{R_E} - i_b - h_{21E} \cdot i_b = 0$$

$$(B) \quad \frac{v_b}{R_1} + \frac{v_b - v_g}{R_g} + i_b = 0$$

$$(C) \quad \frac{v_c}{R_C \parallel R_P} - h_{21E} \cdot i_b = 0$$

$$i_b = \frac{v_b - v_e}{h_{11E}}$$

$$(E) \quad v_e = R_E \cdot i_b \cdot (1 + h_{21E})$$

$$(B) \quad v_b = v_g \cdot \frac{R_1}{R_1 + R_g} - i_b \cdot \frac{R_1 \cdot R_g}{R_1 + R_g}$$



$$i_b = \frac{v_g \cdot \frac{R_1}{R_1 + R_g}}{R_E \cdot (1 + h_{21E}) + \frac{R_1 \cdot R_g}{R_1 + R_g} + h_{11E}}$$

$$v_p = v_c = -h_{21E} \cdot i_b \cdot R_C \parallel R_P$$

$$A_n = \frac{v_c}{v_p} = -\frac{h_{21E} \cdot R_C \parallel R_P \cdot \frac{R_1}{R_1 + R_g}}{R_E \cdot (1 + h_{21E}) + \frac{R_1 \cdot R_g}{R_1 + R_g} + h_{11E}} = 10$$

II način za određivanje naponskog pojačanja

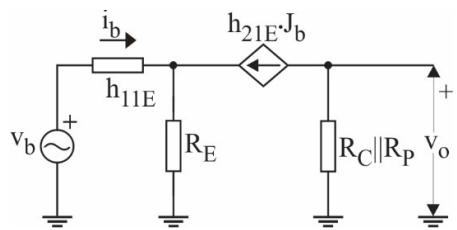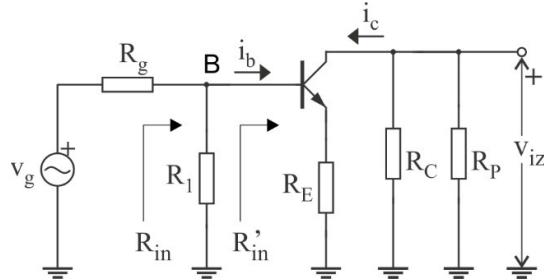
Primenom teoreme o kompenzaciji i korišćenjem ulazne otpornosti



$$i_b = \frac{v_b}{R'_{in}}$$

$$v_o = -h_{21E} \cdot i_b \cdot R_C \parallel R_P = -h_{21E} \cdot \frac{v_b}{R'_{in}} \cdot R_C \parallel R_P$$
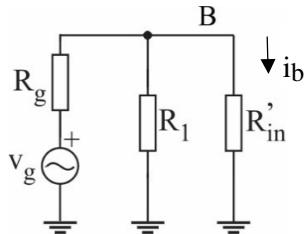
$$\frac{v_o}{v_b} = -h_{21E} \cdot \frac{R_C \parallel R_P}{R'_{in}}$$




$$\frac{v_b}{v_g} = \frac{R_{in}}{R_g + R_{in}}$$

$$A_n = \frac{v_o}{v_g} = \frac{v_o}{v_b} \cdot \frac{v_b}{v_g} = -h_{21E} \cdot (R_C \parallel R_P) \cdot \frac{R_{in}}{R_{in} + R_g} \cdot \frac{1}{R'_{in}}$$

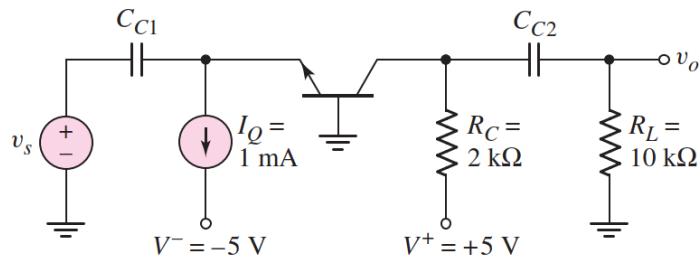3. ZADATAK

Na slici je prikazan pojačavač u sprezi sa zajedničkom bazom. Ukolik je: $\beta=80$, $V_{BE}=0,7 \text{ V}$, $V_A = 100 \text{ V}$ odrediti:

- Radnu tačku tranzistora;
- Parametre naizmeničnom režima rada;
- Naponsko pojačanje $A = \frac{v_o}{v_s}$
- Iznaznu otpornost R_o



Rešenje:

a)

$$V_E = -V_{BE} = -0,7 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{1 + \beta}$$

$$I_E = I_Q = 1 \text{ mA}$$

$$I_C + \frac{V_C - V_{CC}}{R_C} = 0$$

$$I_C = I_Q \frac{\beta}{\beta + 1} = 0,98 \text{ V}$$

$$V_C = V_{CC} - R_C \cdot I_C = 3,02 \text{ V}$$



$$V_{CE} = V_C + V_{BE} = 3,72 \text{ V}$$

b)

$$r_\pi = h_{11E} = \frac{V_T}{I_B} = \frac{26 \text{ mV}}{12,3 \mu\text{V}} = 2,1 \text{ k}\Omega$$

$$g_m = \frac{I_C}{V_T} = \frac{0,98 \text{ mA}}{26 \text{ mV}} = 37,7 \text{ mS}$$
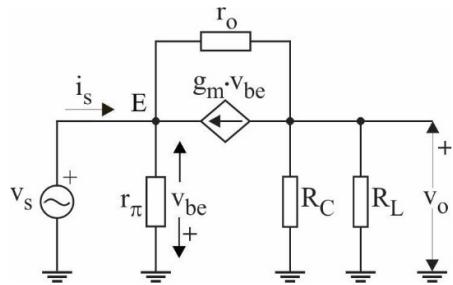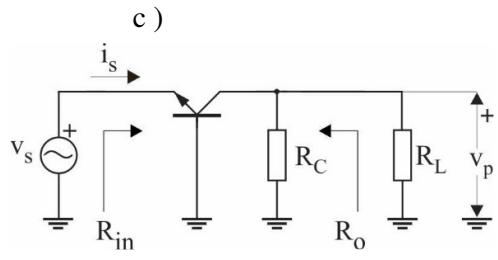
$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{0,98 \text{ mA}} = 102 \text{ k}\Omega$$



$$R_{CB} = R_C \parallel R_L = 1,66 \text{ k}\Omega$$


$$\frac{v_o}{R_{CB}} + \frac{v_o - v_s}{r_o} + g_m \cdot v_{be} = 0$$

$$v_{be} = -v_s$$

$$\underline{v_o = \frac{g_m + \frac{1}{r_o}}{\frac{1}{R_{CB}} + \frac{1}{r_o}} \cdot v_s}$$

$$A_n = \frac{v_o}{v_s} = \frac{g_m \cdot R_{CB} \cdot r_o + R_{CB}}{R_{CB} + r_o} = 61,6$$

d)

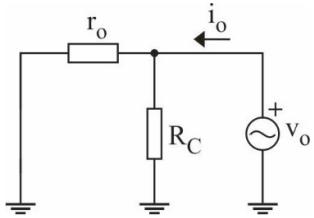


$$\frac{v_o}{r_o} + \frac{v_o}{R_C} - i_o = 0$$

$$R_o = \frac{v_o}{i_o} = \frac{R_C \cdot r_o}{R_C + r_o} \approx R_C = 2 \text{ k}\Omega$$

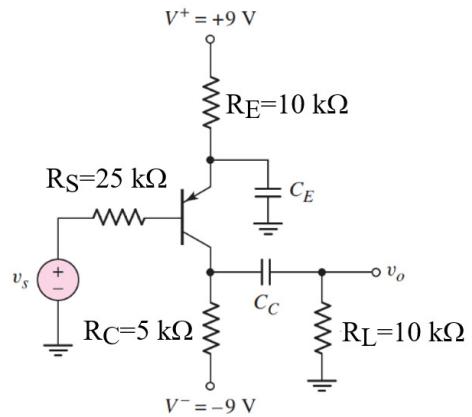4. ZADATAK

Tranzistor u kolu sa slike ima koeficijent strujnog pojačanja $\beta=80$, $V_{BE} = -0,65 V$, $V_A \nearrow \infty$. Odrediti naponsko pojačanje pojačavača $A = \frac{v_o}{v_s}$.




Rešenje:

$$-I_B \cdot R_S + V_{BE} - R_E \cdot I_E + V_{CC} = 0$$

$$I_B = \frac{V_{CC} + V_{BE}}{R_S + (1 + \beta) \cdot R_E} = \frac{8,35 V}{835 k\Omega} = 10 \mu A$$

$$r_\pi = h_{11E} = \frac{V_T}{I_B} = \frac{26 mV}{10 \mu A} = 2,6 k\Omega$$

$$h_{21E} = \beta = 80$$

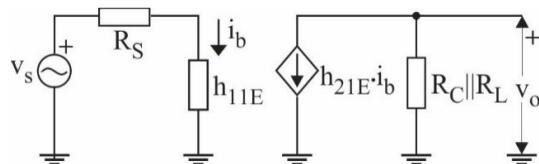

$$R_{CE} = R_C \parallel R_L = 3,3 k\Omega$$

$$v_b = h_{11E} \cdot i_b$$

$$\frac{v_b}{h_{11E}} + \frac{v_b - v_s}{R_S} = 0$$


$$\frac{v_o}{R_{CE}} + h_{21E} \cdot i_b = 0$$

$$A_n = \frac{v_o}{v_s} = -\frac{h_{21E} \cdot R_{CE}}{R_S + h_{11E}} = 9,5$$

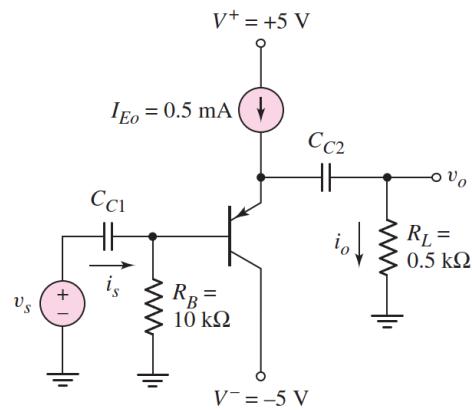5. ZADATAK

Na slici je prikazan pojačavač u sprezi sa zajedničkom bazom. Ukoliko je: $\beta=80$, $V_{BE}=0,7$ V, $V_A = 100$ V odrediti:

- Ulagnu otpornost $R_{in} = \frac{v_s}{i_s}$
- Naponsko pojačanje $A = \frac{v_o}{v_s}$
- Iznaznu otpornost R_o





Rešenje:

a)

$$I_B = \frac{I_{Eo}}{1 + \beta} = \frac{0.5 \text{ mA}}{1 + 80} = 6.17 \mu\text{A}$$
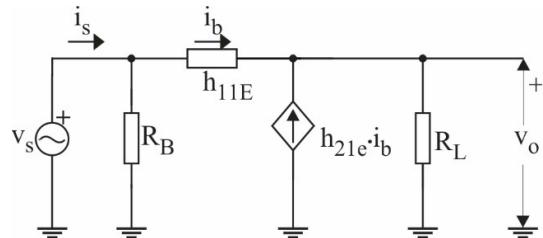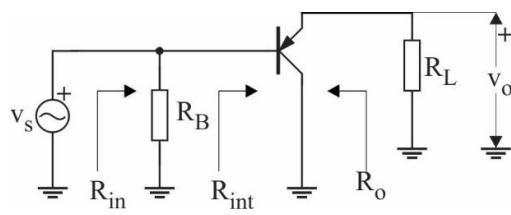
$$h_{11E} = \frac{V_T}{I_B} = \frac{26 \text{ mV}}{6.17 \mu\text{V}} = 4.2 \text{ k}\Omega$$



$$-i_b - h_{21E} \cdot i_b + \frac{v_0}{R_L} = 0$$

$$\underline{i_b = \frac{v_s - v_o}{h_{11E}}}$$

$$v_o = i_b \cdot R_L + h_{21E} \cdot i_b \cdot R_L$$

$$v_s = h_{11} \cdot i_b + v_o$$

$$v_s = h_{11} \cdot i_b + i_b \cdot R_L + h_{21E} \cdot i_b \cdot R_L$$


$$R_{int} = \frac{v_s}{i_b} = h_{11} + R_L + h_{21E} \cdot R_L = 44.7 \text{ k}\Omega$$

$$R_{in} = R_{int} \parallel R_B = 8.17 \text{ k}\Omega$$

b)

$$A_n = \frac{v_o}{v_s} = \frac{i_b}{v_s} \cdot \frac{v_o}{i_b} = \frac{1}{R_{int}} \cdot (1 + h_{21E}) \cdot R_L = \frac{(1 + h_{21E}) \cdot R_L}{h_{11} + R_L + h_{21E} \cdot R_L} = 0,9$$

c)

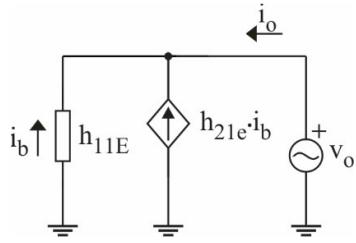

$$i_b = -\frac{v_o}{h_{11E}}$$

$$-i_o - i_b - h_{21E} \cdot i_b = 0$$

$$i_o = v_o \cdot \left(\frac{1 + h_{21E}}{h_{11E}} \right)$$

$$R_o = \frac{v_o}{i_o} = \frac{h_{11E}}{(1 + h_{21E})} = 52 \Omega$$