

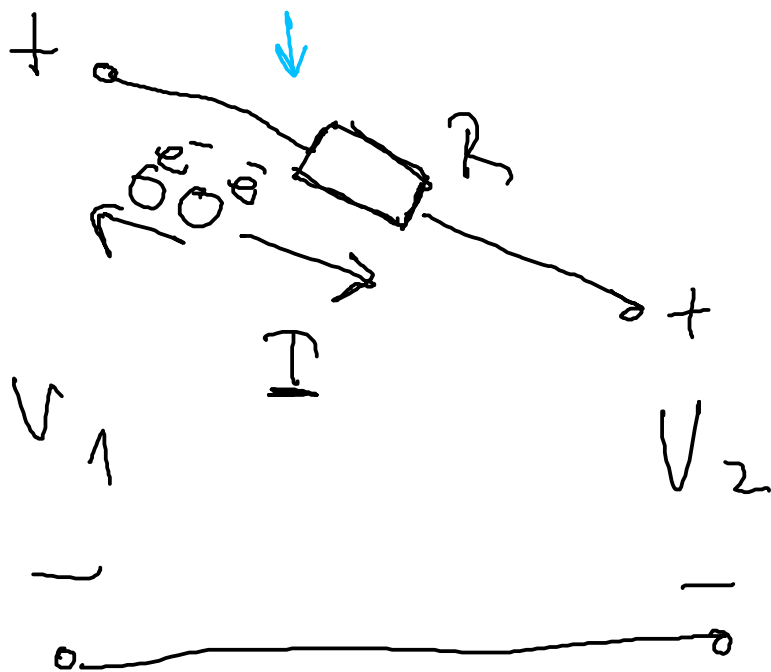


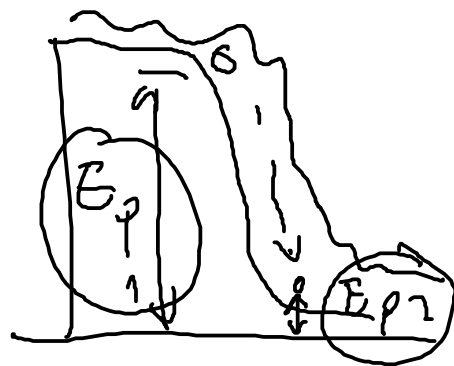• ОМОВ ЗАКОН: $I = \frac{V}{R} [A]$ $A = \frac{V}{\Omega} \rightarrow$ Ohm \leftarrow
 $I = V \cdot G [A]$ $A = V \cdot S \rightarrow$ who \rightarrow




$$I = \frac{V_1 - V_2}{R}$$

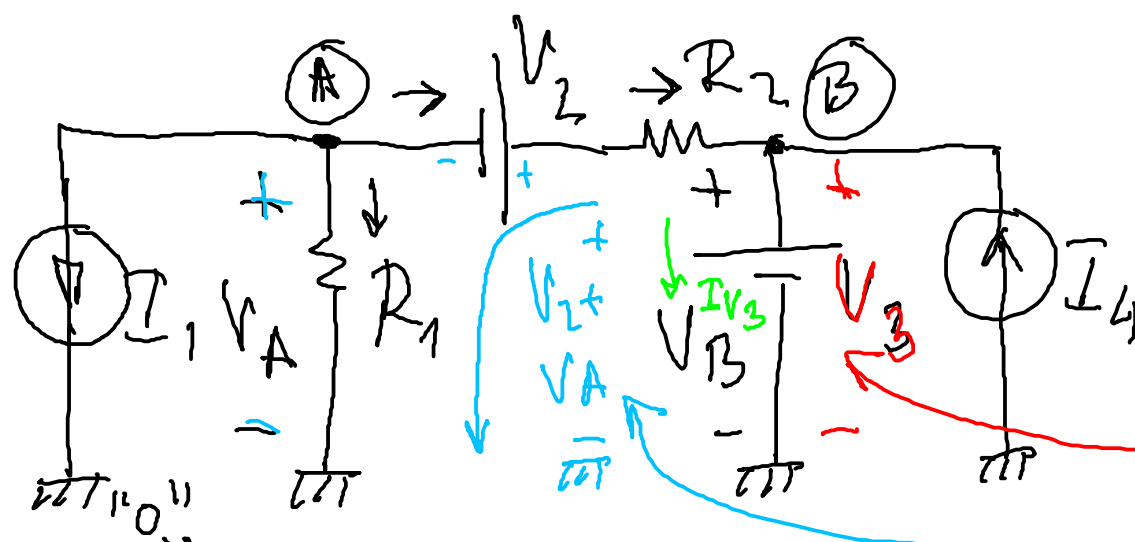



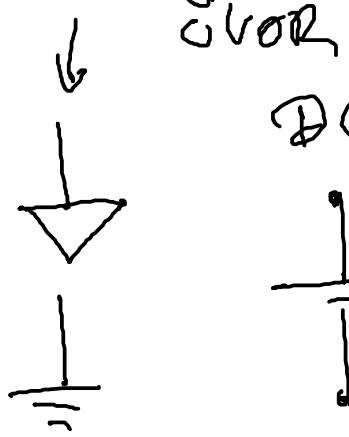
$$\textcircled{A} \quad I_1 + \frac{V_A}{R_1} + \frac{V_A + V_2 - V_3}{R_2} = 0$$



DC NAPRISKI IZVOR



≈

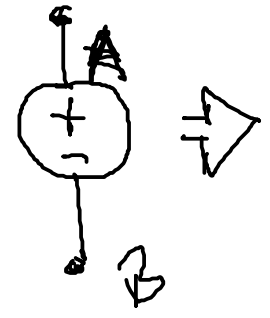

$$u_{AB} = V_{DC} + V_{AC}$$

$$\textcircled{B} \quad -I_4 - \frac{V_A + V_2 - V_3}{R_2} + I_{V_3} = 0$$

$$\textcircled{A} \quad I_1 + \frac{V_A}{R_1} + \frac{V_A + V_2 - V_3}{R_2} = 0$$

$$\textcircled{B} \quad -I_4 - \frac{V_A + V_2 - V_3}{R_2} + I_{V_3} = 0$$

$$\frac{1}{R_1} + \frac{1}{R_2} = G_1 + G_2 = \frac{1}{R_1 || R_2}$$

SLOBODNI
↓ VEKTOR

$$\frac{R_1 + R_2}{R_1 R_2} = \frac{1}{\frac{R_1 R_2}{R_1 + R_2}}$$

$$\begin{array}{l} \textcircled{A} \\ \textcircled{B} \end{array} \begin{bmatrix} G_1 + G_2 & 0 \\ -G_2 & 1 \end{bmatrix} \begin{bmatrix} V_A \\ V_2 \end{bmatrix} = \begin{bmatrix} -I_1 - (V_2 - V_3)G_2 \\ I_4 + (V_2 - V_3)G_2 \end{bmatrix}$$

↗
 $A_{2 \times 2}$

MATRICA SISTEMA

↗

$x_{2 \times 1} =$
VEKTOR PROMENLIVIH. $b_{2 \times 1}$

$$\begin{bmatrix} G_1 + G_2 & 0 \\ -G_3 & 1 \end{bmatrix} \begin{bmatrix} V_A \\ I_{V_3} \end{bmatrix} = \begin{bmatrix} -I_x - (V_2 - V_3)G_2 \\ I_y \end{bmatrix} ; \Delta = G_2 + G_1$$

$$V_A = \frac{\Delta V_A}{\Delta}$$

$$\Delta V_A = \begin{vmatrix} I_x & 0 \\ I_y & 1 \end{vmatrix} = I_x$$


$$\frac{G_3}{G_1 + G_2} = \frac{R_1 || R_2}{R_3}$$

$$I_{V_3} = \frac{\Delta I_{V_3}}{\Delta}$$

$$\frac{1}{G_1 + G_2} = R_1 || R_2$$

$$V_A = \frac{I_x}{G_1 + G_2} = I_x \cdot (R_1 || R_2) \quad \Delta I_{V_3} = \begin{vmatrix} G_1 + G_2 & I_x \\ -G_3 & I_y \end{vmatrix} = (G_1 + G_2)I_y + G_3 I_x$$


$$I_{V_3} = I_y + \frac{G_3}{G_1 + G_2} I_x = I_y + \frac{R_1 || R_2}{R_3} \cdot I_x$$

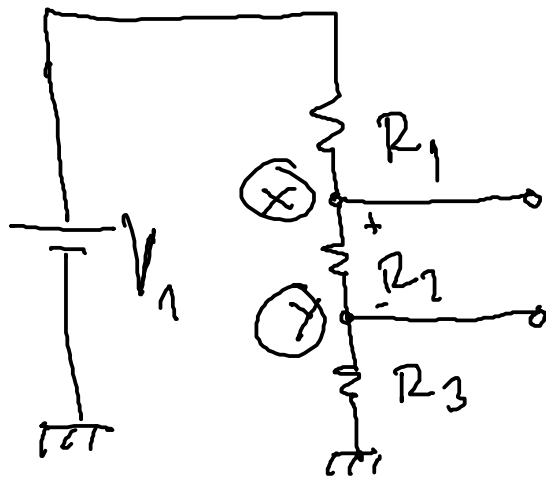


$$V_x = V_1 \cdot \frac{R_2 + R_3}{R_2 + R_3 + R_1}$$

$$V_y = V_1 \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

$$; V_{xy} = V_{R_2} = V_x - V_y$$

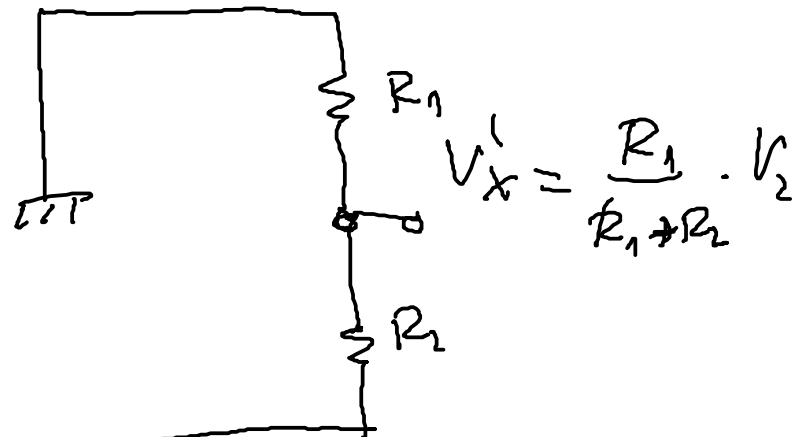

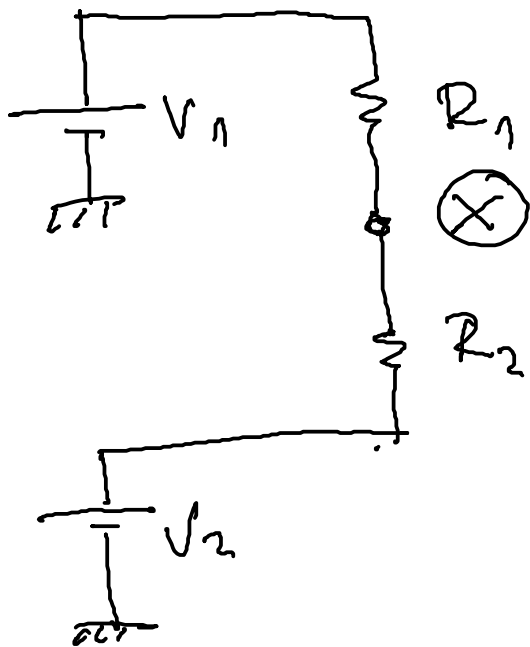
$$V_x' = \frac{R_1}{R_1 + R_2} \cdot V_2$$




! SUPERPOZICIJA !


$$V_x = V_x' + V_x''$$

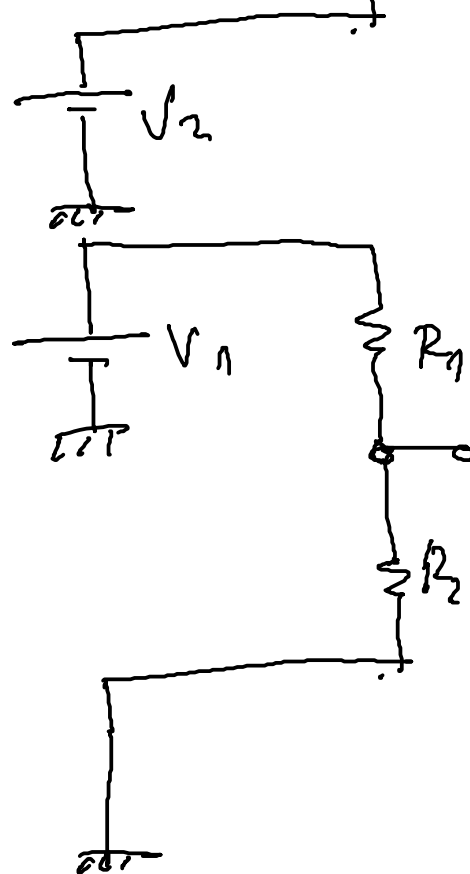

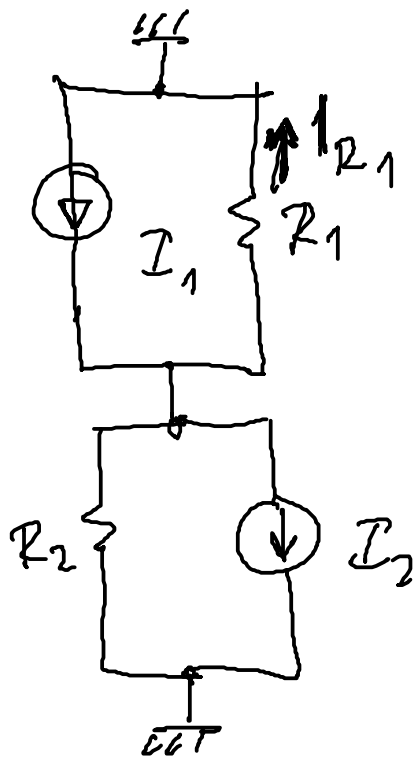
$$V_x'' = \frac{R_2}{R_2 + R_1} \cdot V_1$$




$$I_{R_1} = I_{R_1}^I + I_{R_1}^{II}$$

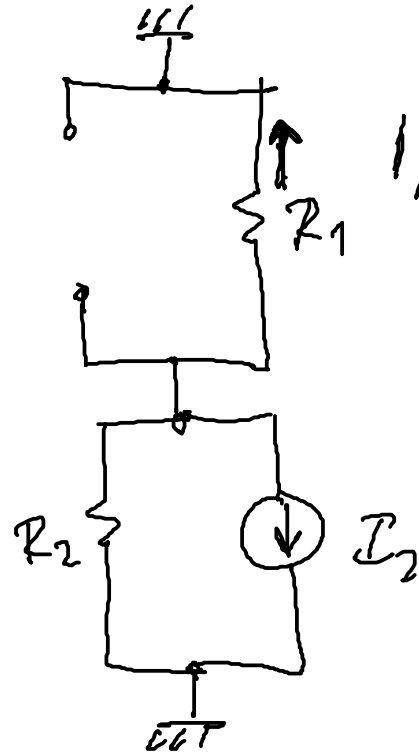
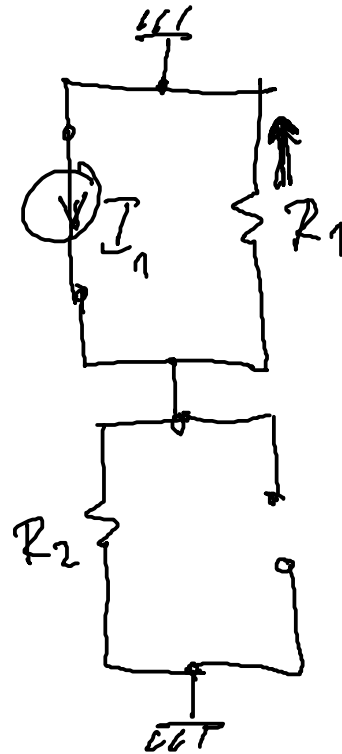
$$I_{R_1}^I = \frac{R_2}{R_1 + R_2} \cdot I_2$$


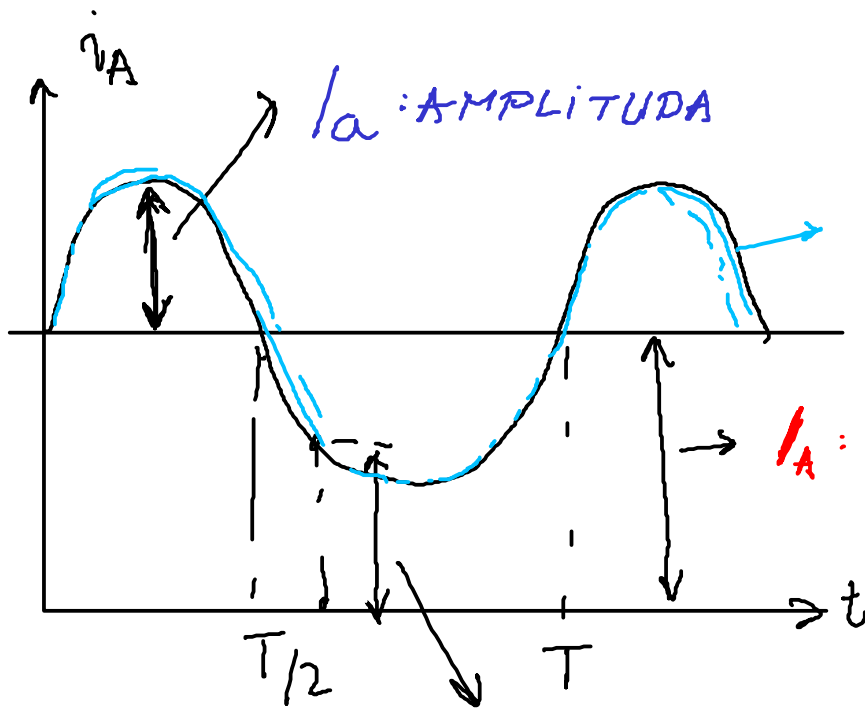
$$I_{R_1}^{II} = \frac{R_2}{R_1 + R_2} \cdot I_1$$



i_a : VREMENSKI PROMENLJIVI DEO SIGNALA (AC)

I_A : SREDNJA VREDNOST (DC)

TREKUTNJA VREDNOST: $i_A = \overset{DC}{I_A} + \overset{AC}{i_a} = I_A + I_a \cdot f(\omega t)$

DC ANALIZA: U KOLU PRISUTNI SAMO VREMENSKI NE PROMENLJIVI SIGNAL.

ANALIZA VELIKIH SIGNALA: —||— SAMO PROMENLJIVI SIGNALI VELIKIH PRIRASTAJA - AMPLITUDA (REDA NAPONA NAPAJANJA)

ANALIZA MALIH SIGNALA: —||— SAMO VREMENSKI PROMENLJIVI SIGNALI MALIH PRIRASTAJA - AMPLITUDA (REDA $\frac{kT}{2}$ (mV)).