

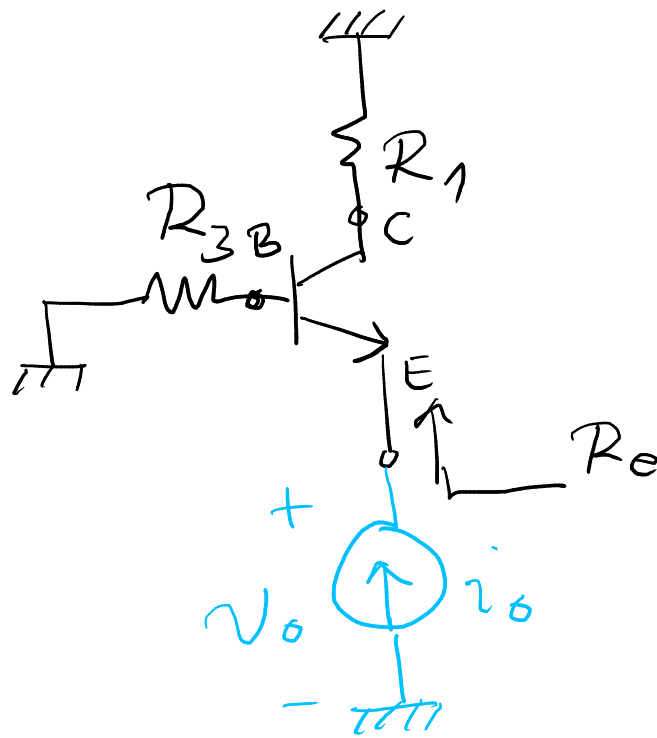


$$R_b = r_{\pi} + (1 + \beta)R_2$$

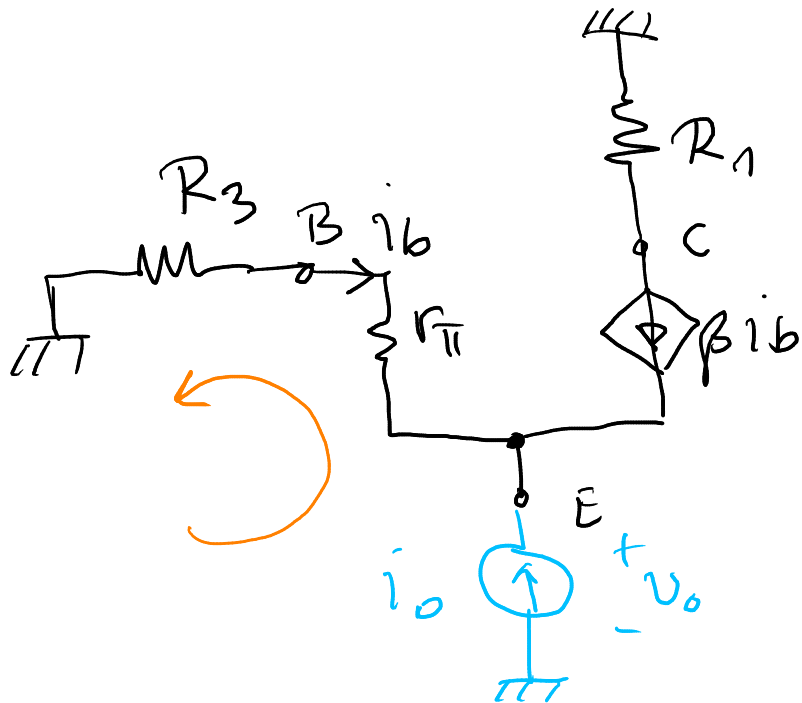

$$R_e = \frac{V_o}{i_o}$$

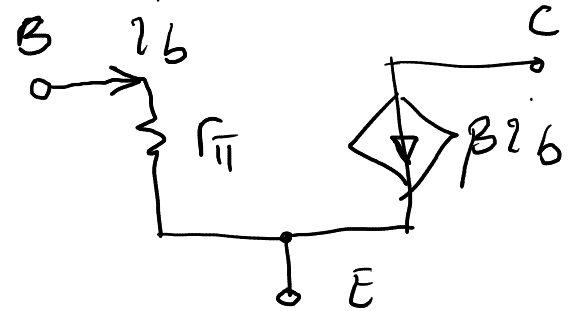

$$\textcircled{E} \quad (1 + \beta)i_b + i_o = 0$$

$$\textcircled{K} \quad v_o = -i_b(r_{\pi} + R_3)$$



$$R_e = \frac{v_o}{i_o} = \frac{r_{\pi} + R_3}{1 + \beta}$$

$$\beta \gg 1 \Rightarrow R_e = \frac{r_{\pi} + R_3}{\beta} \Big|_{\beta = g_m \cdot r_{\pi}} = \frac{1}{g_m} + \frac{R_3}{\beta} \Big|_{R_3 \rightarrow 0} \approx \frac{1}{g_m}$$

AKO JE $V_A \rightarrow \infty V$ KOLIKO JE R_c ?

$$V_A \rightarrow \infty V \Rightarrow r_o \approx \frac{V_A}{I_C} \rightarrow \infty \Omega$$

$$R_c \rightarrow \infty \Omega$$

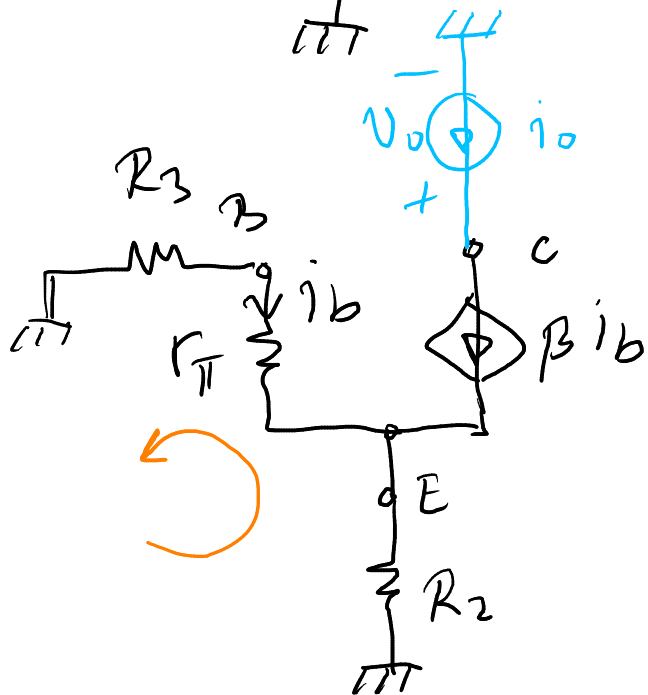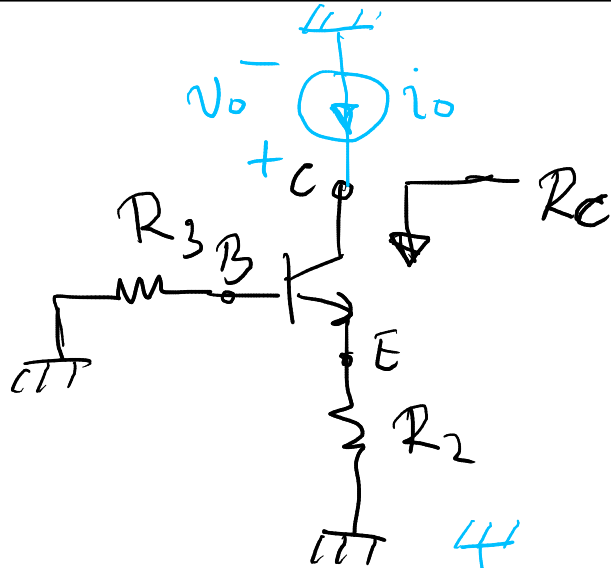


$$(C) \quad i_o = \beta i_b \Rightarrow i_b = \frac{i_o}{\beta}$$

$$(E) \quad (1 + \beta) i_b = \frac{V_e}{R_2} \quad \left. \vphantom{(E)} \right\} \Rightarrow i_b = 0 A$$

$$(K) \quad V_e = -i_b (r_{\pi} + R_3) \quad \left. \vphantom{(K)} \right\} \begin{array}{l} \Rightarrow i_b = 0 A \\ \Downarrow \\ i_o = \beta i_b = 0 A \end{array}$$
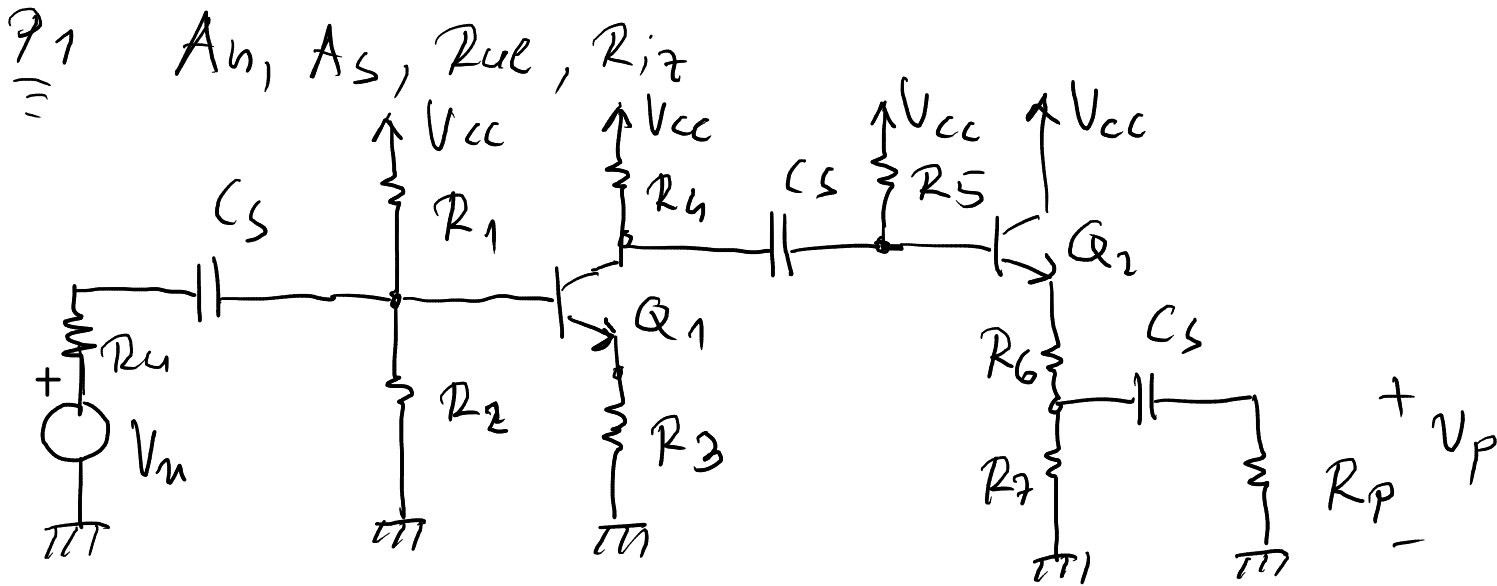
$$R_c = \frac{V_o}{i_o} \rightarrow \infty \Omega$$



(DC) $X_{Cs} = \frac{1}{\omega C_s} = \frac{1}{2\pi f \cdot C_s} \Big|_{\substack{\text{ZA DC, } f \rightarrow 0 \text{ Hz} \\ \rightarrow \infty \Omega}}$

$V_T = \frac{kT}{q} \Big|_{\substack{\approx 26 \text{ mV} \\ T=300 \text{ K}}}$


$I_{B_1} = \frac{V_{TEV} - V_{BE}}{R_{TEV} + (1+\beta)R_3} \Rightarrow I_{C_1} = \beta I_{B_1} \Rightarrow g_{m_1} = \frac{I_{C_1}}{V_T}$

$R_{TEV} = R_4 \parallel R_2$

$V_{TEV} = \frac{R_2}{R_2 + R_1} \cdot V_{CC}$

$r_{\pi_1} = \frac{V_T}{I_{B_1}} = \frac{\beta_1}{g_{m_1}}$

$r_{o_1} \approx \frac{V_{A1}}{I_{C_1}} \Big|_{\substack{\rightarrow \infty \Omega \\ V_A \rightarrow \infty \text{ V}}}$

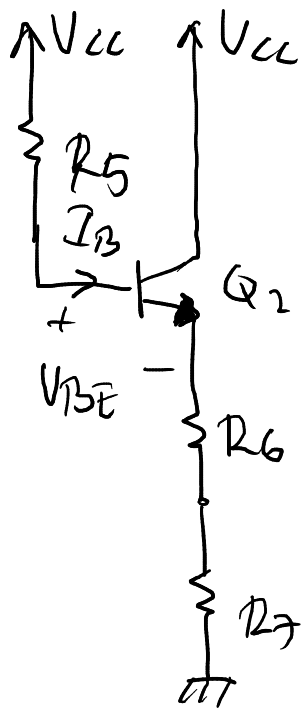


$$I_{B_2} = \frac{V_{CC} - V_{BE}}{R_5 + (1 + \beta_2)(R_6 + R_7)} \Rightarrow I_{C_2} = \beta_2 I_B \Rightarrow g_{m_2} = \frac{I_{C_2}}{V_T}$$



$$r_{o_2} \approx \frac{V_{A_2}}{I_{C_2}} \quad \left| \begin{array}{l} \rightarrow \infty \Omega \\ V_{A_2} \rightarrow \infty V \end{array} \right.$$

$$r_{\pi_2} = \frac{V_T}{I_{B_2}} = \frac{\beta_2}{g_{m_2}}$$

SS (AC) ; $C_s \rightarrow \infty F \Rightarrow X_{C_s} = \frac{1}{2\pi f \cdot C_s} \rightarrow 0 \Omega$ (MF, 2F)


A_n

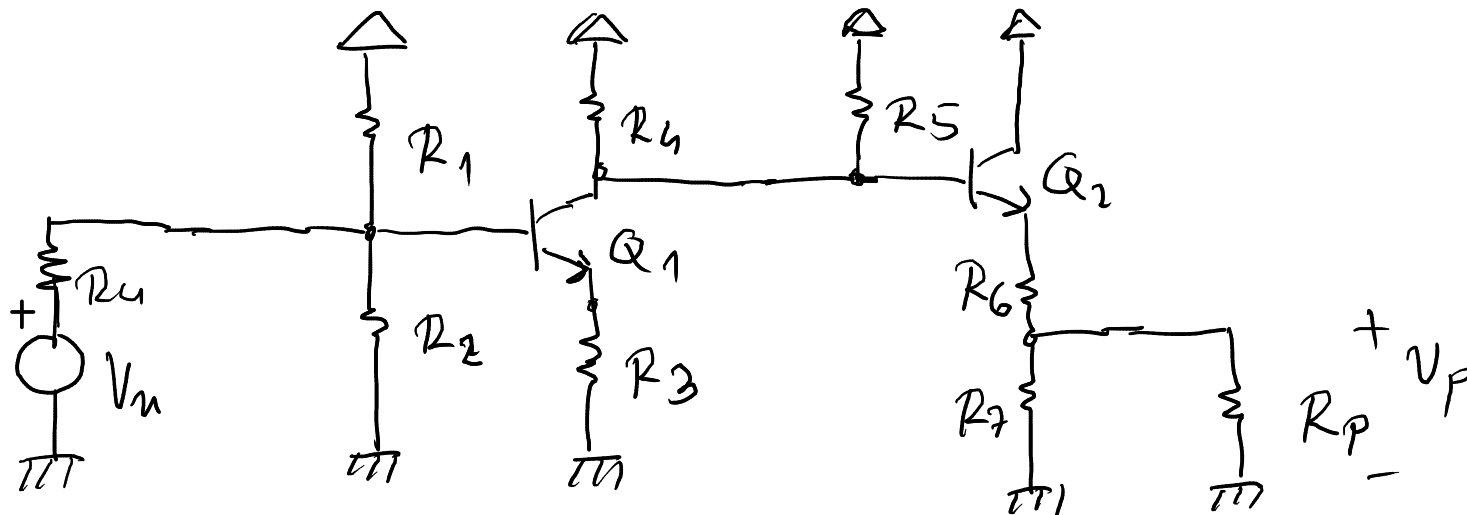

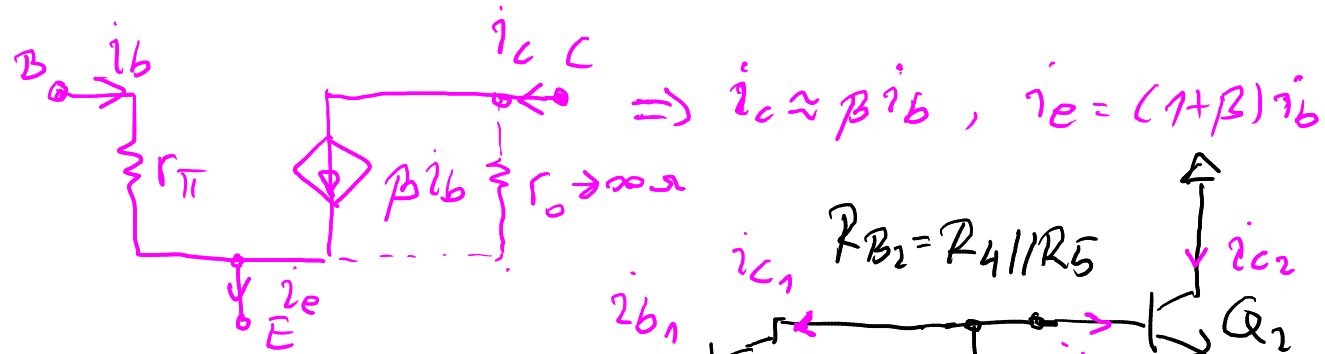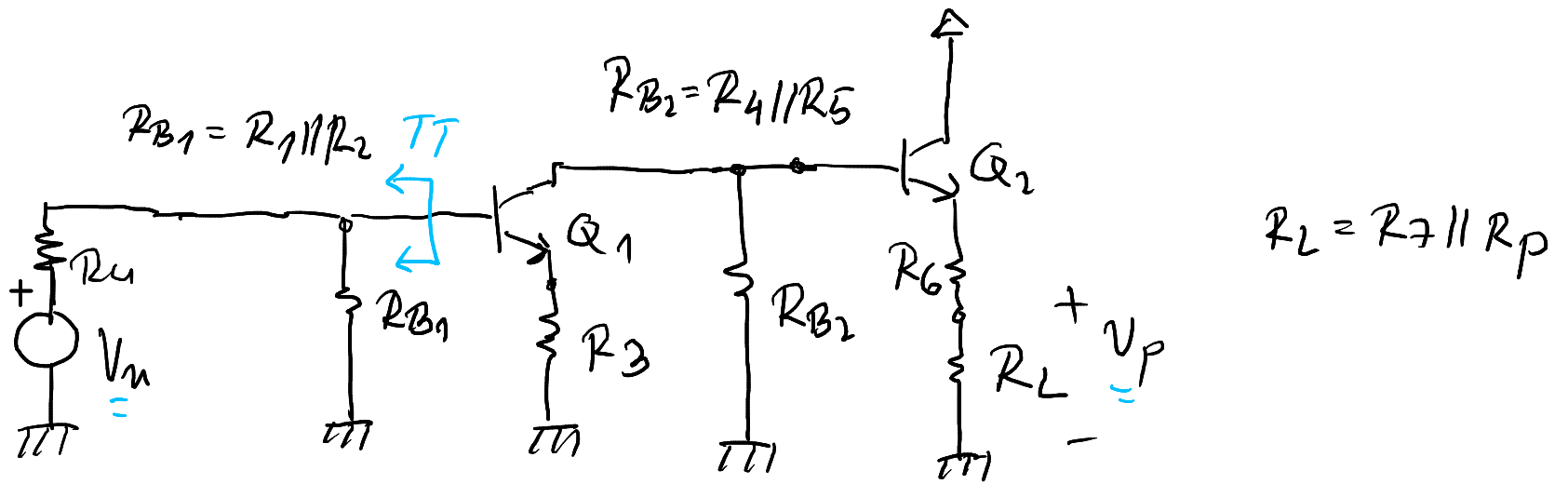


$$R_{tev} = R_{B1} || R_u$$

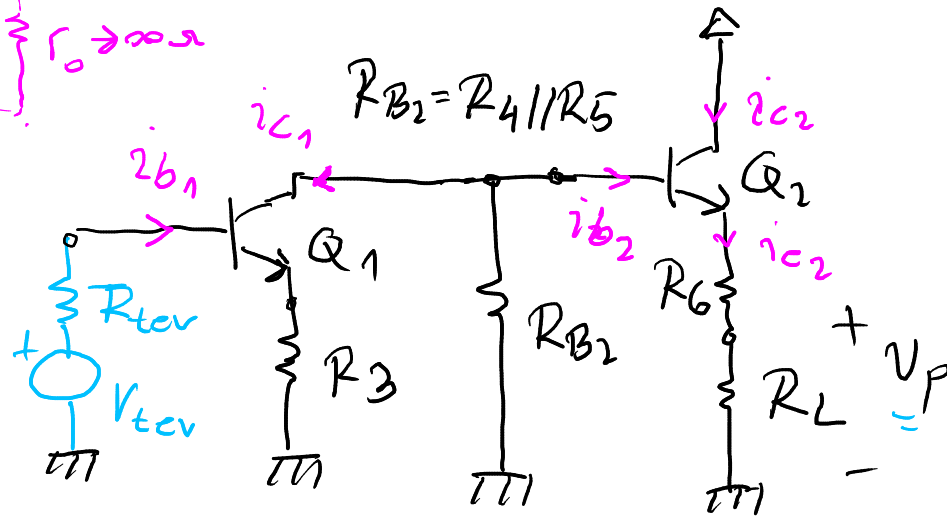
$$V_{tev} = \frac{R_{B1}}{R_{B1} + R_u} \cdot V_u$$



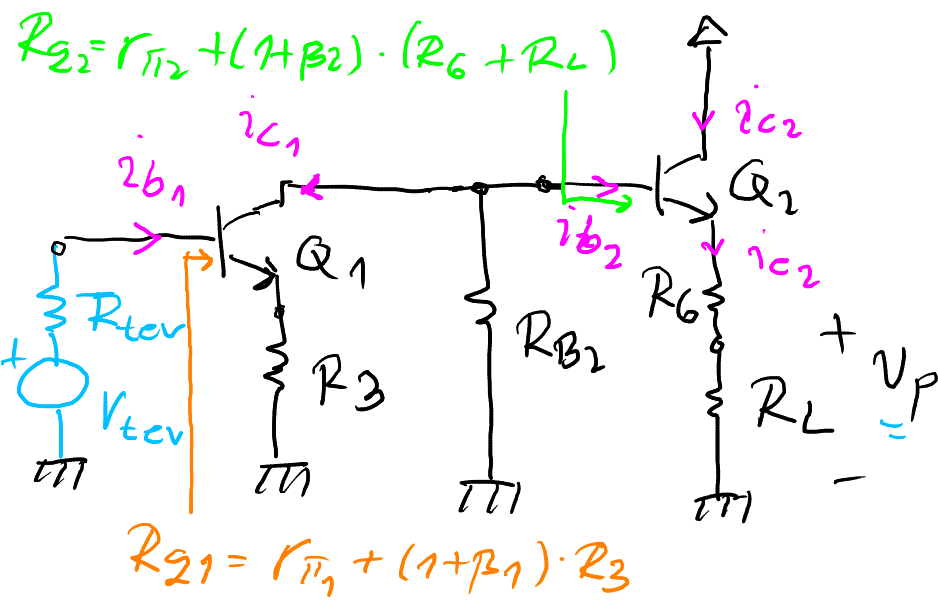
$$A_n = \frac{V_p}{V_u} = \frac{V_p}{i_{e2}} \cdot \frac{i_{e2}}{i_{b2}} \cdot \frac{i_{b2}}{i_{c1}} \cdot \frac{i_{c1}}{i_{b1}} \cdot \frac{i_{b1}}{V_{tev}} \cdot \frac{V_{tev}}{V_u}$$


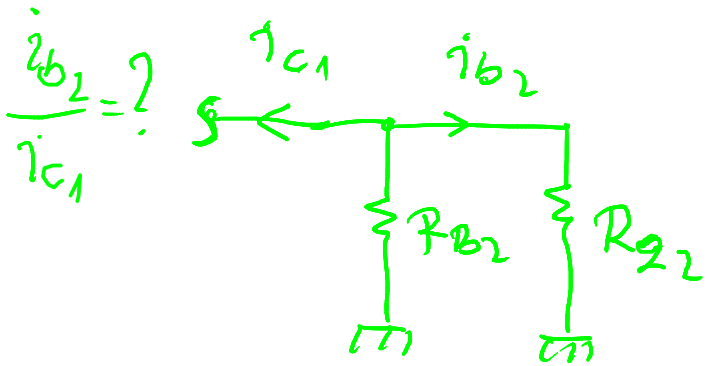
$$A_n = R_L \cdot (1 + \beta_2) \cdot \left(- \frac{R_{B2}}{R_{B2} + R_{Q2}} \right) \cdot \beta_1 \cdot \frac{1}{R_{tev} + R_{Q1}} \cdot \frac{R_{B1}}{R_{B1} + R_u}$$


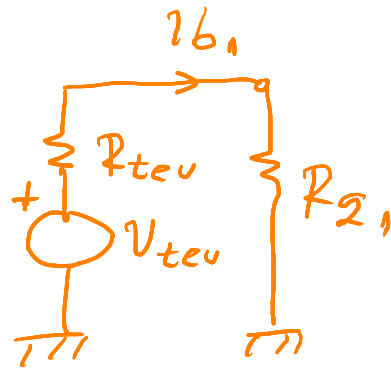
$$\frac{i_{b2}}{i_{c1}} = \frac{-R_{B2}}{R_{B2} + R_{Q2}}$$




$$\frac{i_{b1}}{V_{tev}} = \frac{1}{R_{tev} + R_{Q1}}$$



A_s

R_{ue}

R_{iz}

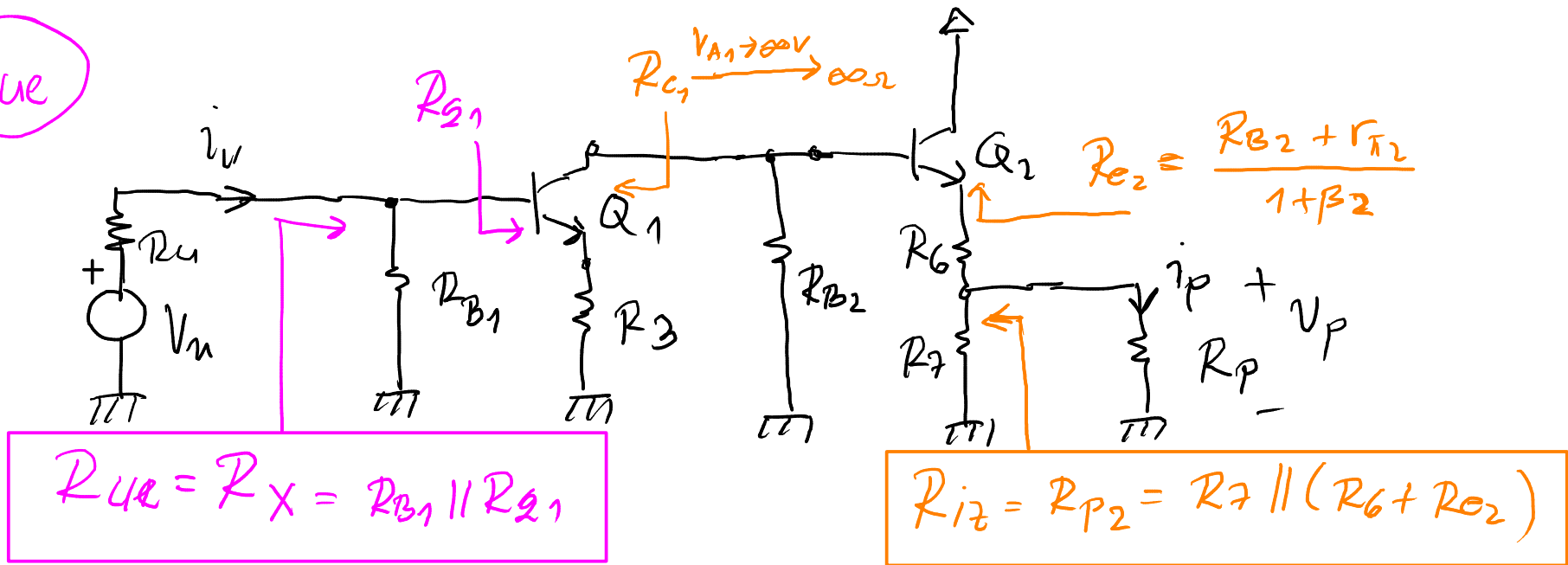
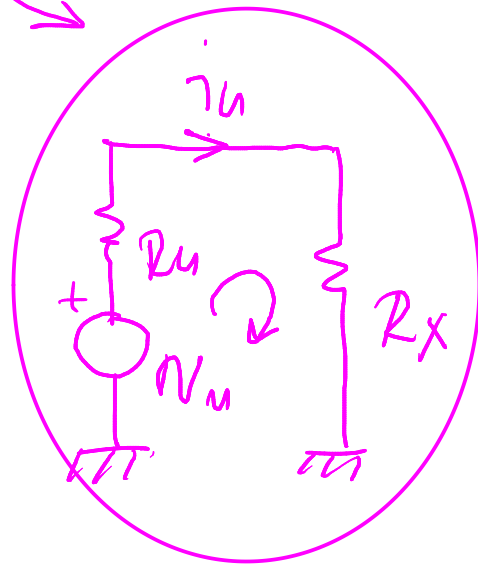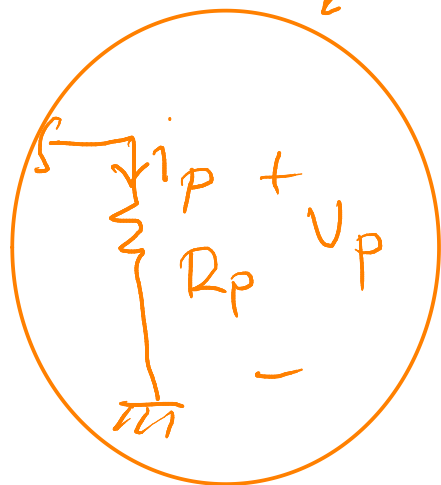
$$A_s = \frac{i_p}{i_u} = \left(\frac{i_p}{v_p} \right) \frac{v_p}{v_u} \cdot \left(\frac{v_u}{i_u} \right) = \frac{1}{R_p} \cdot A_u \cdot (R_u + R_x) = \frac{R_u + R_x}{R_p} \cdot A_u$$








MOS-FET POLARIZACIJA (DC REŽIM)

$$I_D = A (V_{GS} - V_{TH})^2 \rightarrow \text{NMOS} (V_{TH} > 0V)$$

$$A = \left[\frac{A}{V^2} \right] = \mu_{eff} C_{ox} \frac{W}{2L} = A$$

$$I_S = A (V_{SG} - |V_{TH}|)^2 \rightarrow \text{PMOS} (V_{TH} < 0V)$$

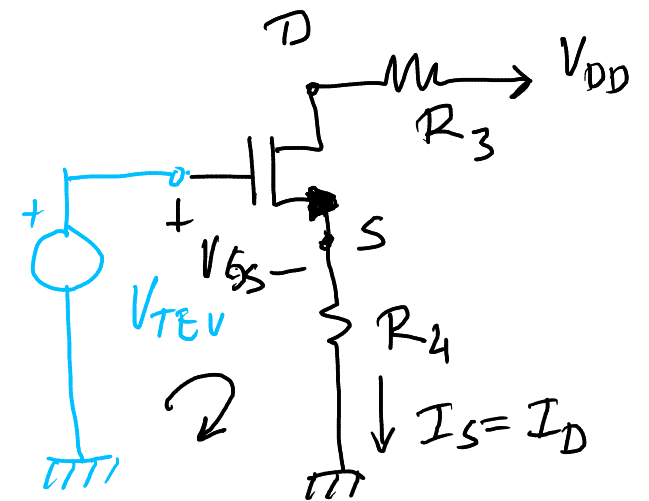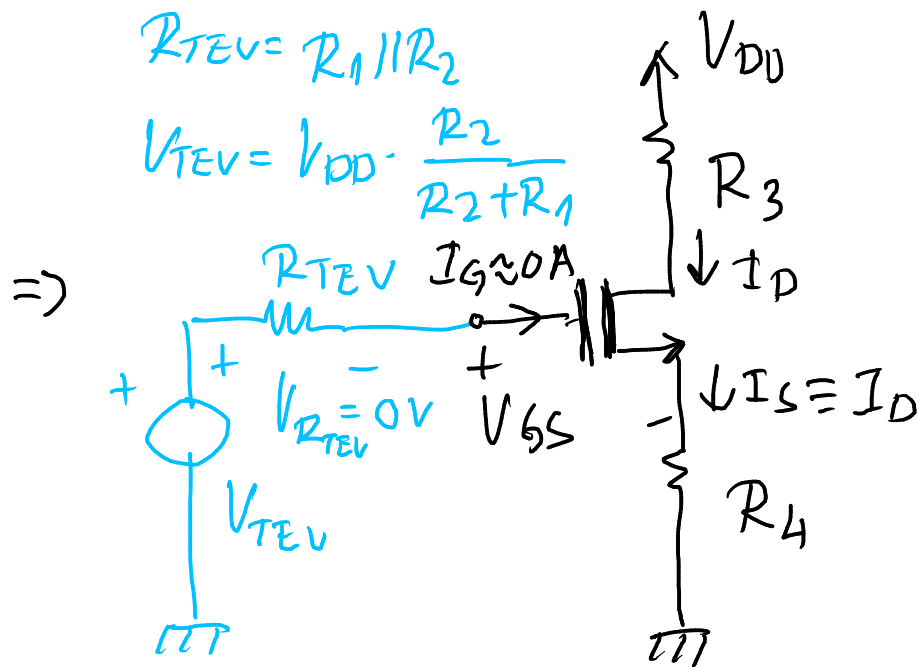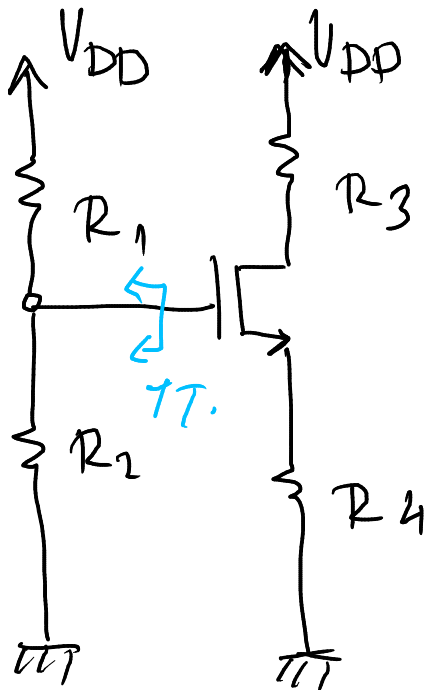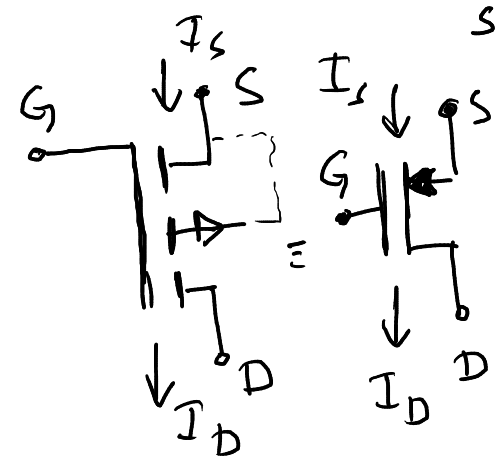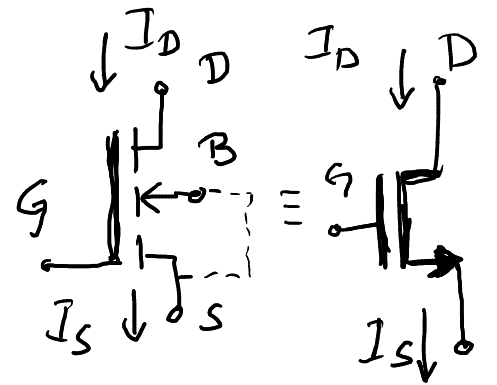

$$V_{TEV} = V_{GS} + I_D \cdot R_4 = V_{GS} + A \cdot \underbrace{(V_{GS} - V_{TH})^2}_{V_{OV} = V_{GS} - V_{TH} \rightarrow \text{"OVERDRIVE"} \text{ НАПОН}} \cdot R_4$$

$$V_{TEV} - V_{TH} = V_{GS} - V_{TH} + A \cdot R_4 (V_{GS} - V_{TH})^2$$

$$V_{TEV} - V_{TH} = V_{OV} + A R_4 \cdot V_{OV}^2$$

$$V_{OV}^2 (A \cdot R_4) + V_{OV} - (V_{TEV} - V_{TH}) = 0$$

$$V_{OV_{1/2}} = \frac{-1 \pm \sqrt{1 + 4 A R_4 \cdot (V_{TEV} - V_{TH})}}{2 \cdot (A \cdot R_4)}$$


$$V_{OV} > 0 \Rightarrow V_{OV} = \frac{-1 + \sqrt{1 + 4 A R_4 (V_{TEV} - V_{TH})}}{2 A R_4}$$

$$I_D = A \cdot V_{OV}^2 ; \quad g_m = \frac{\partial I_D}{\partial V_{GS}} = 2 A V_{OV} = \frac{2 I_D}{V_{OV}} = 2 \sqrt{A \cdot I_D} \quad \Big| \quad I_D = A \cdot V_{OV}^2$$

- MODULACIJA DUŽINE KANALA \equiv ERLIJEV EFEKAT KOD BJT

$$I_D = A (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}); \quad \lambda \propto \frac{\Delta L}{L}; \quad \lambda = \frac{1}{V_A}$$

$$r_o = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{\lambda \rightarrow 0} \approx \frac{1}{\lambda I_D} \equiv \frac{V_A}{I_D}$$

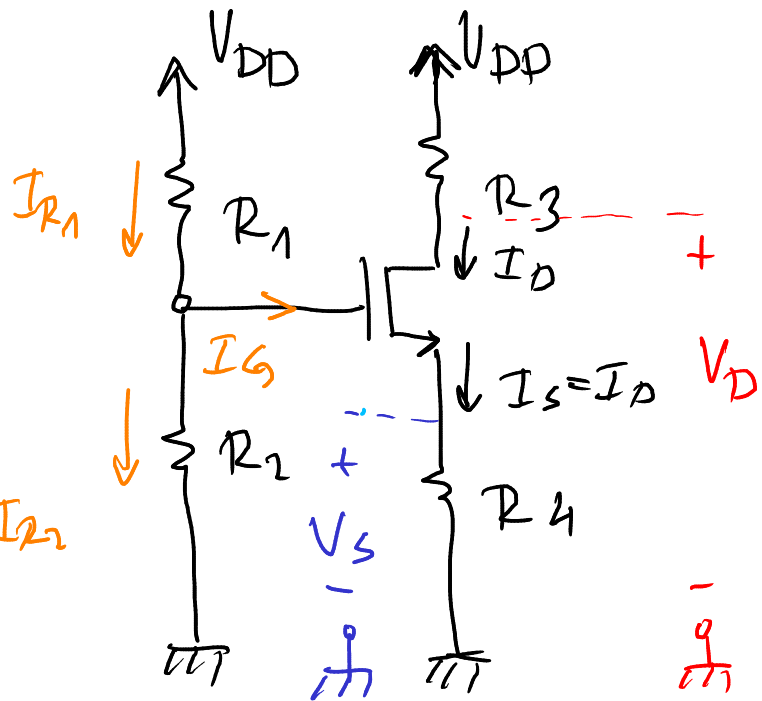

$$V_G = V_{TEV} = \frac{R_2}{R_2 + R_1} V_{DD}$$

$$I_G \rightarrow 0 \text{ A} \Rightarrow I_{R1} = I_{R2}$$

$$V_D = V_{DD} - R_3 I_D$$

$$I_{R1} = I_{R2} = \frac{V_{DD}}{R_1 + R_2}$$

$$V_S = R_4 \cdot I_D$$

$$\text{ZA } R_4 \rightarrow 0 \Omega \Rightarrow V_G = V_{TEV} = V_{GS} \Rightarrow$$

$$V_{OV} = V_{TEV} - V_{TH} \Rightarrow I_D = A \cdot V_{OV}^2$$