

P1
 POZHATI SU SUI PARAMETRI MOS-FET (A_i, V_{THi}, V_{A_i}) i
 POZHATI SU SUI ELEMENTI KOCA
 (R_i, V_{DD}).


za DC: $I_D \approx A (V_{GS} - V_{TH})^2$

$V_{DD} = I_{D1} \cdot R_1 + V_{GS1} \leftarrow$ SA OBE STRANICE
 ODUZETI V_{TH1}

$V_{DD} - V_{TH1} = A \cdot R_1 (V_{GS1} - V_{TH1})^2 + V_{GS1} - V_{TH1}$

$A \cdot R_1 V_{OV1}^2 + V_{OV1} - (V_{DD} - V_{TH1}) = 0$

$V_{OV1} = V_{GS1} - V_{TH1}$

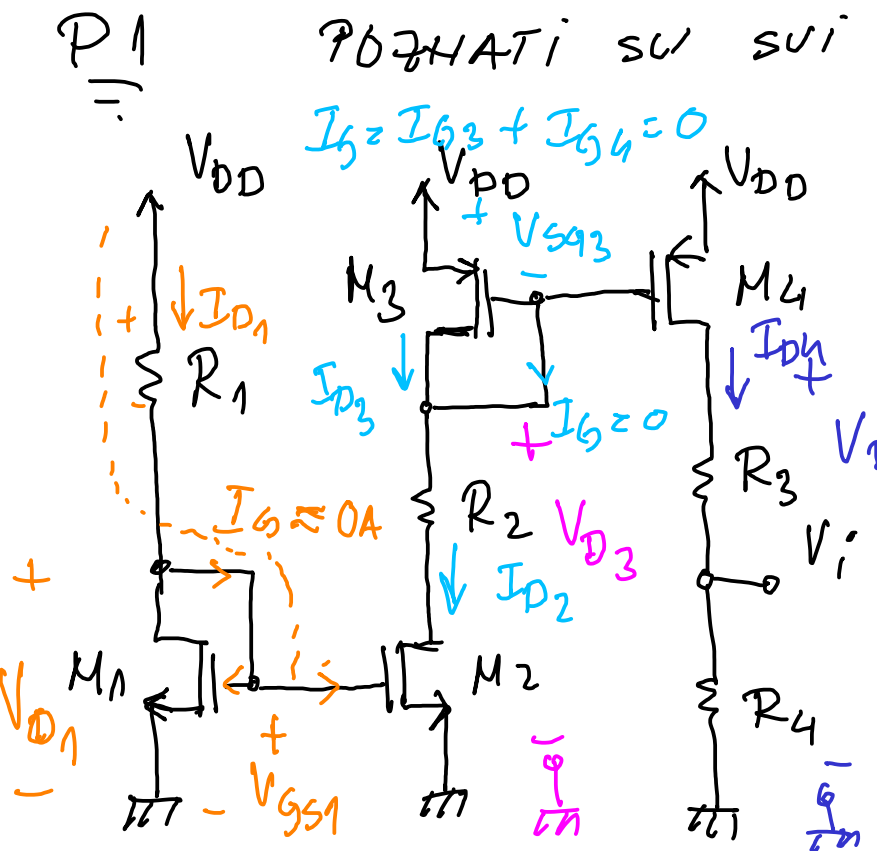

$I_{G2} = I_{G1} + I_{G2} = 0A$

$$V_{OV1} = \frac{-1 + \sqrt{1 + 4 \cdot A \cdot R_1 \cdot (V_{DD} - V_{TH1})}}{2 \cdot A \cdot R_1}$$

$\Rightarrow I_{D1} = A_1 \cdot V_{OV1}^2$
 $V_{GS1} = V_{GS1} = V_{TH1} + V_{OV1}$

ZADATAK

$A_2 \neq A_1, V_{GS2} = V_{GS1} \Rightarrow \underbrace{V_{TH1} + \sqrt{\frac{I_{D1}}{A_1}}}_{V_{GS1}} = \underbrace{V_{TH2} + \sqrt{\frac{I_{D2}}{A_2}}}_{V_{GS2}} \Rightarrow \frac{I_{D1}}{A_1} = \frac{I_{D2}}{A_2}$

$V_{TH2} = V_{TH1}$
 SA ŽEME

$$I_{D2} = \frac{A_2}{A_1} \cdot I_{D1}$$

$$I_{D3} = I_{D2}$$

$$V_{D3} = V_{DD} - V_{SG3}$$

$$A_3 \neq A_4 \Rightarrow \frac{I_{D3}}{A_3} = \frac{I_{D4}}{A_4} \Rightarrow I_{D4} = \frac{A_4}{A_3} I_{D3} \Rightarrow V_{SG3} = |V_{TH3}| + \sqrt{\frac{I_{D3}}{A_3}} = V_{SG4}$$

$$V_{D1} = V_{G1} = V_{GS1} = V_{TH1} + \sqrt{\frac{I_{D1}}{A_1}} = V_{DD} - I_{D1} \cdot R_1$$

$$V_{D4} = I_{D4} \cdot (R_3 + R_4)$$

$$V_i = I_{D4} \cdot R_h = \frac{R_h}{R_3 + R_4} \cdot V_{D4}$$

$$P_2 \{A_u, R_{ul}, R_{iz}\} = ?$$



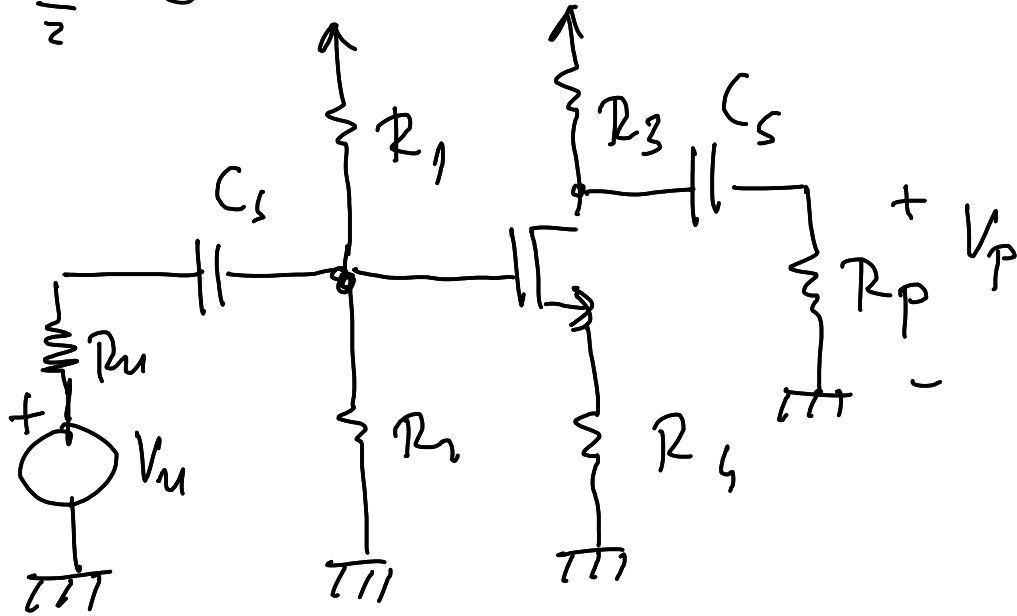
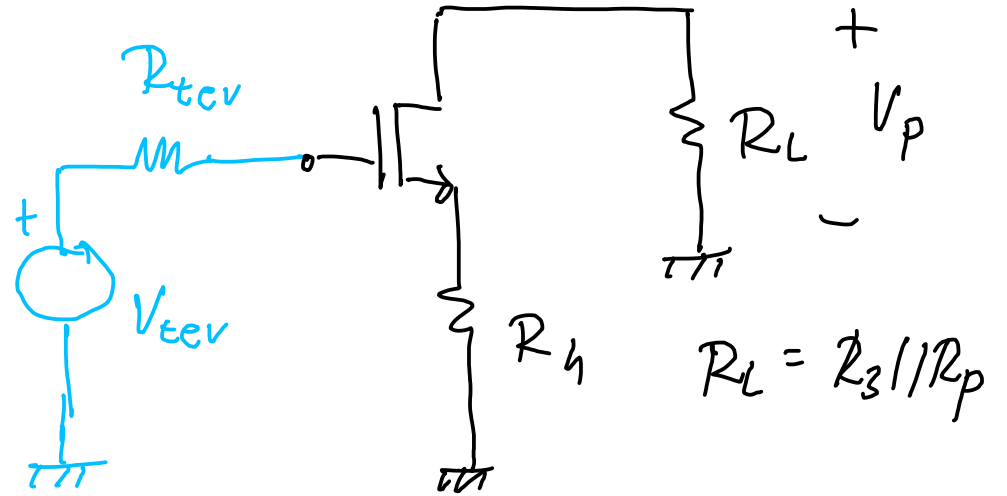
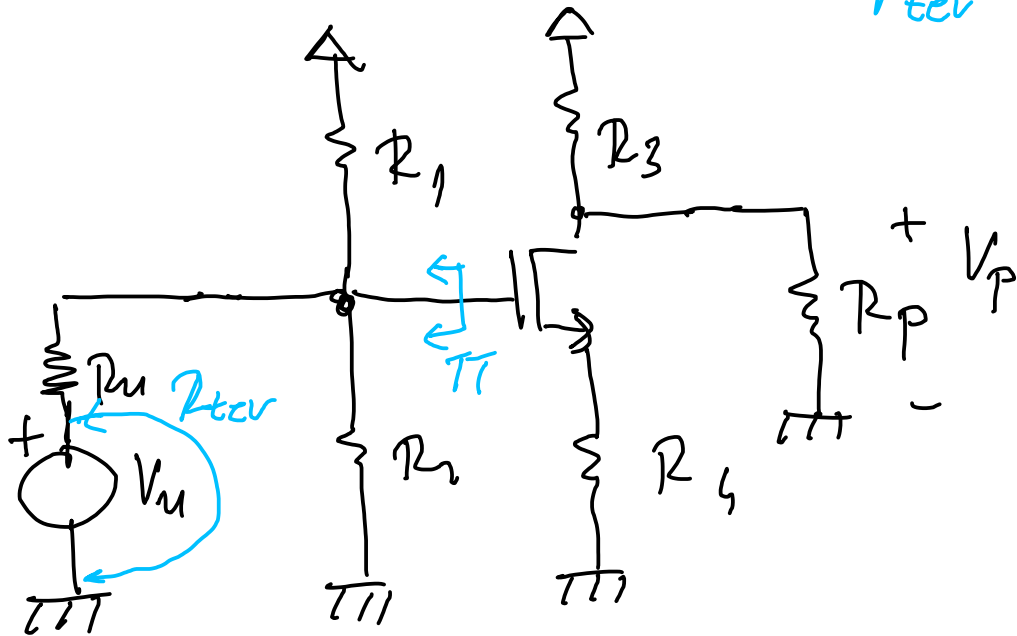



Схема экв AC ("SS")
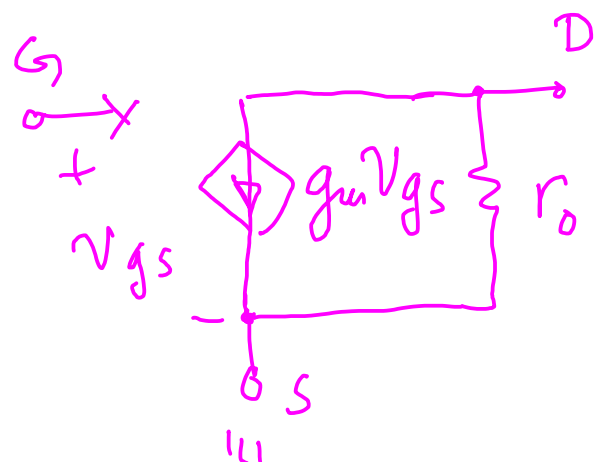
$$V_{tecv} = \frac{R_g}{R_g + R_u} V_u, \quad R_g = R_1 \parallel R_2, \quad R_{tecv} = R_g \parallel R_u$$




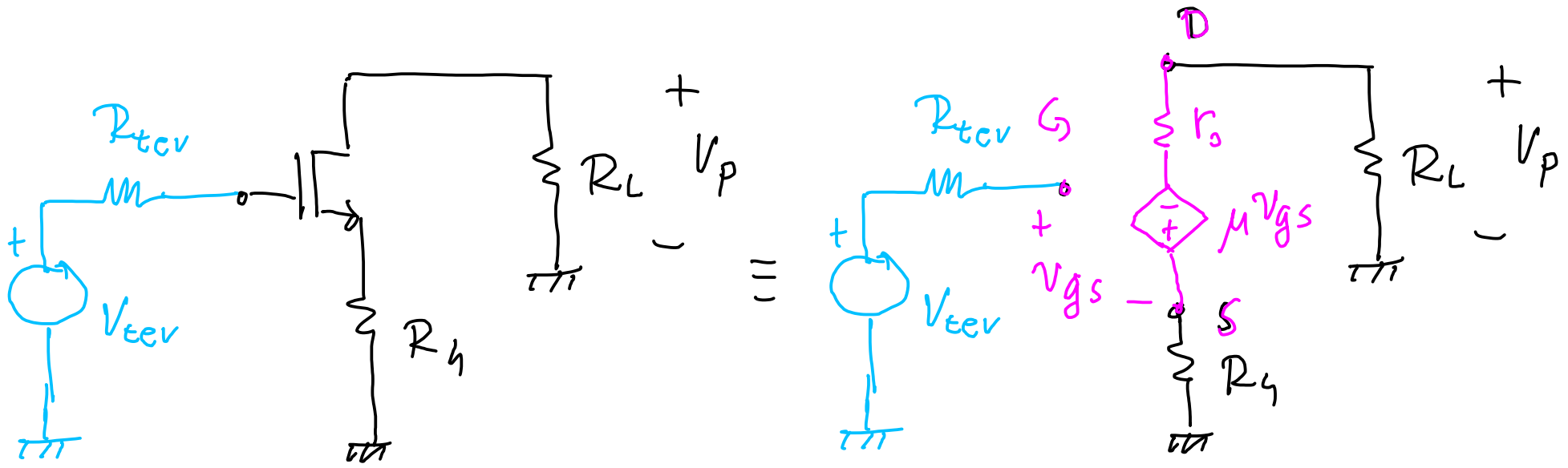

$I_n' = g_m V_{gs}$
 $Z_{in}' = r_o$

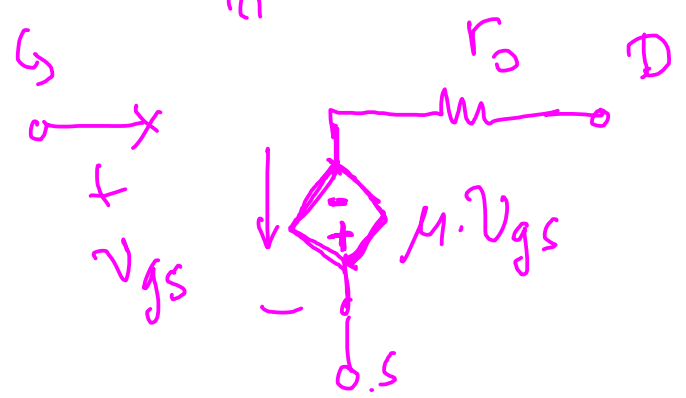

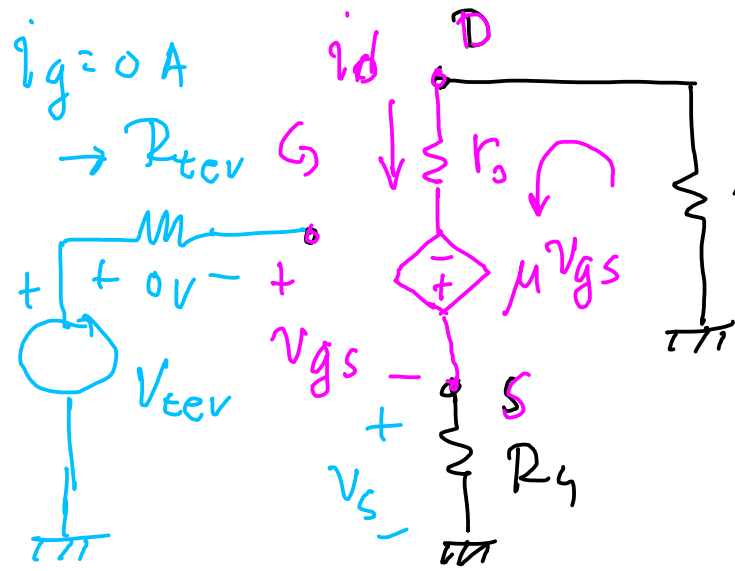$V_{teev}' = I_n' \cdot R_n' = g_m r_o V_{gs} = \mu V_{gs} \Rightarrow \mu = g_m \cdot r_o$
 $R_{teev}' = Z_{in}' = r_o$



$i_g = 0 \text{ A}$
 $\rightarrow R_{teer}$
 V_{teer}
 v_{gs}
 v_s
 $V_g = V_{teer}$; $v_s = i_d R_s$

$$0 = i_d (R_L + r_o) - \mu v_{gs} + i_d R_s$$

$$v_{gs} = V_g - v_s = V_{teer} - i_d \cdot R_s$$

$$V_p = -i_d \cdot R_L$$

$$0 = i_d (R_L + r_o + R_s) - \mu V_{teer} + \mu i_d R_s$$


$$i_d = \frac{\mu \cdot V_{teer}}{R_L + r_o + (1 + \mu) R_s}$$

$$V_p = -i_d \cdot R_L = - \frac{\mu R_L \cdot V_{teer}}{R_L + r_o + (1 + \mu) R_s} = \frac{R_G V_u}{R_G + R_u} \cdot \frac{-\mu R_L}{R_L + r_o + (1 + \mu) R_s}$$

$$A_u = \frac{V_p}{V_u} = \frac{R_G}{R_G + R_u} \cdot \frac{-\mu R_L}{R_L + r_o + (1 + \mu) R_s}$$

ZA POJAČAVAČ SA ZS BEZ DEGENERACIJE SORSA:

$$Z_A AC: Z_h = \frac{R_L}{1 + s C_s R_L} \quad \left| \begin{array}{l} \rightarrow 0 \Omega \\ C_s \rightarrow \infty F \end{array} \right.$$

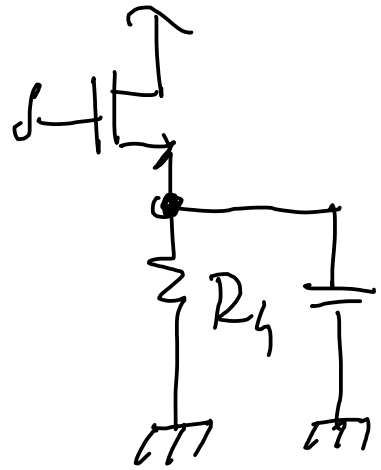


$$A_n = \frac{R_G}{R_G + R_{in}}$$


$$\frac{-\mu \cdot R_L}{R_L + r_o} = \frac{R_G}{R_G + R_{in}} \cdot (-g_m (R_L || r_o))$$

$\mu = g_m r_o$



Z_{ul}

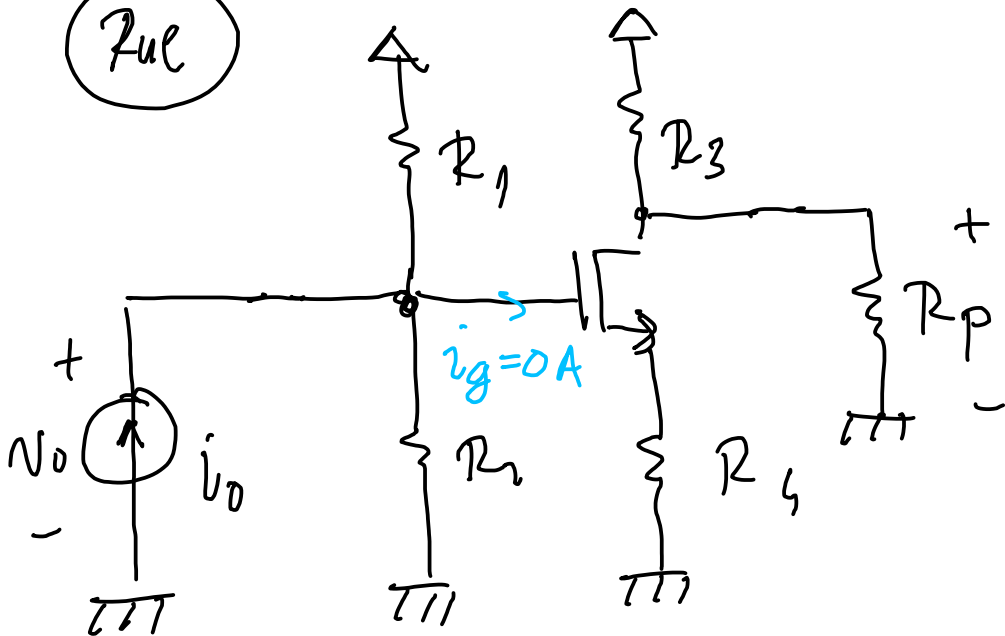

$$Z_{ul} = \frac{v_0}{i_0} = R_G \approx R_1 || R_2$$

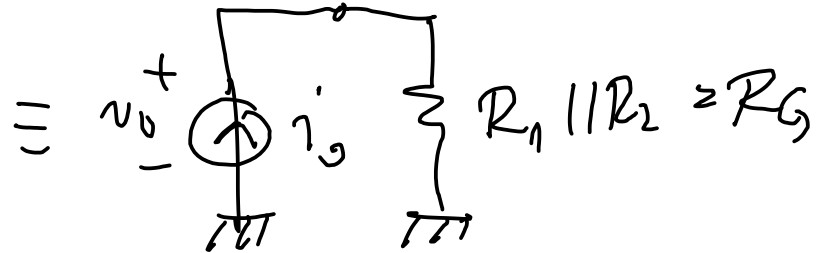

Z_{it}

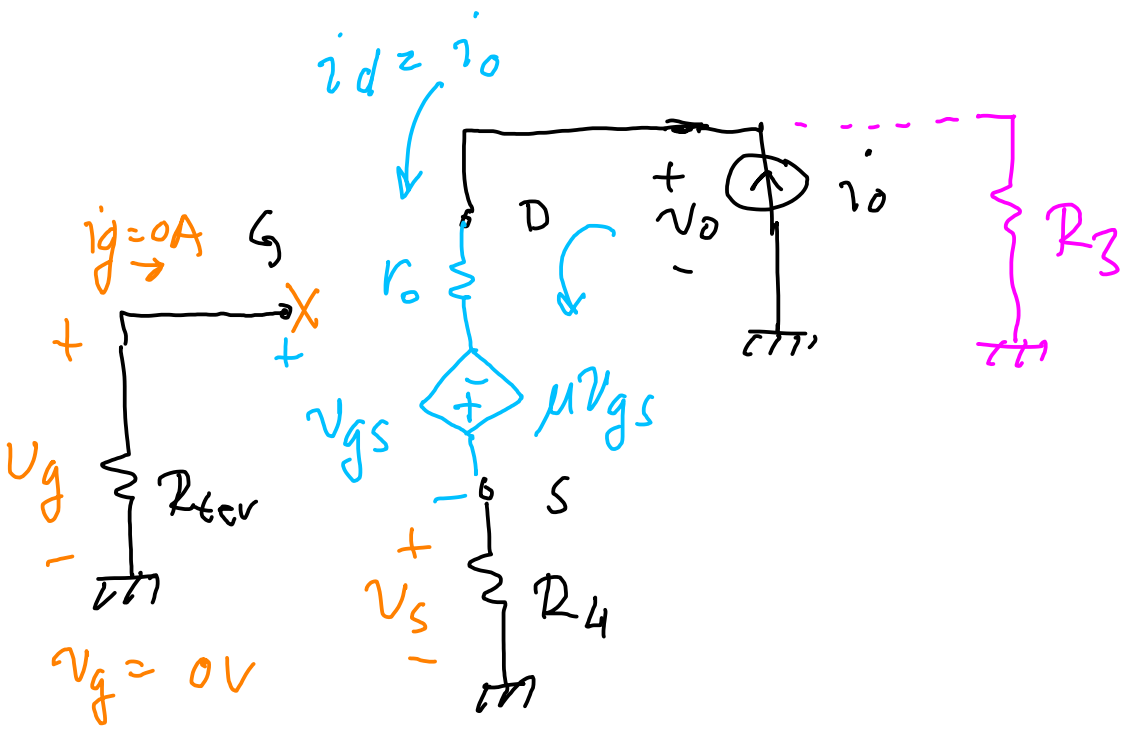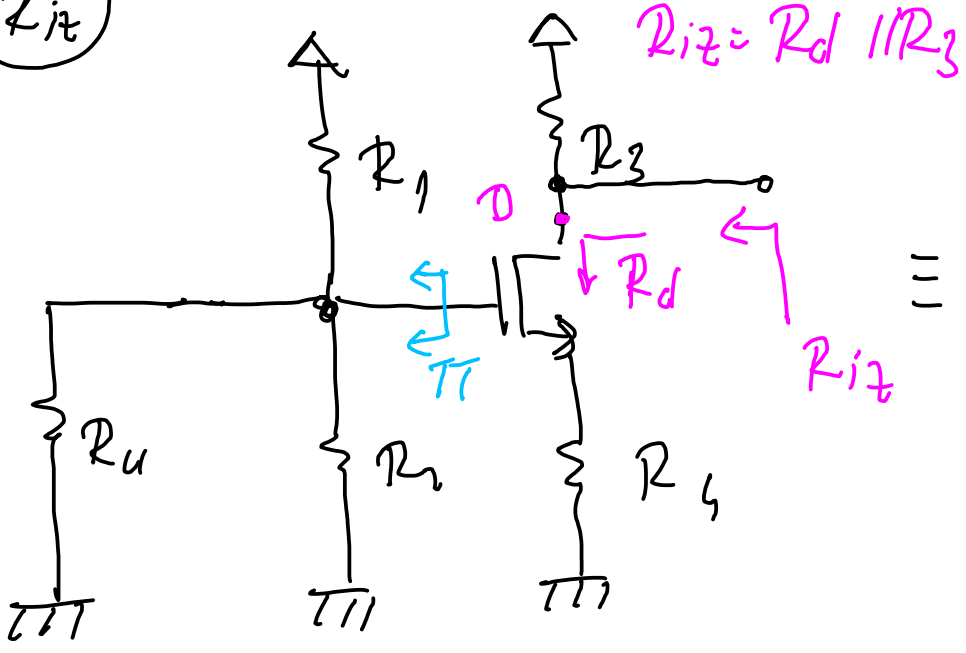


$$Z_{it} = R_d \parallel R_3$$

$$v_0 = i_0 \cdot r_0 - \mu v_{gs} + i_0 R_d$$


$$v_{gs} = v_g - v_s = -v_s = -i_0 R_4$$

$$v_0 = i_0 (r_0 + R_d) + \mu i_0 R_4$$

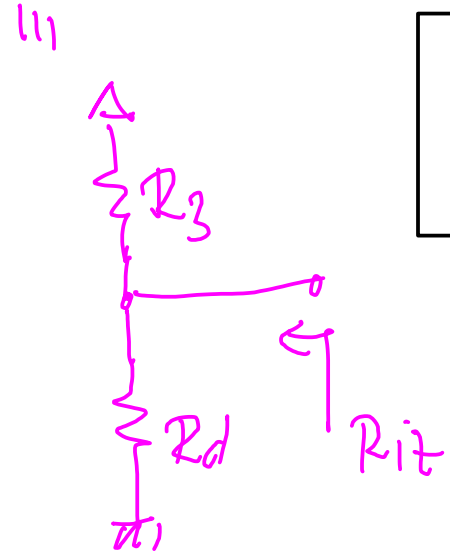
$$R_d = \frac{v_0}{i_0} = r_0 + (1 + \mu) R_4$$



R_s

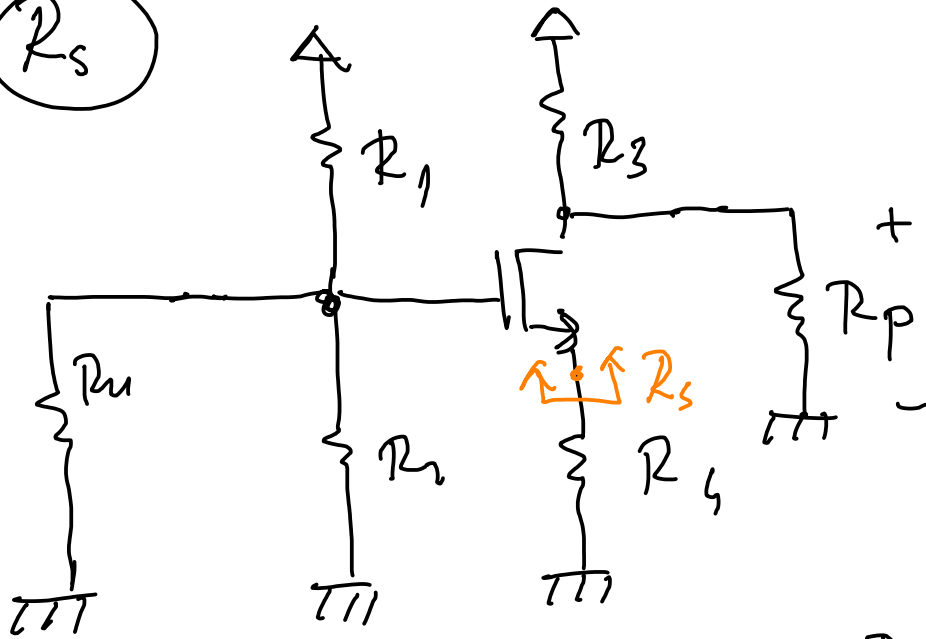
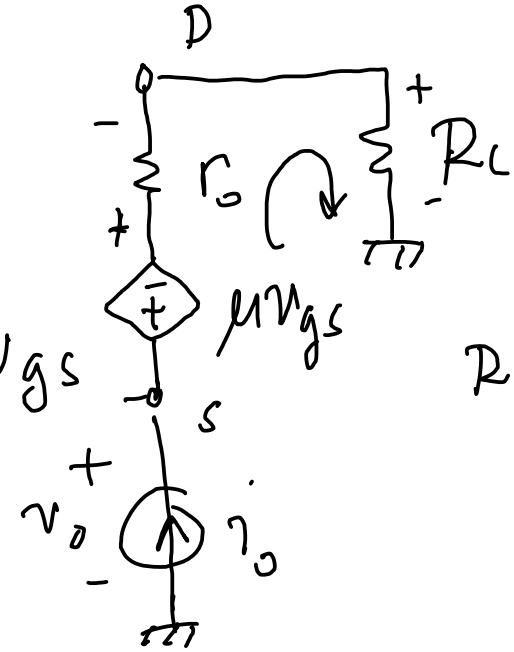
$$R_{teq} = R_4 \parallel R_2 \parallel R_m$$




$$R_L = R_3 \parallel R_p$$


$$v_o = \mu v_{gs} + i_o (r_o + R_L) \quad ; \quad v_{gs} = v_g - v_s = 0 - v_o$$

$$v_o = -\mu v_o + i_o (r_o + R_L) \Rightarrow$$
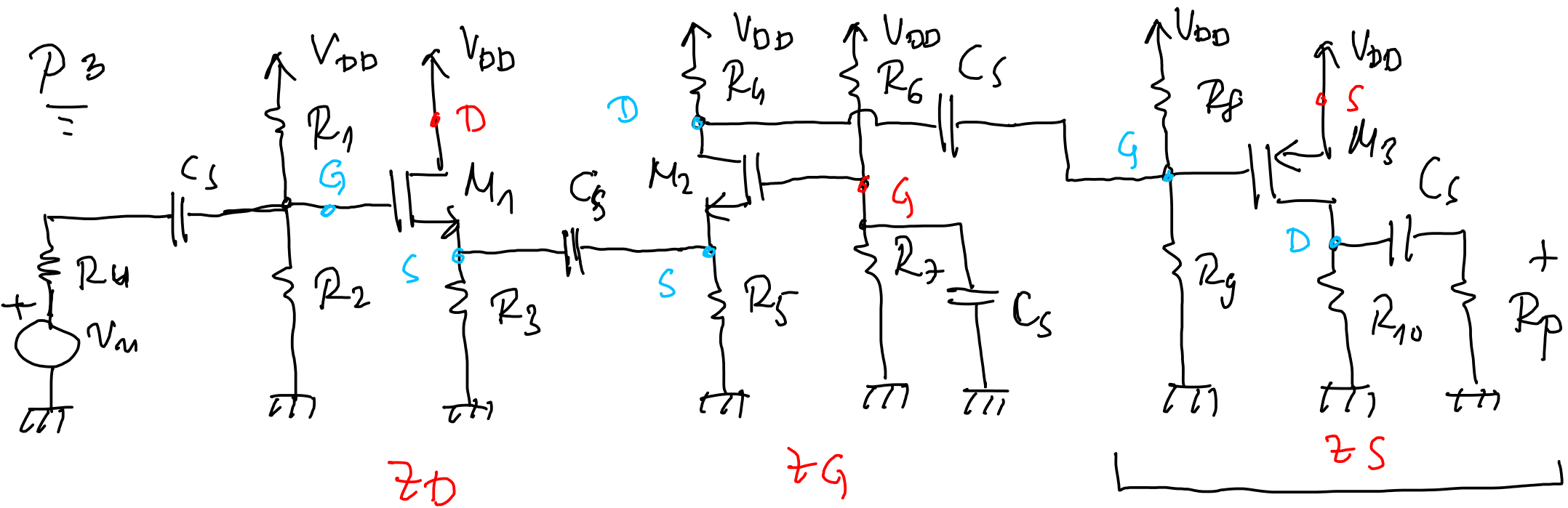
$$R_s = \frac{v_o}{i_o} = \frac{r_o + R_L}{1 + \mu}$$



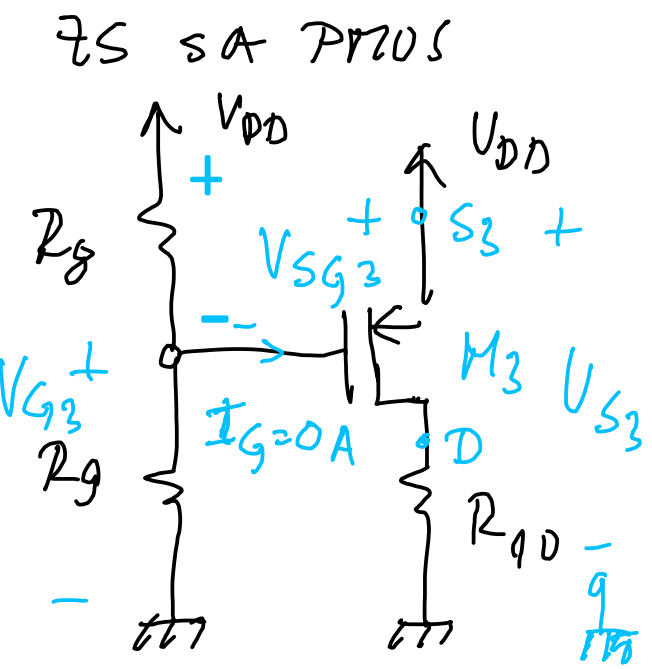НАПОМБЕНА : ЗА ДОМАЋИ УРАДИТИ DC ЗА Z_D ; Z_G




$$V_{G3} = \frac{R_f}{R_g + R_f} \cdot V_{DD} ; \quad V_{SD3} = V_{S3} - V_{G3}$$


$$= V_{DD} - \frac{R_g}{R_g + R_f} \cdot V_{DD}$$

$$V_{D3} = I_{D3} \cdot R_{L0}$$

$$I_{D3} = A_3 (V_{SD3} - |V_{th3}|)^2 \Leftrightarrow V_{SD3} = \frac{R_f}{R_f + R_g} \cdot V_{DD}$$

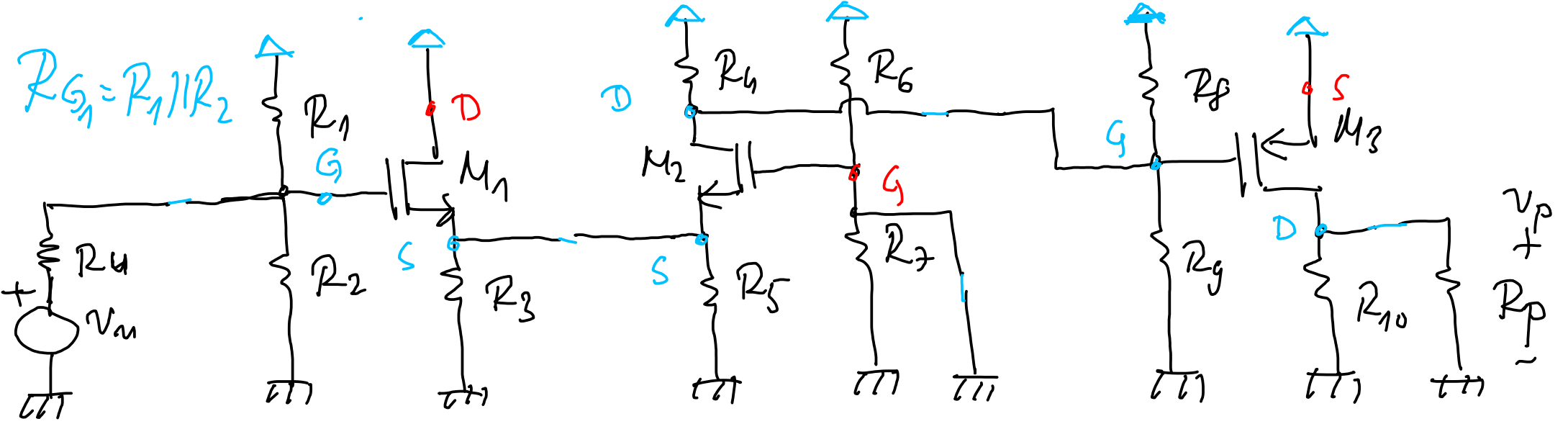

$$R_{G1} = R_1 || R_2$$

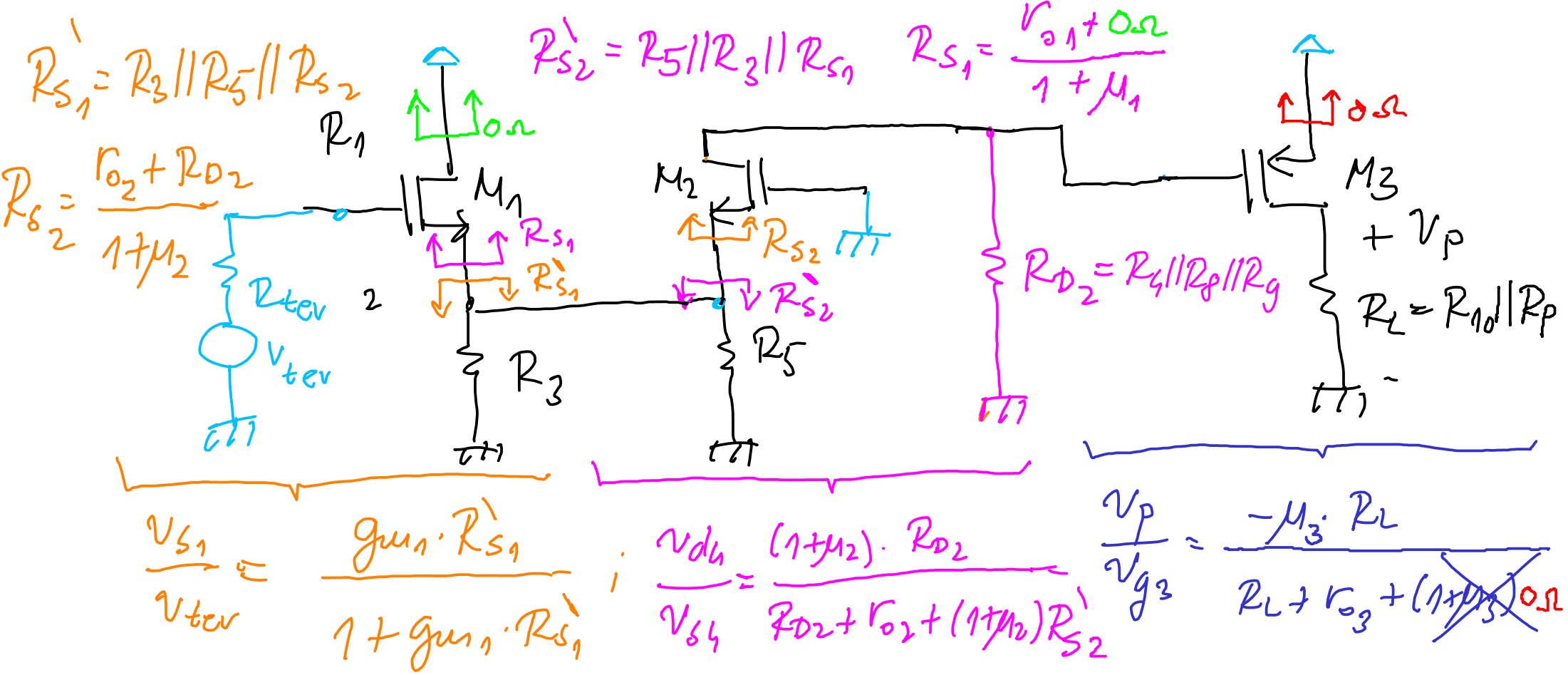

$$R_{S1}' = R_3 || R_5 || R_{S2}$$

$$R_{S2}' = R_5 || R_3 || R_{S1} \quad R_{S1} = \frac{r_{o1} + 0\Omega}{1 + \mu_1}$$

$$R_{S2} = \frac{r_{o2} + R_{D2}}{1 + \mu_2}$$

$$R_{D2} = R_4 || R_6 || R_g$$




$$R_L = R_{10} || R_p$$

$$\frac{V_{S1}}{V_{ter}} = \frac{g_{m1} \cdot R_{S1}'}{1 + g_{m1} \cdot R_{S1}'}$$

$$\frac{v_{d1}}{V_{S1}} = \frac{(1 + \mu_2) \cdot R_{D2}}{R_{D2} + r_{o2} + (1 + \mu_2) R_{S2}'}$$

$$\frac{V_p}{V_{g3}} = \frac{-\mu_3 \cdot R_L}{R_L + r_{o3} + (1 + \mu_3) 0\Omega}$$

70

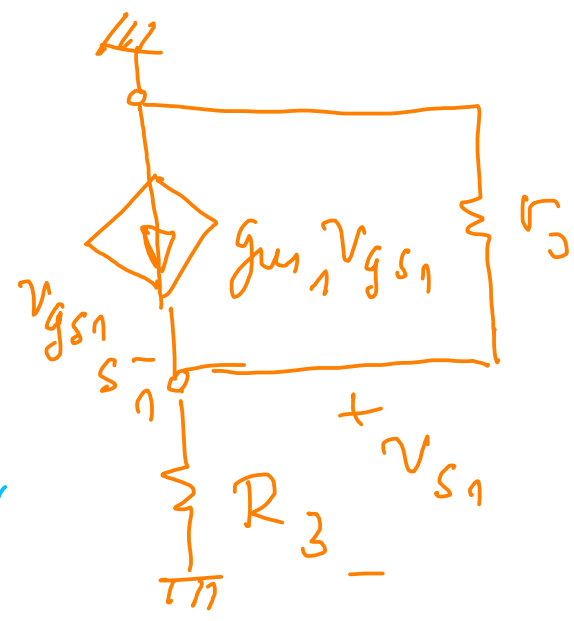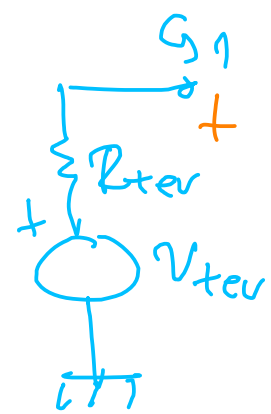
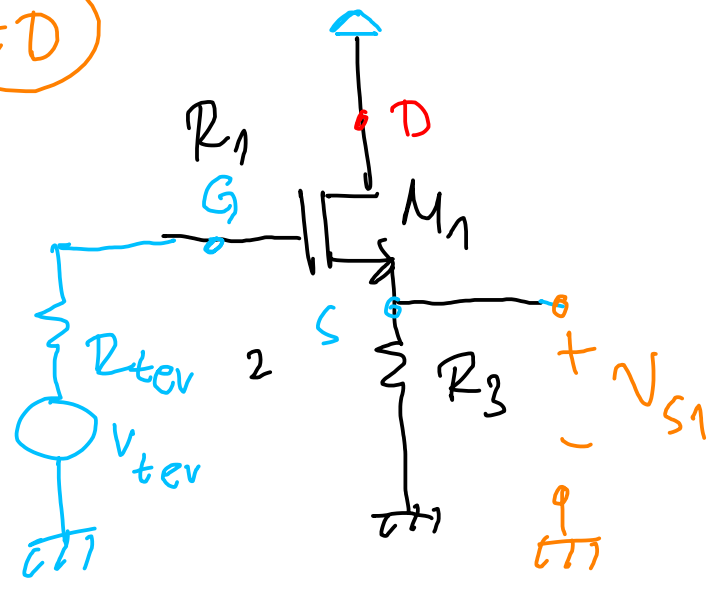


$$A_n' = \frac{V_{S1}}{V_{tev}} = \frac{g_{m1} R_L'}{1 + g_{m1} R_L'} \approx 1$$

$$V_{S1} = (g_{m1} \cdot V_{gs1}) \cdot R_L'$$

$$V_{gs1} = V_{g1} - V_{S1}$$
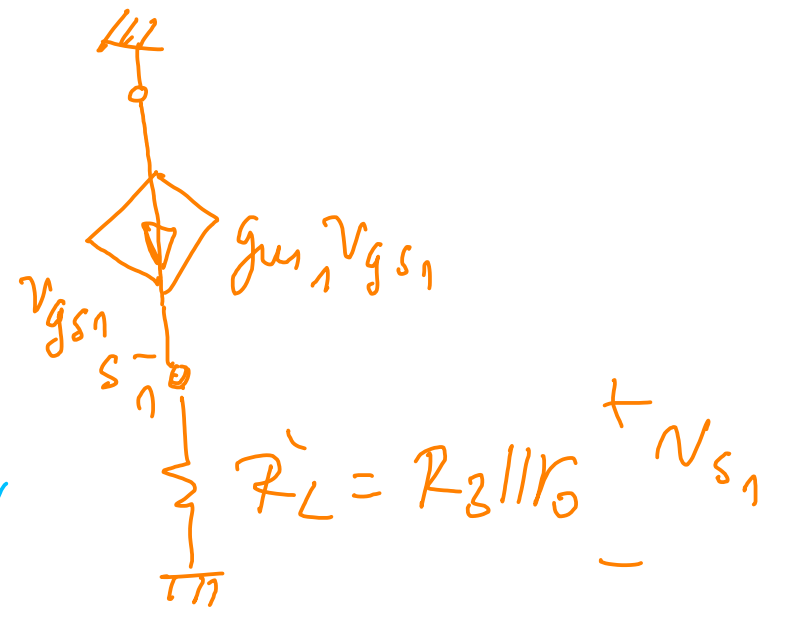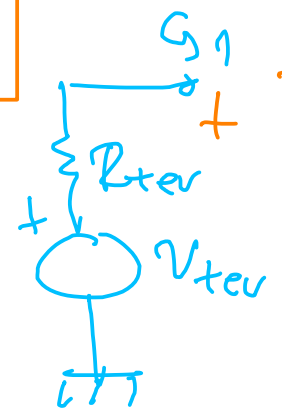
$$\approx V_{tev} - V_{S1} \Rightarrow V_{S1} = g_{m1} R_L' \cdot (V_{tev} - V_{S1})$$






$$A_u = \frac{V_{s1}}{V_{tev}} = \frac{g_{m1} R_L'}{1 + g_{m1} R_L'} = \frac{g_{m1}}{\frac{1}{R_L'} + g_{m1}} = \frac{g_{m1}}{\frac{1}{R_{o1}} + \frac{1}{R_3} + g_{m1} \parallel R_3}$$

$$A_u' = \frac{M_1 R_3}{R_3 + R_{o1} + M_1 \cdot R_3} = \frac{M_1 R_3}{R_{o1} + (1 + M_1) R_3}$$

$$A_u = \frac{V_{s1}}{V_{in}} = \frac{V_{s1}}{V_{tev}} \cdot \frac{V_{tev}}{V_u} = A_u' \cdot \frac{R_G}{R_G + R_u} \quad ; \quad R_G = R_1 \parallel R_2$$

ZG

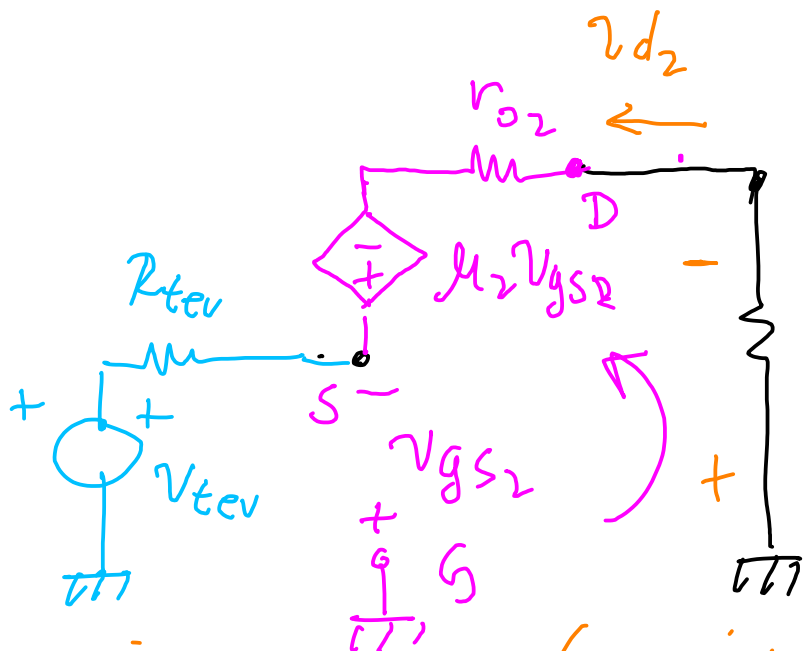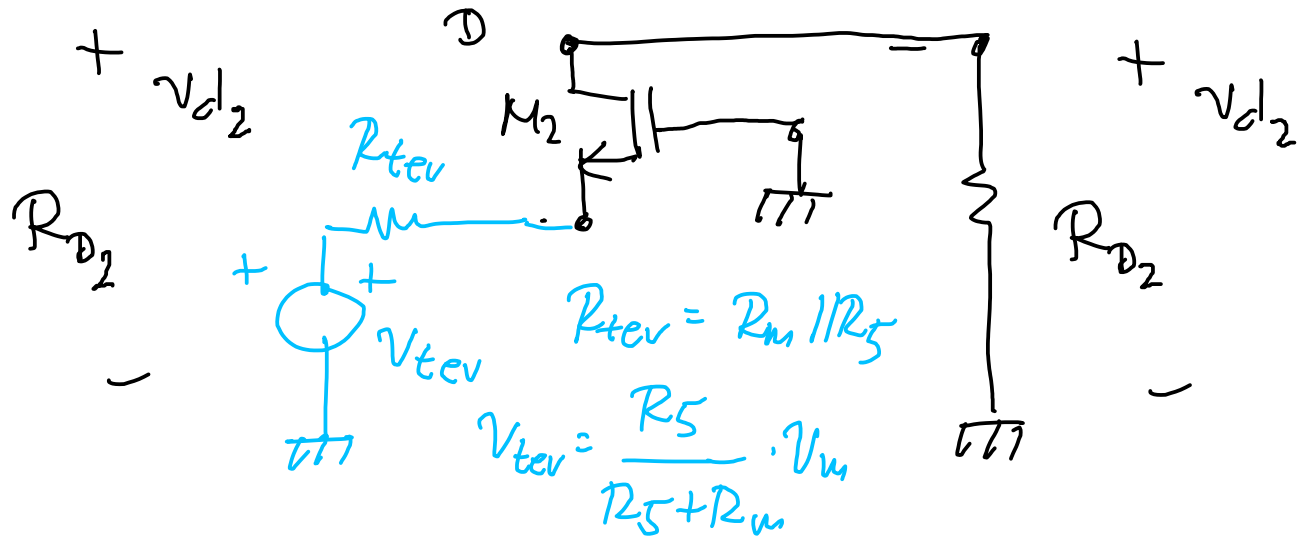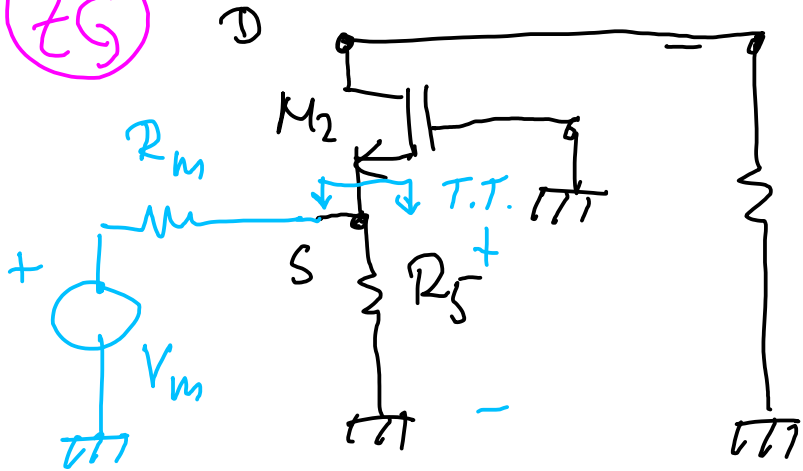

$$0 = i_{d2}(R_{D2} + r_{o2}) - \mu_2 V_{gs2}$$

$$+ i_{d2} R_{teq} + V_{teq}$$

$$V_{gs2} = 0 - (i_{d2} R_{teq} + V_{teq})$$

$$0 = \underline{i_{d2}} r_{o2} - \mu_2 (- \underline{i_{d2}} R_{teq} - V_{teq}) + \underline{i_{d2}} R_{teq} + V_{teq} + \underline{i_{d2}} R_{D2}$$


$$i_{d2} = \frac{-(1 + \mu_2) V_{teq}}{r_{o2} + (1 + \mu_2) R_{teq} + R_{D2}}$$

$$\Rightarrow v_{D2} = -i_{d2} \cdot R_{D2}$$

$$A_{v1} = \frac{v_{d2}}{v_{tecv}} = \frac{(1 + \mu_2) R_{D2}}{r_{o2} + R_{D2} + (1 + \mu_2) R_{tecv}}$$

$$A_v = \frac{v_{d2}}{v_m} = \frac{R_S}{R_S + R_m} \cdot A_{v1}$$
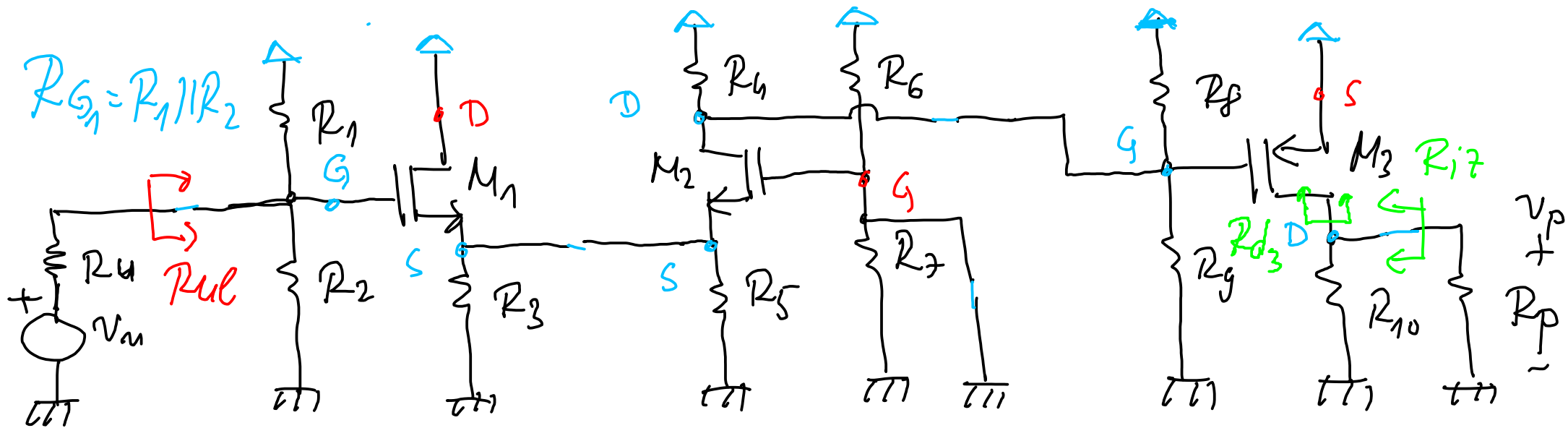
$$A_v = \frac{v_p}{v_m} = \frac{R_{G1}}{R_{G1} + R_u} \cdot \frac{g_{m1} \cdot R_{S1}}{1 + g_{m1} \cdot R_{S1}} \cdot \frac{(1 + \mu_2) \cdot R_{D2}}{R_{D2} + r_{o2} + (1 + \mu_2) R_{S2}} \cdot \frac{-\mu_3 \cdot R_L}{R_L + r_{o3}}$$



$$R_{ul} = R_1 \parallel R_2 = R_{G1}$$

$$R_{12} = R_{10} \parallel R_{d3}$$

$$R_{d3} = r_{o3} + (1 + \mu_3) \cdot r_{o3}$$