
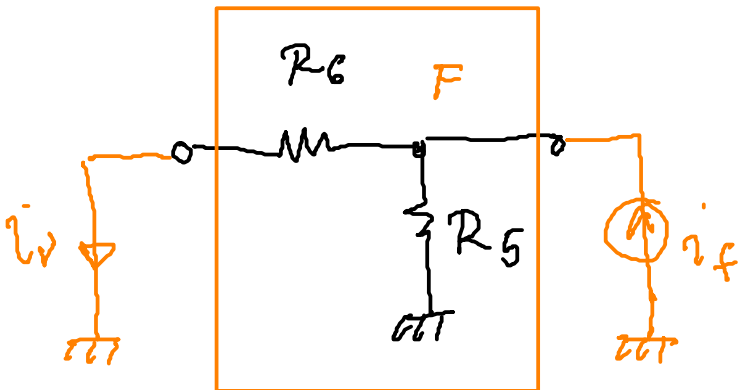


A → STRUJNO PODAČANJE

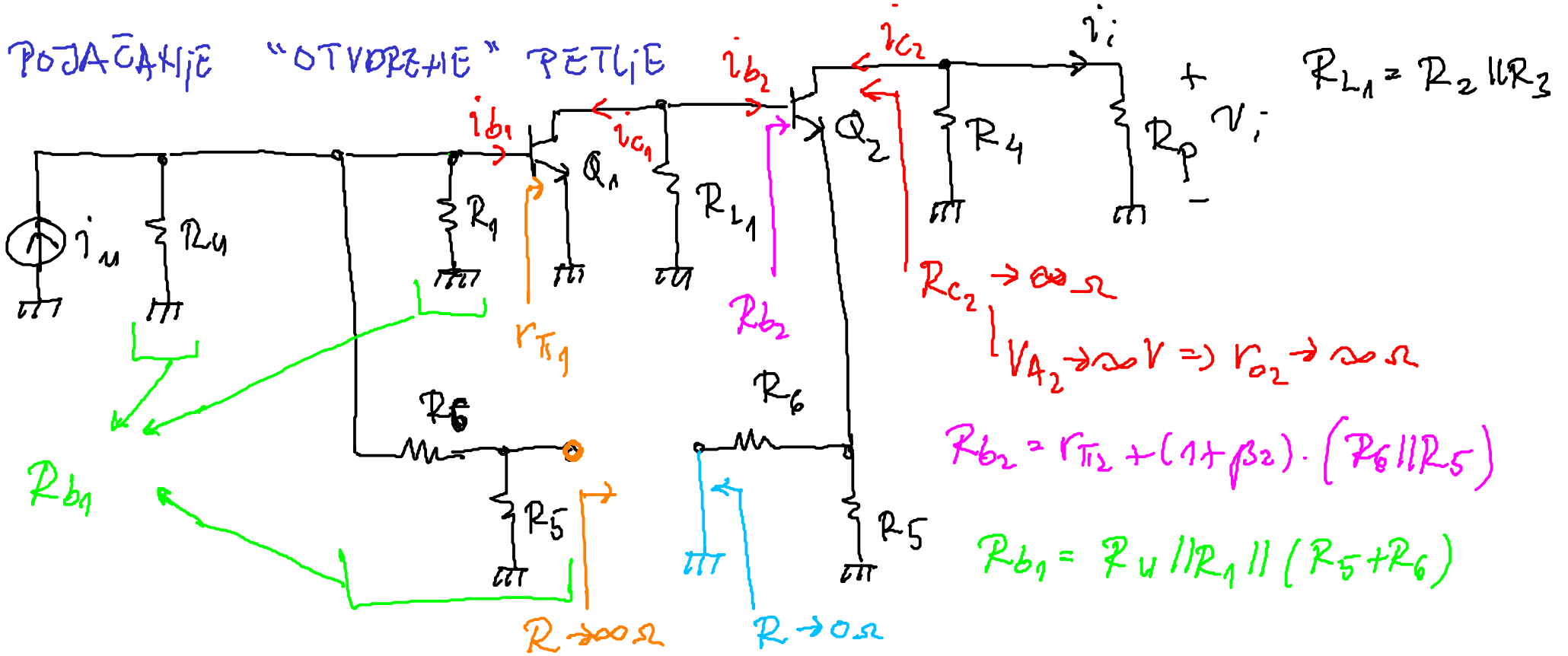

$$F = \frac{i_v}{i_f} = \frac{R_5}{R_5 + R_6}$$

POJAČAVNIJE "OTVORZHE" PETLIJE



$$A = \frac{i_i}{i_{in}} = \frac{i_i}{i_{c2}} \cdot \frac{i_{c2}}{i_{b2}} \cdot \frac{i_{b2}}{i_{c1}} \cdot \frac{i_{c1}}{i_{b1}} \cdot \frac{i_{b1}}{i_{in}} = - \frac{R_4}{R_4 + R_p} \cdot \beta_2 \cdot \left(- \frac{R_{L1}}{R_{L1} + R_{b2}} \right) \cdot \beta_1 \cdot \frac{R_{b1}}{R_{b1} + r_{\pi 1}} \quad [A/A]$$

$$A_f = \frac{A}{1 + A \cdot F}$$

$$R_{ue} = R_{b1} \parallel r_{\pi 1}$$


$$R_{ulr} = R_{ue} / (1 + A \cdot F) \Rightarrow R_{ulr,amp} = \frac{1}{G_{ulr,amp}}$$

$$R_{ulr,amp} = \frac{1}{G_{ulr,amp}}$$

$$G_{ulr,amp} = G_{ulr} - G_u$$

$\frac{1}{R_{ulr}}$ $\frac{1}{R_u}$
 \uparrow \uparrow

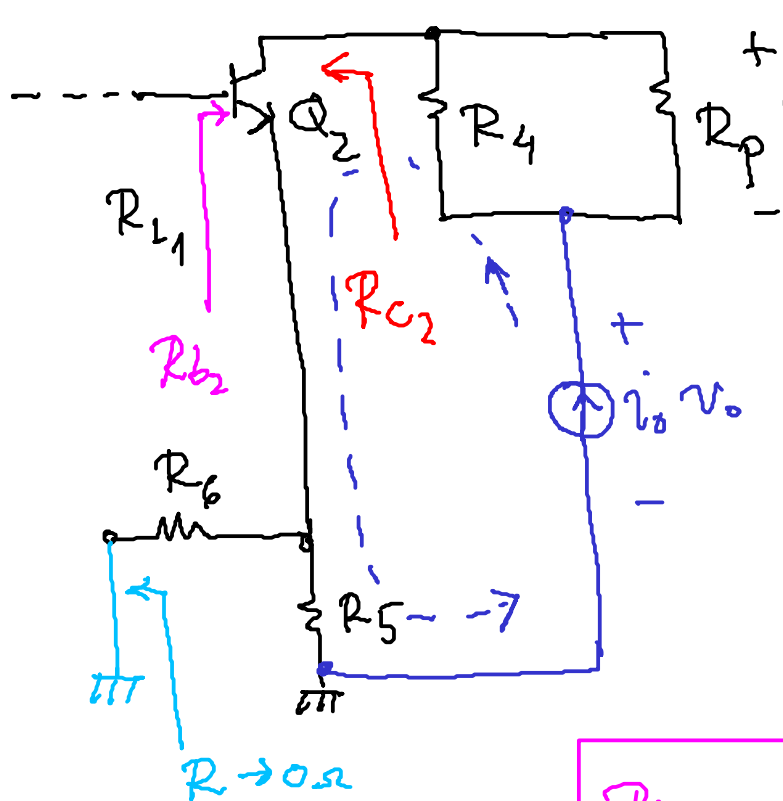• KOD PREDNE (STRUJNE) SPREGE R_{ek} JE ODPORNOST KONTIŽURE!



$$R_{L1} = R_2 \parallel R_3$$

$$R_{ek} = \frac{v_0}{i_0} \equiv R_{iz}$$

$$R_{c2} \rightarrow \infty \Omega$$

$$V_{A2} \rightarrow \infty V \Rightarrow r_{o2} \rightarrow \infty \Omega$$

$$R_{b2} = r_{\pi 2} + (1 + \beta_2) \cdot (R_6 \parallel R_5)$$

$$R_{ek} = (R_4 \parallel R_p) + R_{c2}$$

$$R_{b1} = R_u \parallel R_1 \parallel (R_5 + R_6)$$

$$R_{ek} \rightarrow \infty \Omega \Rightarrow R_{iz} \rightarrow \infty \Omega$$

$$R_{izr} = R_{iz} (1 + AF) \rightarrow \infty \Omega$$





$$R_{izr,amp} = R_{izr} - R_p \rightarrow \infty \Omega$$

* AKO BI SE TRA ŽILO LAPOLISKO POJAČAČIJE SA REAKCIJOM:

$$A_{r,n} = \frac{v_i}{v_u} = \frac{v_i}{i_i} \cdot \frac{i_i}{i_u} \cdot \frac{i_u}{v_u} = \left(\frac{v_i}{i_i} \right) \cdot A_r \cdot \left(\frac{i_u}{v_u} \right)$$

ODREDITI IZ KOLA.

P_2 "Colpitts" LC OSCILLATOR

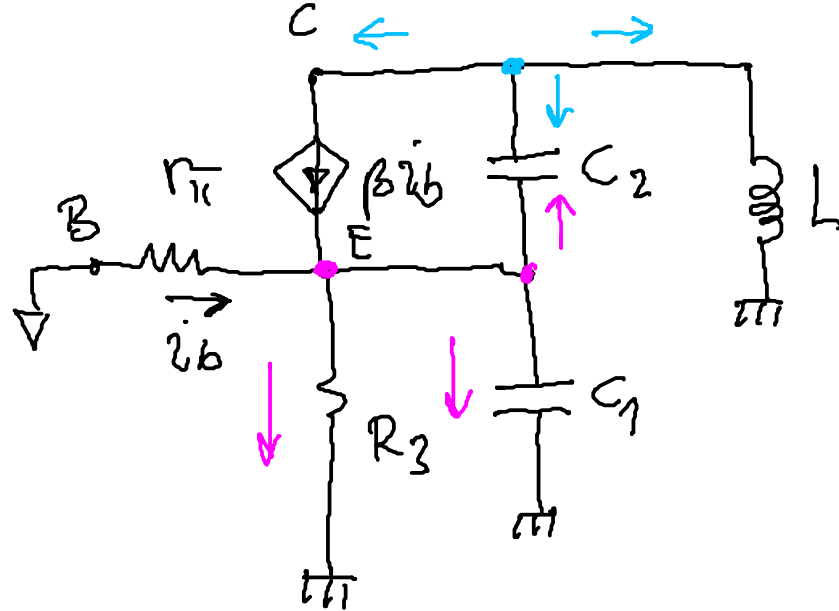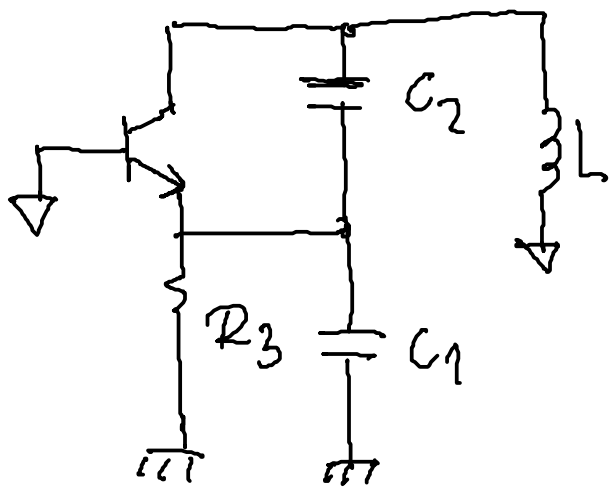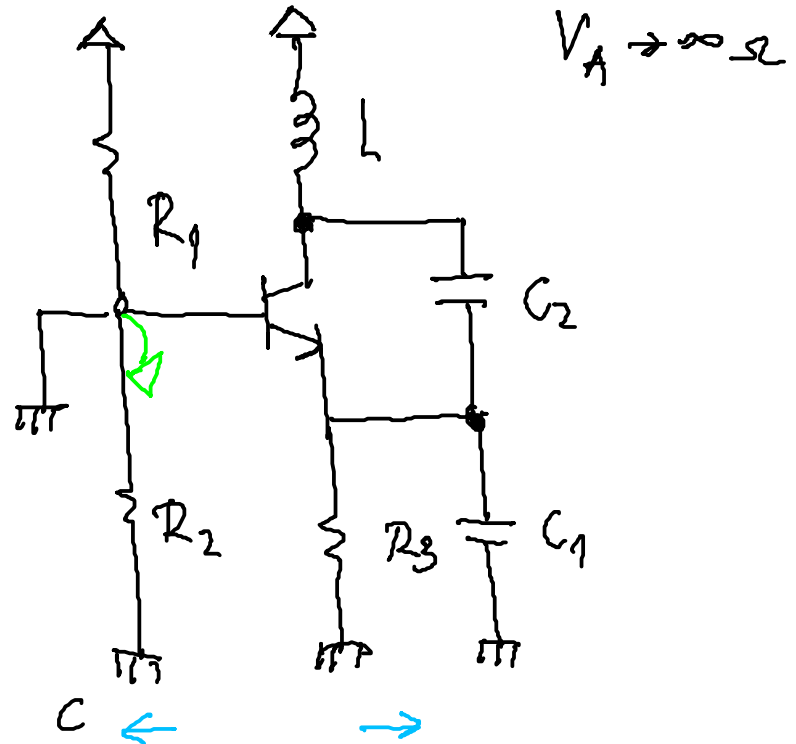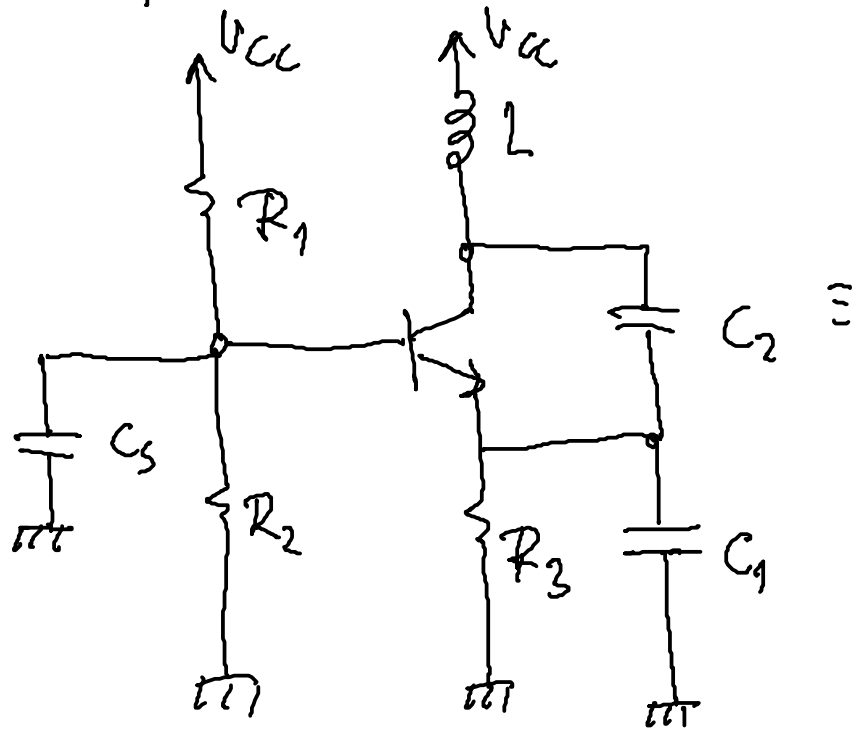

$$\textcircled{C} \beta i_b + (v_c - v_e) \cdot sC_2 + v_c / sL = 0$$

$$\textcircled{E} -(1+\beta) i_b + (v_e - v_c) \cdot sC_2 + v_e / R_3 + v_e \cdot sC_1 = 0$$

$$\textcircled{HJ} i_b = -v_e / r_{\pi} \uparrow$$

$$\textcircled{C} v_c \left[-sC_2 - \frac{\beta}{r_{\pi}} \right] + v_c \left[sC_2 + \frac{1}{sL} \right] = 0 \quad * \beta = r_{\pi} \cdot g_m$$

$$\textcircled{E} v_e \left[sC_2 + \frac{1}{R_3} + sC_1 + \frac{(1+\beta)}{r_{\pi}} \right] + v_c \left[-sC_2 \right] = 0$$

$$\Delta = \begin{vmatrix} -(sC_2 + g_m) & sC_2 + \frac{1}{sL} \\ s(C_1 + C_2) + \frac{1}{R_3} + \frac{1}{r_{\pi}} + g_m & -sC_2 \end{vmatrix} \stackrel{\Delta}{=} 0 \Rightarrow \begin{matrix} \text{Re}\{\Delta\} = 0 \\ \text{Im}\{\Delta\} = 0 \end{matrix}$$

$B = 1$

$$s C_2 (s C_2 + g_m) - \left(s C_2 + \frac{1}{s L} \right) \cdot \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} + g_m + s (C_1 + C_2) \right) = 0$$

$$s^2 \left[C_2^2 - C_2 (C_1 + C_2) \right] - s \left[-g_m C_2 + C_2 \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} + g_m \right) \right]$$

$$- \frac{1}{s} \cdot \frac{1}{L} \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} + g_m \right) - \frac{C_1 + C_2}{L} = 0 \quad / \cdot s$$

$$s^3 \left[-C_2 C_1 \right] - s^2 \left[C_2 \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} \right) \right] - s \frac{C_1 + C_2}{L} - \frac{1}{L} \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} + g_m \right) = 0$$

$$\operatorname{Re} \{ \Delta \} = \omega_0^2 C_2 \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} \right) - \frac{1}{L} \left(\frac{1}{R_3} + \frac{1}{R_{\pi}} + g_m \right) = 0$$

$$\operatorname{Im} \{ \Delta \} = -\omega_0 \frac{C_1 + C_2}{L} + \omega_0 C_2 C_1 = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{L C_{eq}}} ; C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi} \cdot \frac{1}{\sqrt{L C_{eq}}}$$

FREKVENCIA
OSCILOVANJA

$$\omega_0^2 C_2 \left(\frac{1}{R_3} + \frac{1}{r_{\pi}} \right) - \frac{1}{L} \left(\frac{1}{R_2} + \frac{1}{r_{\pi}} + g_m \right) = 0$$

$$\frac{1}{\cancel{L} \cdot \frac{C_1 C_2}{C_1 + C_2}} \cdot \cancel{L}^2 \left(\frac{1}{R_3} + \frac{1}{r_{\pi}} \right) = \frac{1}{\cancel{L}} \left(\frac{1}{R_2} + \frac{1}{r_{\pi}} + g_m \right)$$

$$\left(1 + \frac{C_2}{C_1} \right) \left(\frac{1}{R_3} + \frac{1}{r_{\pi}} \right) = g_m + \left(\frac{1}{R_2} + \frac{1}{r_{\pi}} \right) \quad \left\{ \text{USLOV OSCILOVANJA} \right.$$

$$g_m = \frac{C_2}{C_1} \cdot \left(\frac{1}{R_2} + \frac{1}{r_{\pi}} \right) \Rightarrow \frac{C_2}{C_1} \cdot \frac{1}{R_2 \parallel r_{\pi}}$$

$$g_m = \frac{V_T}{I_C} \rightarrow \frac{kT}{2} \approx 25 \text{ mV} \quad @ \quad T = 300 \text{ K}$$

POLARIZACIJA (VREDNOSTI ODPORNIKA)