

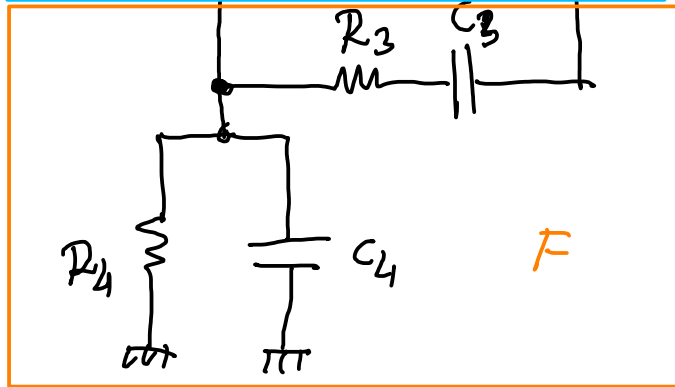
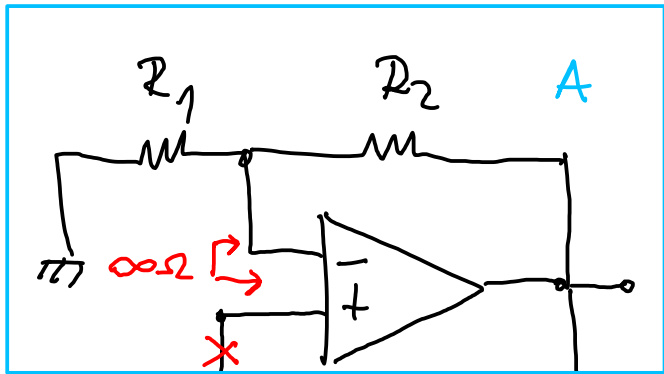


P_{11}

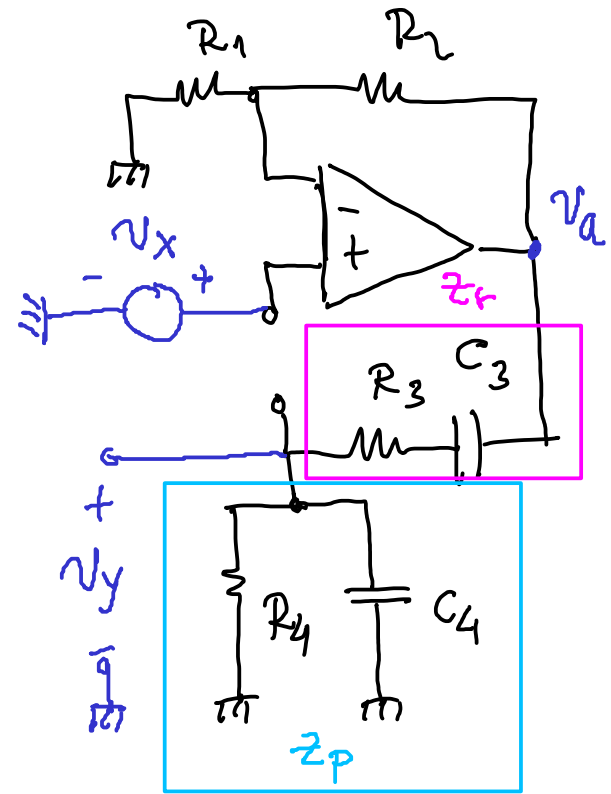

V_{osc}

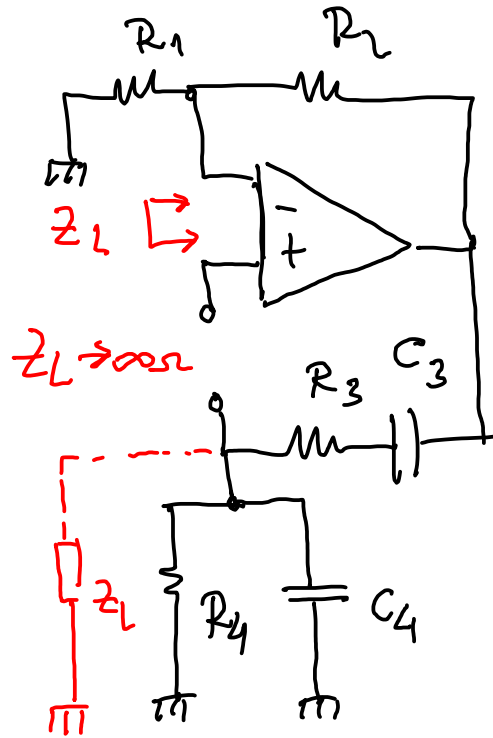

$$B = A \cdot F = \frac{V_y}{V_x} = \frac{V_y}{V_a} \cdot \frac{V_a}{V_x} = \frac{Z_p}{Z_p + Z_r} \cdot k, \quad k = 1 + R_2/R_1$$

$$B = \frac{\frac{R_4}{1 + sC_4 R_4}}{\frac{R_4}{1 + sC_4 R_4} + \frac{1 + sC_2 R_3}{sC_3}} \cdot k = \frac{k \cdot sC_2 R_4}{sC_2 R_4 + (1 + sC_2 R_3)(1 + sC_4 R_4)}$$

$$B = \frac{k \cdot s C_3 R_4}{1 + s [C_3 (R_4 + R_2) + C_4 R_4] + s^2 C_2 R_3 C_4 R_4} = 1$$

$$1 + s [C_3 (R_4 (1-k) + R_2) + C_4 R_4] + s^2 C_2 R_3 C_4 R_4 = 0$$

$$s = j\omega_0$$

$$\text{Re: } 1 - \omega_0^2 C_2 R_3 C_4 R_4 = 0 \Rightarrow$$

$$\omega_0 = \frac{1}{\sqrt{C_2 R_3 C_4 R_4}}, \quad f_0 = \frac{\omega_0}{2\pi} \quad [\#7]$$


$$\text{Im: } \omega_0 [C_3 (R_4 (1-k) + R_2) + C_4 R_4] = 0$$

$$C_3 R_4 - C_3 R_4 k + C_3 R_3 + C_4 R_4 = 0$$


$$k = \frac{C_3 (R_4 + R_3) + C_4 R_4}{C_3 R_4} = 1 + \frac{R_3}{R_4} + \frac{C_4}{C_3} \quad ; \quad k = 1 + \frac{R_2}{R_4}$$

$$1 + \frac{R_2}{R_4} = 1 + \frac{R_3}{R_4} + \frac{C_4}{C_3} \Rightarrow$$
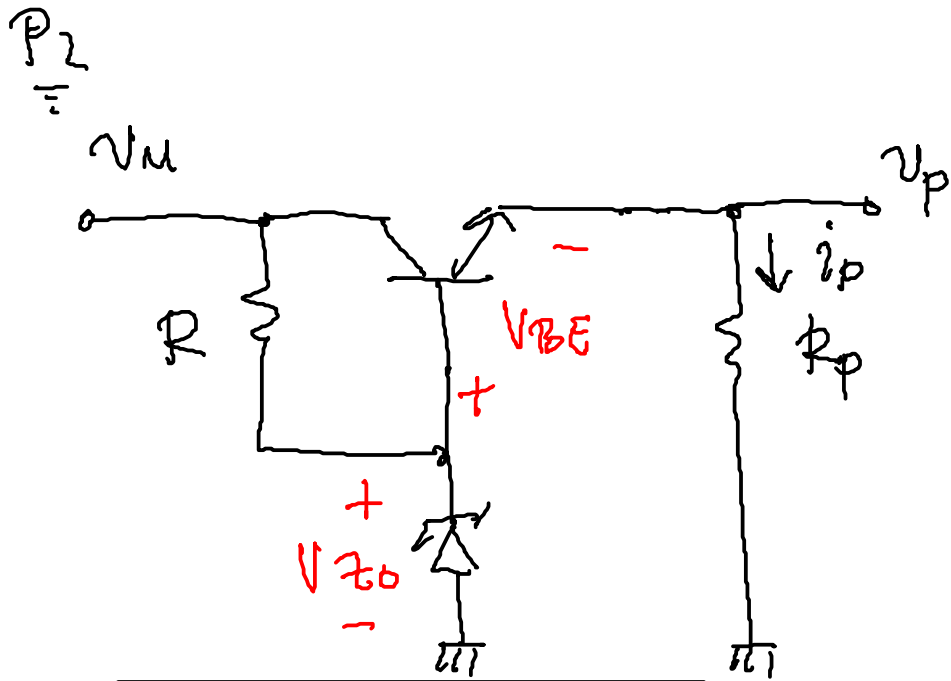
$$\frac{R_2}{R_4} = \frac{R_3}{R_4} + \frac{C_4}{C_3}$$




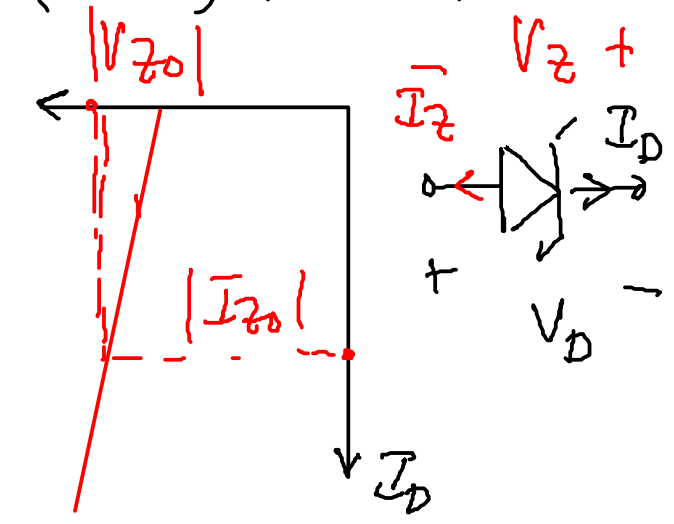a) DC НАРОН НА ИЗЛАТУ, V_p
 $(\beta \gg 1)$, $V_{z0} = (3-12)V$, $R_{z0} \approx (10-20)\Omega$



a) $V_p = V_{z0} - V_{BE}$

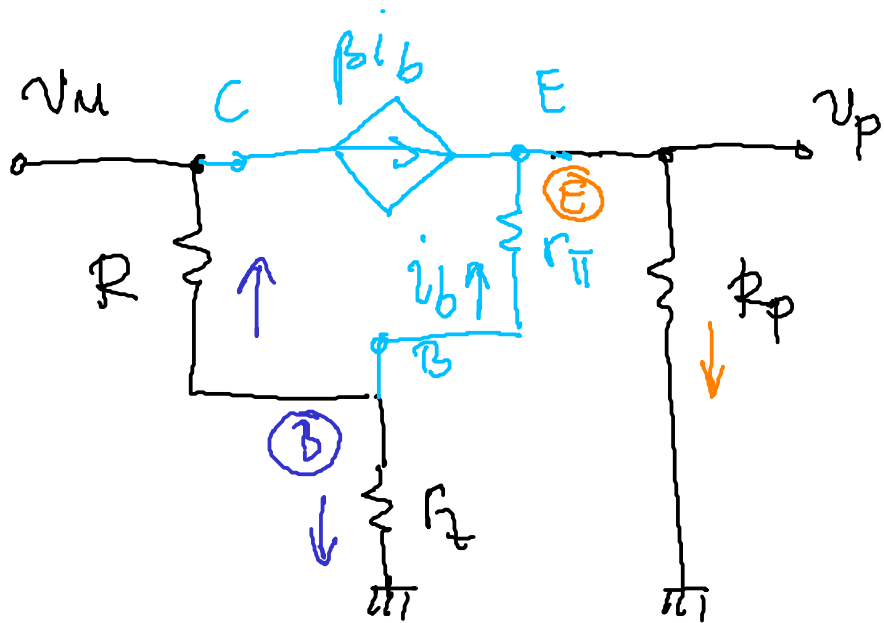b) $S_V = \frac{v_p}{v_u}$ (АНАЛИЗА МАЛИХ СИГНАЛА - AC)



$$\textcircled{B} \quad \frac{v_b - v_M}{R} + \frac{v_b}{r_E} + i_b = 0$$

$$\textcircled{E} \quad \frac{v_p}{R_P} - (1 + \beta) i_b = 0$$

$$\textcircled{HJ} \quad v_b = \frac{v_b - v_p}{r_{\pi}}$$

$$\begin{bmatrix} \frac{1}{R} + \frac{1}{r_E} + \frac{1}{r_{\pi}} & -\frac{1}{r_{\pi}} \\ -\frac{(1+\beta)}{r_{\pi}} & \frac{1}{R_P} + \frac{(1+\beta)}{r_{\pi}} \end{bmatrix} \begin{bmatrix} v_b \\ v_p \end{bmatrix} = \begin{bmatrix} \frac{v_M}{R} \\ 0 \end{bmatrix}$$

$$S_V = \frac{v_p}{v_M} = \frac{\Delta v_p}{\Delta} \cdot \frac{1}{v_M}$$

$$\Delta V_p = \begin{vmatrix} \frac{1}{R} + \frac{1}{r_z} + \frac{1}{r_{\pi}} & \frac{v_u}{R} \\ -\frac{(1+\beta)}{r_{\pi}} & 0 \end{vmatrix} = \frac{(1+\beta)v_u}{r_{\pi} \cdot R}$$


$$\Delta = \begin{vmatrix} \frac{1}{R} + \frac{1}{r_z} + \frac{1}{r_{\pi}} & -\frac{1}{r_{\pi}} \\ -\frac{(1+\beta)}{r_{\pi}} & \frac{1}{R_p} + \frac{(1+\beta)}{r_{\pi}} \end{vmatrix} = \left(\frac{1}{R} + \frac{1}{r_z} + \frac{1}{r_{\pi}} \right) \left(\frac{1}{R_p} + \frac{(1+\beta)}{r_{\pi}} \right) - \frac{(1+\beta)}{r_{\pi}^2}$$

$$S_v = \frac{\frac{(1+\beta)}{r_{\pi} R}}{\frac{(1+\beta)}{r_{\pi} R} = \frac{\left(\frac{1}{R} + \frac{1}{r_z} + \frac{1}{r_{\pi}} \right) \left(\frac{1}{R_p} + \frac{(1+\beta)}{r_{\pi}} \right) - \frac{(1+\beta)}{r_{\pi}^2} \left(\frac{1}{R} + \frac{1}{r_z} \right) \frac{(1+\beta)}{r_u} + \frac{1}{R_p} \left(\frac{1}{R} + \frac{1}{r_z} + \frac{1}{r_{\pi}} \right)}$$

$$\lim_{r_z \rightarrow 0} S_V = \frac{(1+\beta) / (r_{\pi} \cdot R)}{\frac{(1+\beta)}{r_{\pi}} \cdot \frac{1}{r_z} + \frac{1}{R_p} \cdot \frac{1}{r_z}} = r_z \cdot \frac{(1+\beta)}{R + r_{\pi} \frac{R}{R_p}}$$

$$\approx \frac{(1+\beta) r_z}{R (1 + r_{\pi}/R_p)} = \frac{R_p}{R_p + r_{\pi}} \cdot (1+\beta) \cdot \frac{r_z}{R} \quad \left| \quad r_z \ll \{R_p, r_{\pi}, R\}\right.$$

c) R_{iz} (ANALIZA MALIH SIGNALA - AC)

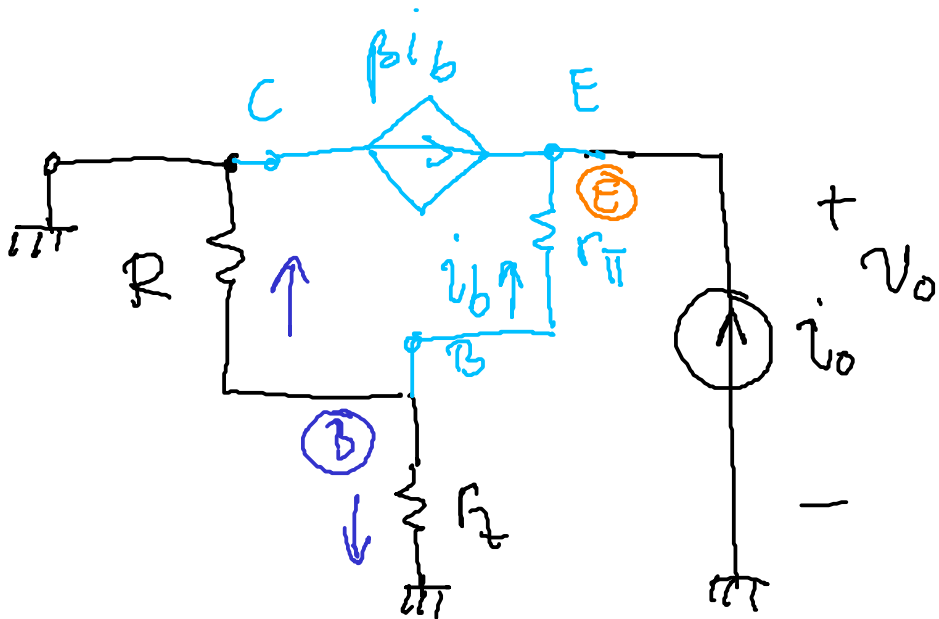

$$R_{iz} = \frac{v_o}{i_o}$$

$$\textcircled{E} \quad (1+\beta) i_b + i_o = 0$$

$$\textcircled{B} \quad v_b \left(\frac{1}{R} + \frac{1}{R_z} \right) + i_b = 0$$


$$\textcircled{HJ} \quad i_b = \frac{v_b - v_o}{r_{\pi}} \quad \rightarrow \quad \frac{1}{R \parallel R_z}$$

$$\begin{bmatrix} \frac{(1+\beta)}{r_{\pi}} & -\frac{(1+\beta)}{r_{\pi}} \\ \frac{1}{R_{11}r_2} + \frac{1}{r_{\pi}} & -\frac{1}{r_{\pi}} \end{bmatrix} \begin{bmatrix} v_b \\ v_o \end{bmatrix} = \begin{bmatrix} -i_o \\ 0 \end{bmatrix} \quad R_{11} = \frac{v_o}{i_o} = \frac{\Delta v_o}{\Delta i_o}$$

$$\Delta v_o = \begin{vmatrix} \frac{(1+\beta)}{r_{\pi}} & -i_o \\ \frac{1}{R_{11}r_2} + \frac{1}{r_{\pi}} & 0 \end{vmatrix} = i_o \left(\frac{1}{R_{11}r_2} + \frac{1}{r_{\pi}} \right)$$

$$\Delta = \begin{vmatrix} \frac{(1+\beta)}{r_{\pi}} & -\frac{(1+\beta)}{r_{\pi}} \\ \frac{1}{R_{11}r_2} + \frac{1}{r_{\pi}} & -\frac{1}{r_{\pi}} \end{vmatrix} = -\frac{(1+\beta)}{r_{\pi}^2} + \frac{(1+\beta)}{R_{11}r_2 r_{\pi}}$$

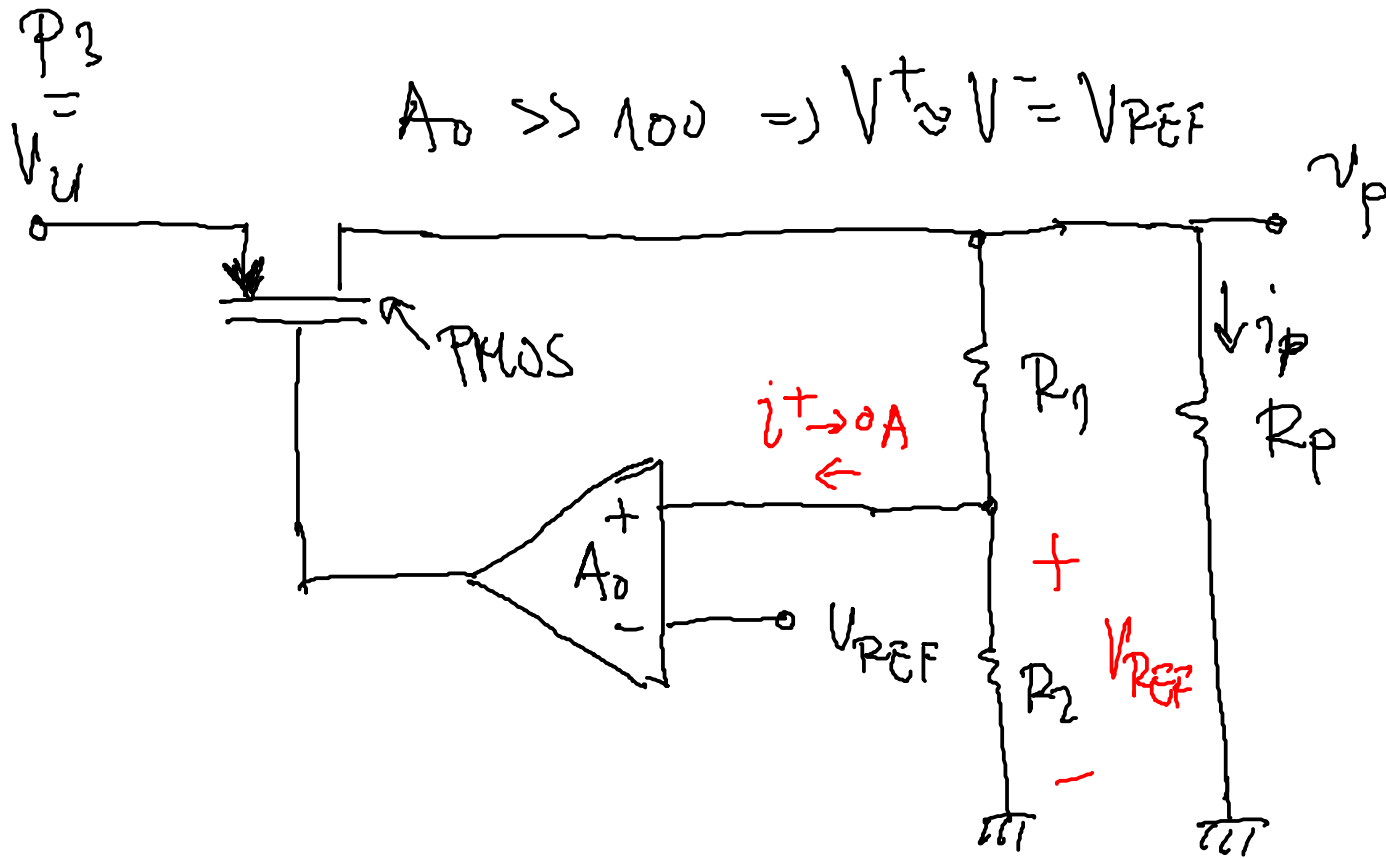
$$R_{iZ} = \left(\frac{1}{R_1 \parallel R_2} + \frac{1}{r_{\pi}} \right) / \frac{(1+\beta) \cdot 1}{R_1 \parallel R_2 \cdot r_{\pi}} = \frac{r_{\pi} + R_1 \parallel R_2}{(1+\beta)}$$



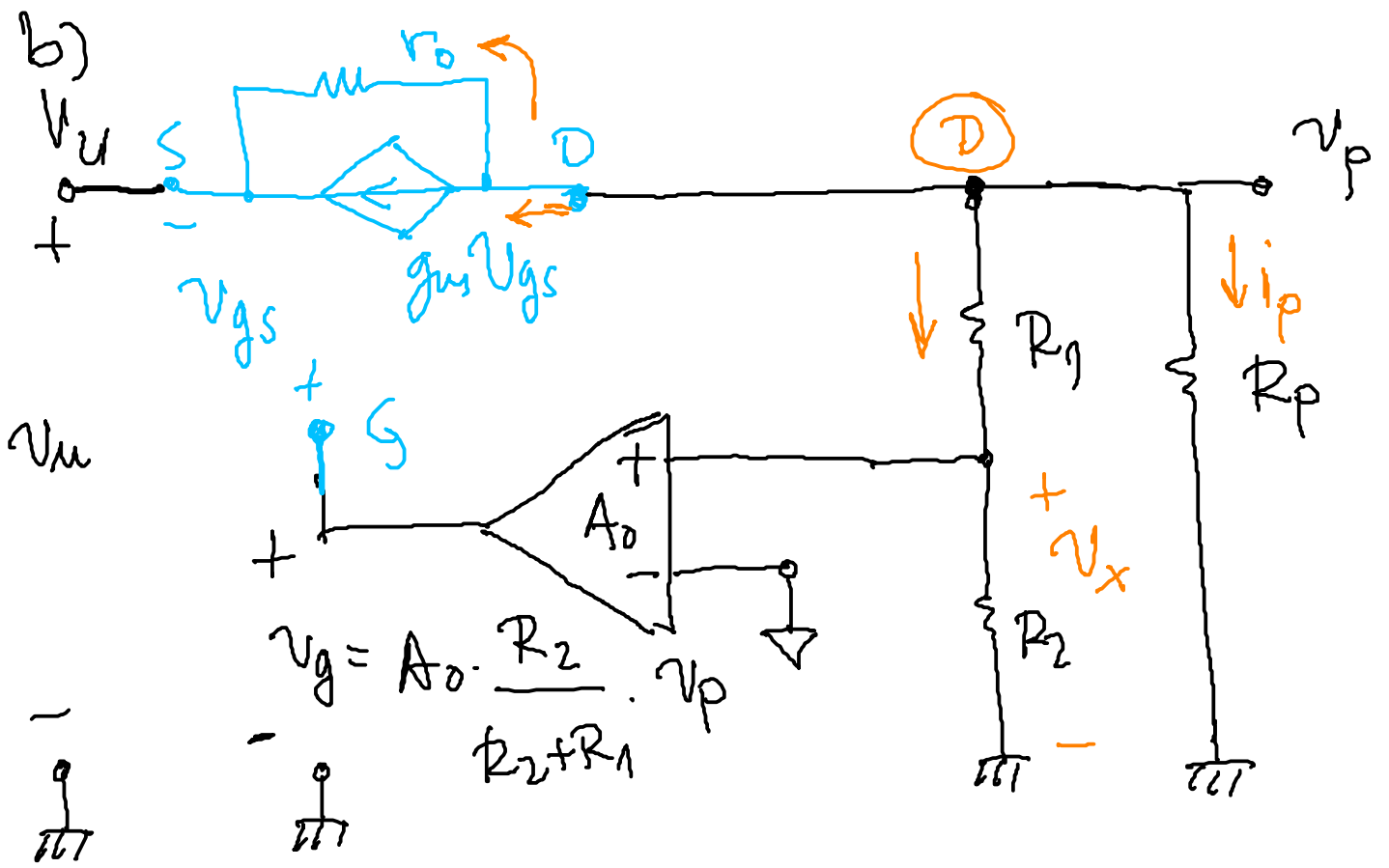a) DC НАПОН НА
ИЗЛАЗУ.

$$V_p = \left(1 + \frac{R_1}{R_2} \right) V_{REF}$$

$$V_{REF} = \frac{R_2}{R_2 + R_1} \cdot V_p$$



$$S_v = \frac{v_p}{v_u}$$

$$v_x = \frac{R_2}{R_2 + R_1} \cdot v_p$$

$$v_g = A_0 \cdot v_x$$

$$v_s = v_m$$


ⓓ
$$g_m v_{gs} + \frac{v_p - v_x}{R_1} + \frac{v_p}{R_p} + \frac{v_p - v_m}{r_o} = 0$$

$$g_m \left(A_0 \frac{R_2}{R_2 + R_1} \cdot v_p - v_m \right) + v_p \left(\frac{1}{R_1} + \frac{1}{R_p} + \frac{R_2}{R_2 + R_1} \cdot \left(\frac{1}{R_1} + \frac{1}{r_o} \right) \right) - \frac{v_m}{r_o} = 0$$

$$S_v = \frac{v_p}{v_n} = \frac{g_m + 1/r_o}{\frac{1}{R_1} + \frac{1}{R_p} + \frac{R_2}{R_2 + R_1} \left(\frac{1}{R_1} + g_m \cdot A_o \right)}$$

$$\lim_{A_o \rightarrow \infty} S_v = \frac{g_m + 1/r_o}{\frac{R_2}{R_2 + R_1} \cdot g_m A_o} = \left(1 + \frac{R_1}{R_2} \right) \cdot \frac{1 + \frac{1}{\mu}}{A_o} \rightarrow 0$$

| $\mu = g_m R_o \gg 1$

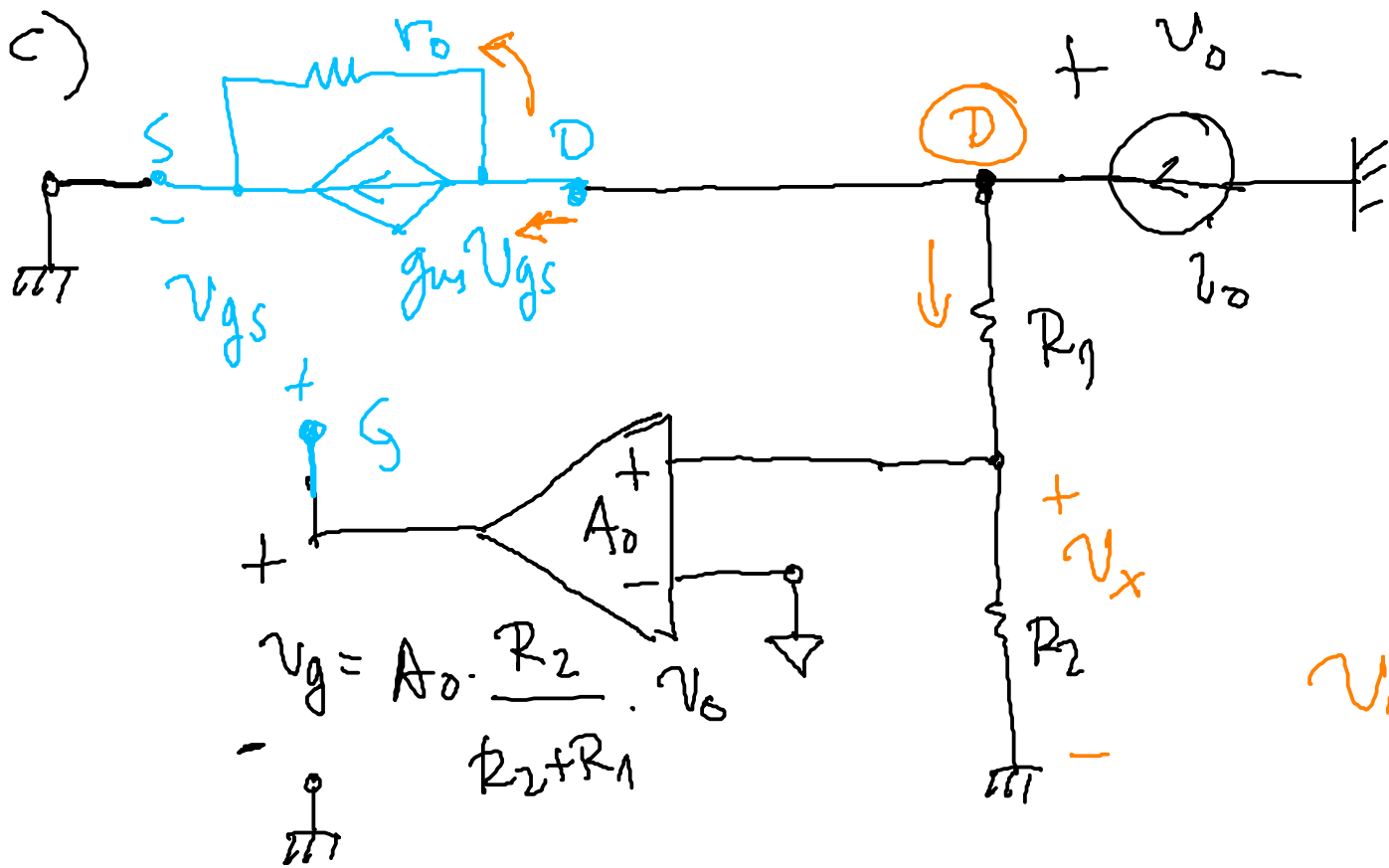

$$R_{i2} = \frac{v_o}{i_o}$$

$$v_s = 0 \text{ V}$$

$$v_x = \frac{R_2}{R_2 + R_1} \cdot v_o$$

$$v_g = A_o v_x = A_o \frac{R_2}{R_1 + R_2} v_o$$

$$\textcircled{D} \quad g_m v_{gs} + \frac{v_o}{r_o} + \frac{v_o - v_x}{R_1} = i_o$$

$$\left(g_m A_o \frac{R_2}{R_2 + R_1} + \frac{1}{r_o} + \frac{1}{R_1} - \frac{1}{R_1} \cdot \frac{R_2}{R_1 + R_2} \right) v_o = i_o$$

$$R_{iz} = \frac{v_o}{i_o} = \frac{1}{\left(\mu A_o \frac{R_2}{R_2 + R_1} + \frac{1}{r_o} + \frac{1}{R_1} - \frac{1}{R_1} \cdot \frac{R_2}{R_1 + R_2} \right)}$$

$$= \frac{1}{\mu A_o \frac{R_2}{R_1 + R_2} + \frac{1}{r_o} + \frac{1}{R_1} \left(1 - \frac{R_2}{R_1 + R_2} \right)}$$

$$= \frac{r_o}{1 + \mu A_o \frac{R_2}{R_1 + R_2} + \frac{r_o}{R_1} \left(\frac{R_1}{R_1 + R_2} \right)}$$

$$R_{iz} = \frac{r_o}{1 + \mu A_o \cdot \frac{R_2}{R_1 + R_2} + \frac{r_o}{R_1 + R_2}} \quad [\Omega]$$

* EKSTRA SPEDIVANJE: $F = \frac{R_2}{R_2 + R_1}$

$$R_{iz} = \frac{\frac{r_o}{1 + \mu A_o \cdot F}}{1 + \frac{r_o}{1 + \mu A_o \cdot F} \cdot \frac{1}{R_1 + R_2}} = \frac{(R_1 + R_2) \cdot \frac{r_o}{1 + \mu A_o \cdot F}}{(R_1 + R_2) + \frac{r_o}{1 + \mu A_o \cdot F}}$$

$$R_{iz} = (R_1 + R_2) \parallel \left(\frac{r_o}{1 + \mu A_o \cdot F} \right)$$